
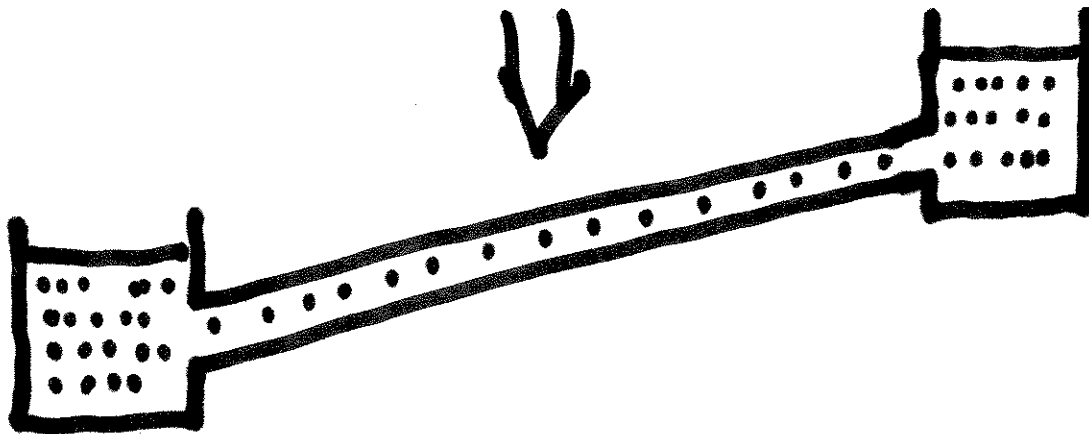


Lecture


3/1/05

ELECTRIC CURRENTS IN CONDUCTORS

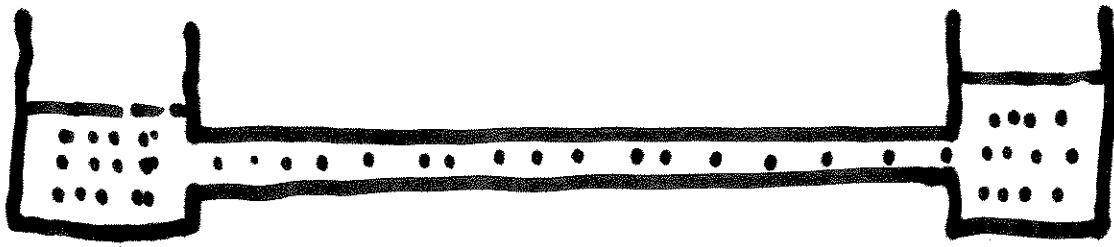

Electric Currents: Interpretation

- Our model

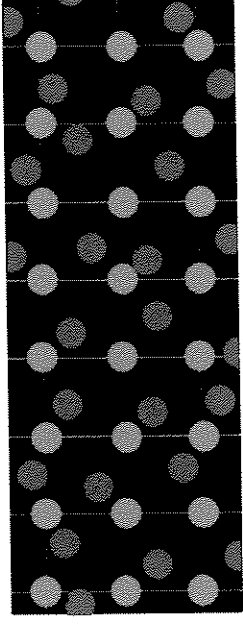


- Analogies

- Air flow

- Water flow



- Ping-pong balls and nails

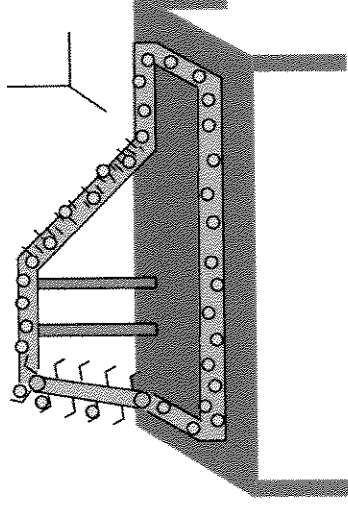

Current Footholds




- Kirchoff's laws
 - *Current conservation*: the total current entering any volume = the total current leaving that volume.
 - *Loop principle*: the sum of the voltage (pressure) drops around any loop = the sum of the rises around that loop.
 - *Ohm's law*: in any resistor, $\Delta V = IR$
- Battery rule
 - A battery is a device that maintain a constant pressure difference across its terminals.
- Wire trick
 - A wire that may be approximated as having 0 resistance is at a constant potential even when it is carrying current.



Series Rule

- In series, the current through each element is the same.
- In series, the pressure drop across the battery equals the sum of the pressure drops across each bulb.
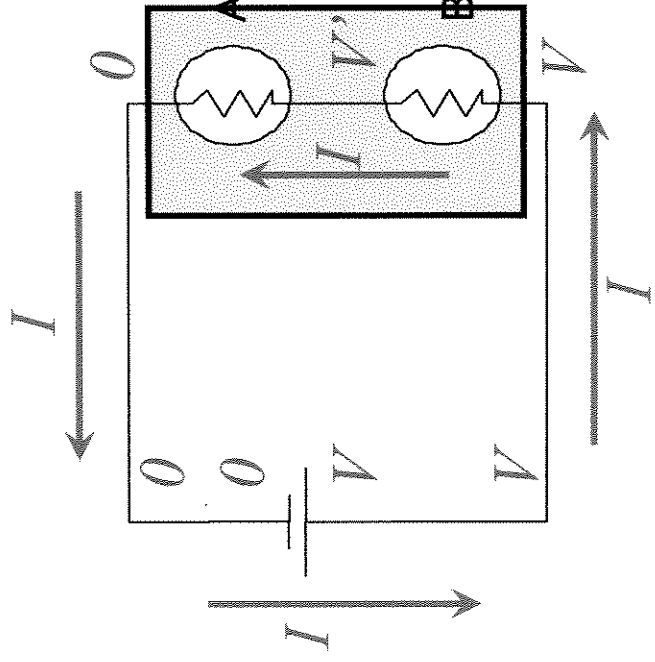
$$\begin{aligned} &=V & =V' & =V-V' \\ \Delta V &= \Delta V_A + \Delta V_B \\ IR_{eff} &= IR_A + IR_B \\ R_{eff} &= R_A + R_B \end{aligned}$$







Parallel Rule

- In parallel, the pressure drop across each element is the same.
- In parallel, the current through all the elements come together and go through the battery.

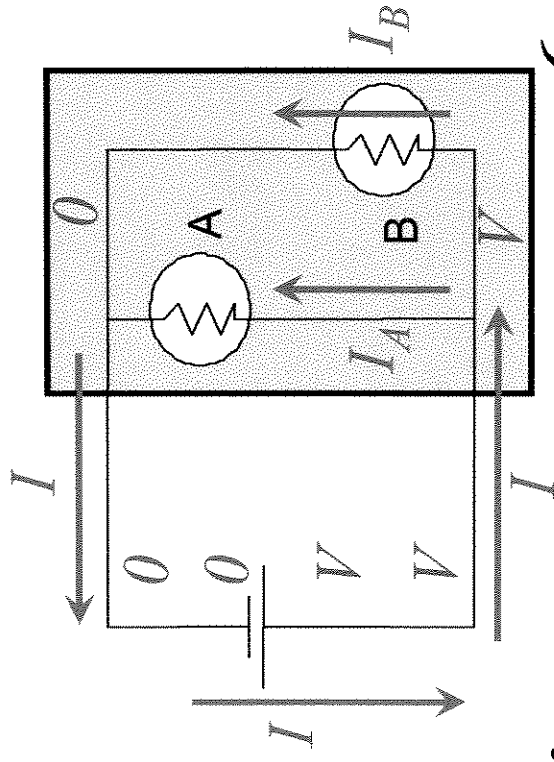
$$I = I_A + I_B$$
$$\frac{\Delta V}{R_{\text{eff}}} = \frac{\Delta V}{R_A} + \frac{\Delta V}{R_B}$$
$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_A} + \frac{1}{R_B}$$



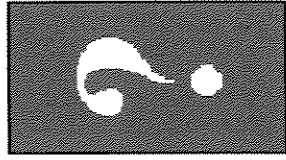- WHY DOES A LIGHT BULB LIGHT UP?
- WHAT DOES IT MEAN IF A BULB GETS BRIGHTER?




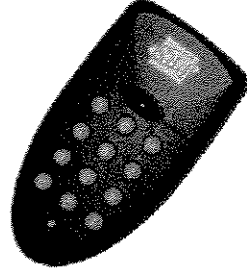
If all the bulbs are identical, then you'd expect




1. bulb B would be the brightest, A and C would be equal and next brightest, and D would be the dimmest.
2. bulbs A and C would be equal and brighter than B and D, which would be equal.
3. bulbs B and D would be equal and brighter than A and C, which would be equal.
4. bulb B would be the brightest, and A, C, and D would all be equally bright.

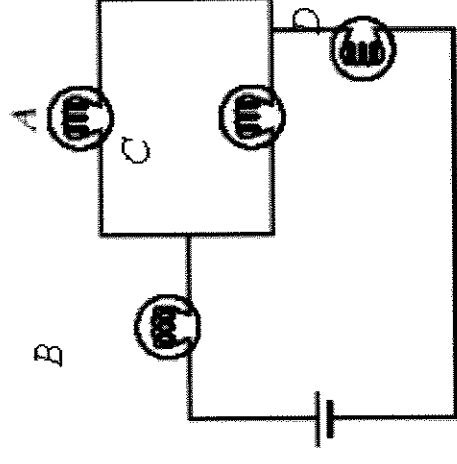5. ^{3/10/04}all bulbs would be equally bright




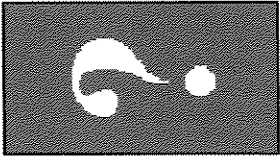

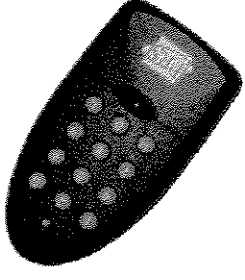The light bulbs in the circuit are identical. When the switch is closed,



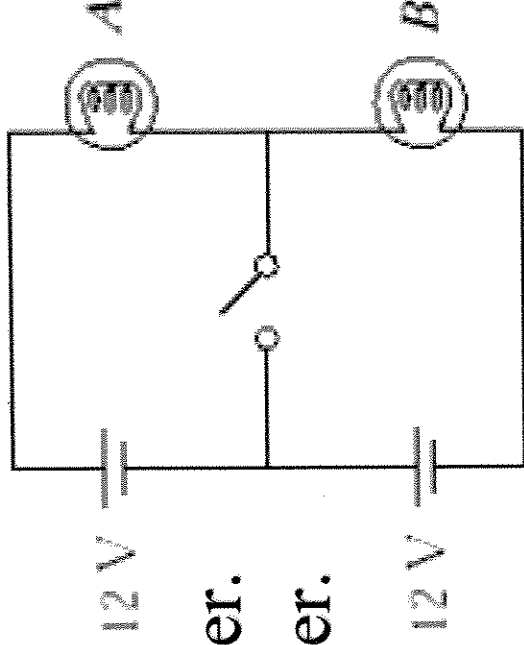1. both bulbs increase in brightness.
2. A gets brighter, B dimmer.
3. B gets brighter, A dimmer.
4. both bulbs get dimmer or go out.
5. nothing changes.



Electric Power Dissipation

- We can figure out the energy needed to push the electrons through the material against the resistance using the work-energy theorem.

$$P = \frac{\Delta W}{\Delta t}$$

= (number of charges moved) ×

(force) × (distance moved in a time Δt) / Δt

$$P = \frac{(nAL)(qE)(v\Delta t)}{\Delta t} = (nAL)qv \frac{\Delta V}{L} = (nAqv)\Delta V = I\Delta V$$