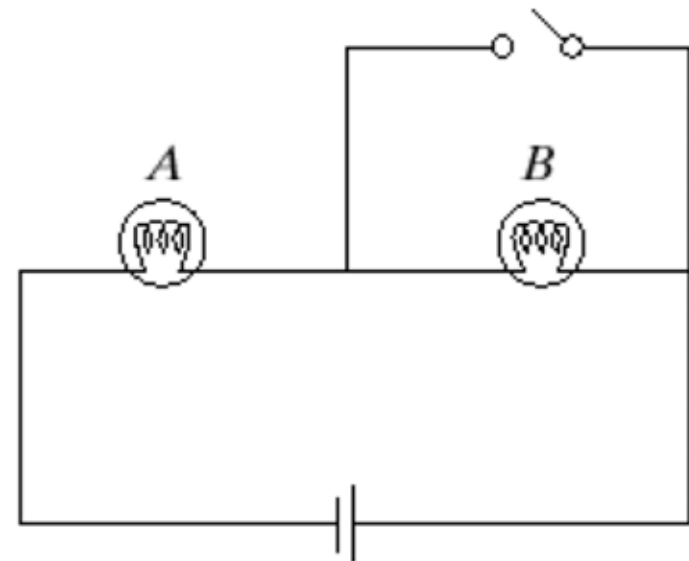




This circuit has two identical light bulbs burning with equal brightness and a single 12 V battery. When the switch is closed, the brightness of bulb A

1. increases
2. decreases
3. decreases to 0
4. remains the same





This circuit has two identical light bulbs burning with equal brightness and a single 12 V battery. When the switch is closed, the brightness of bulb B

1. increases
2. decreases
3. decreases to 0
4. remains the same

