


April 25, 2011 Physics 122 Prof. E. F. Redish

■ **Theme Music:** Joni Mitchell
You Turn Me On, I'm a Radio

■ **Cartoon:** Bob Thaves
Frank & Ernest



A cartoon by Bob Thaves from the 'Frank & Ernest' series. It is set in a clinic. A doctor, wearing a red lab coat and a stethoscope, is talking to a patient. The patient is a small, round, yellow character with a single eye and a large, open mouth. The doctor says, 'I'M FEELING SLUGGISH, SO THEY DID A BATTERY OF TESTS.' The patient replies, 'WHEN I FEEL SLUGGISH, I GET A TEST OF BATTERIES!' The cartoon is signed '© 2011 Thaves' in the bottom right corner.


4/25/11 Physics 122 1

Outline

- Quiz 9
- Recap
 - Current – Foothold ideas
 - Ohm's Law
- Electrical Analogies
- Foothold ideas for circuits (Kirchoff's principles)
 - Ohm's law
 - Flow rule
 - Loop rule
- Examples

4/25/11 Physics 122 2

Foothold Idea:
Local Neutrality




- Most matter is made of of an equal balance of two kinds of charges: positive and negative.
- Since the electric force is very strong, mostly the + and - charges overlap closely and cancel each other.
- Small imbalances in the cancellation leads to:
 - polarization forces
 - potential drop across a resistance
 - observed electric forces.

4/25/11 Physics 122 3

How small an effect? Estimation

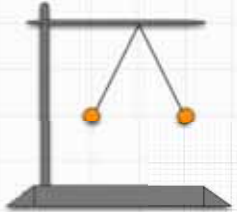- Two small aluminum spheres of mass 1 gram hang by 23 cm long non-conducting threads and are negatively charged. Suppose that the two spheres are equally charged.
- Estimate what fraction of the aluminum atoms in a sphere have an extra electron.




Answer: 1 in 30 billion

4/25/11
Physics 122
4


Picture of current flow

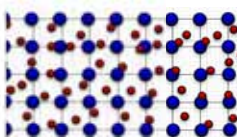- In wires (and in most other substances), the neutral matter breaks up into positive and negative bits but remains neutral.
- Current flow corresponds to (usually) one of the kinds of charge moving through the rest.
- The charges tend to not build up anywhere since the moving charges repel each other if not balanced by the other kind of charge.



4/25/11
Physics 122
7

Foothold ideas: Currents



- Charge is moving:
How much? $I = \frac{\Delta q}{\Delta t}$
- How does this relate to the individual charges? $I = q n A v$
- Constant flow means pushing force balances the drag force
 $ma = F_e - bv$
 $a = 0 \Rightarrow v = \frac{F_e}{b}$
- What pushes the charges through resistance? Electric force implies a drop in V !
 $F_e = qE$
 $\Delta V = -\frac{E}{L}$

4/25/11
Physics 122
8

Ohm's Law

- Current proportional to velocity $I = qnAv \Rightarrow v = \frac{I}{qnA}$
- Due to resistance,
Electric force proportional to velocity. $qE = bv$
- Force proportional to
"electric pressure drop"
= "electric PE" $\Delta V = EL \Rightarrow E = \frac{\Delta V}{L}$
- Therefore, current proportional
to "electric PE" $\Rightarrow \frac{q\Delta V}{L} = \frac{bI}{qnA}$

$$\Delta V = IR \quad \Delta V = I \left(\frac{bL}{q^2 nA} \right) \equiv IR$$

4/25/11

Physics 122

9

Resistivity and Conductance

- The resistance factor in Ohm's Law separates into a geometrical part (L/A) times a part independent of the size and shape but dependent on the material.
- This coefficient is called the *resistivity* of the material (ρ). Its reciprocal (g) is called *conductivity*.

$$R = \left(\frac{bL}{q^2 nA} \right) = \rho \frac{L}{A} = \frac{1}{g} \frac{L}{A}$$

4/25/11

Physics 122

10

Electric Power Dissipation

- We can figure out the energy needed to push the electrons through the material against the resistance using the WE theorem.

$$P = \text{rate of doing work (using energy)} = \frac{\Delta W}{\Delta t}$$

$$= (\text{number of charges moved}) \times$$

$$(\text{force}) \times (\text{distance moved in a time } \Delta t)$$

$$P = \frac{(nAL)(qE)(v\Delta t)}{\Delta t} = (nAL)qv \frac{\Delta V}{L} = (qnAv)\Delta V = I\Delta V$$

4/25/11

Physics 122

11

Units of power

- Since the units of work (energy) is the Joule, the unit of power is the Joule/second.
– 1 Watt = 1 Joule/second (definition)
- Our analysis shows that
current x voltage = power.
- 1 Watt = 1 Ampere x 1 Volt

$$P = I\Delta V$$


4/25/11

Physics 122

12

Electric circuit elements

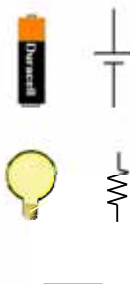- Batteries — devices that maintain a constant electrical pressure difference across their terminals (like a water pump that raises water to a certain height).
- Resistances — devices that have significant drag and oppose current. Pressure will drop across them.
- Wires — have very little resistance. We can ignore the drag in them (mostly — as long as there are other resistances present).



4/25/11

Physics 122

13

Analogy 1 (Drude model): Ping-pong balls and nail board

- In this analogy, we treat the electrons as small particles that can move freely through the conductor. (ping-pong balls)
- The ions that form the fixed body of the conductor are treated as fixed. (nails)
- The electron move freely between the ions until they hit them. Then they scatter in a random direction.

4/25/11

Physics 122

14

Nail Board: Two kinds of regions

■ Ping-pong balls and nail board

No resistance
constant v
even without gravity

No resistance
constant v
even without gravity

Resistance
constant v
even with gravity
($mg=bv$)

4/25/11 15

Properties of analogy 1

- While running horizontally in a region with no resistance (aligned nails), the balls continue with a constant velocity without need for pushing.
- Running downhill through a region with resistance (random nails), the balls continue at the same constant velocity, but are pushed by gravity.
- To get back they have to be carried up by some kind of pump that restores the balls from a region of low PE back to a region of high PE (the demonstrator lifts the balls back up to the top).

4/25/11 Physics 122 16

Analogy 2: The rope model

- Since like charges repel strongly, there can't be a buildup of charge anywhere in the circuit (unless we make a special arrangement -- capacitance).
- Moving charges push other movable charges in front of them. The electrons move like links in a chain or rope.

4/25/11 Physics 122 17

Properties of analogy 2

- In a simple loop, the rope keeps moving around.
- A battery is like a person holding the rope and pulling it, causing a tension throughout the rope.
- A resistor is like a person squeezing the rope, having it pulled through her hands. The friction generates heat.
- The more people are squeezing, the slower the rope goes, even if the battery pulls with the same tension.

4/25/11

Physics 122

18

Analogy 3: Water flow


- The rope analogy fails because electrons can go either way at a junction. A current can split in a way a rope cannot.
- Water flow is a useful analogy because water
 - can divide
 - is conserved and cannot be compressed.

4/25/11

Physics 122

19

Water Model

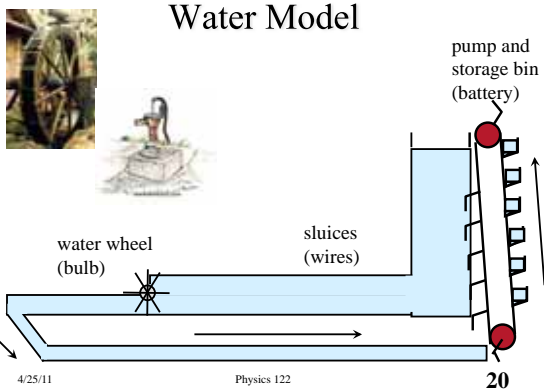

Properties of analogy 3

- Water can divide and recombine.
But: total flow into any volume = total flow out of any volume – no build up.
- Going around any loop – sum of potential rises (positive Δh) equals sum of potential drops (negative Δh).

4/25/11

Physics 122

21

Analogy 4: Air flow

- Pressure is analogous to electric potential.
- Pressure drop produces flow.
- Amount of flow depends on what is connected across a pressure drop.



4/25/11

Physics 122

22

Foothold ideas (Kirchoff's Rules)

- Flow Rule
 - The total amount of current flowing into any point in a network equals the amount flowing out (no significant build-up of charge anywhere).
- Potential Rule
 - Following around any loop in an electrical network the potential has to come back to the same value (sum of drops = sum of rises).
- Ohm's Rule
 - When a current I passes through a resistance R , there is a voltage drop across the resistor of an amount $\Delta V = IR$



4/25/11

Physics 122

23

Very useful heuristic

■ The Constant Potential Trick (CPT)

- Along any part of a circuit with 0 resistance, then $\Delta V = 0$, i.e., the voltage is constant since in any circuit element

$$\Delta V = IR$$

4/25/11


Physics 122

24

What happens when we combine resistors?

■ Consider increasing the width or the length of a resistor.

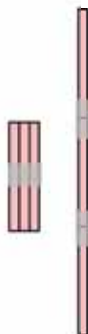- Analogy with air flow
- Using the equation for resistance
- Analyze in terms of potential drops and current flow



4/25/11

Physics 122

26


Series and Parallel Rules

- In series, the current through each element is the same.

$$\Delta V = \Delta V_A + \Delta V_B$$

$$IR_{\text{eff}} = IR_A + IR_B$$

$$R_{\text{eff}} = R_A + R_B$$

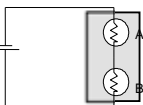


- In parallel, the pressure drop across each element is the same.

$$I = I_A + I_B$$

$$\frac{\Delta V}{R_{\text{eff}}} = \frac{\Delta V}{R_A} + \frac{\Delta V}{R_B}$$
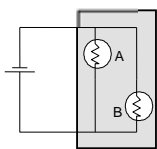
$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_A} + \frac{1}{R_B}$$



4/25/11

Physics 122

27
