

April 27, 2011 Physics 122 Prof. E. F. Redish

■ **Theme Music:** Maynard Ferguson
High Voltage

■ **Cartoon:** Pat Brady
Rose is Rose

Copyright © 1997 United Feature Syndicate, Inc.
Redistribution in whole or in part prohibited

4/27/11 Physics 122 1

Outline

- Go over Quiz 9
- Recap Foothold ideas
- Foothold ideas for circuits
(Kirchoff's principles)
 - Ohm's law
 - Flow rule
 - Loop rule
- Examples


4/27/11 Physics 122 2

Quiz 9

	9.1	9.2	9.3	9.4
a	77%	2%	73%	16%
b	0%	14%	18%	58%
c	2%	83%	5%	6%
d	2%	0%	2%	6%
e	2%	0%	1%	3%
bc	0%	0%	2%	12%
cd	17%	0%	0%	0%

4/27/11 Physics 122 4

Foothold Idea: Local Neutrality




- Most matter is made of of an equal balance of two kinds of charges: positive and negative.
- Since the electric force is very strong, mostly the + and - charges overlap closely and cancel each other.
- Small imbalances in the cancellation leads to:
 - polarization forces
 - potential drop across a resistance
 - observed electric forces.

4/27/11 Physics 122

5

Foothold ideas: Currents



- Charge is moving:
How much? $I = \frac{\Delta q}{\Delta t}$
- How does this relate to the individual charges? $I = q n A v$
- Constant flow means pushing force balances the drag force
 $ma = F_e - bv$
 $a = 0 \Rightarrow v = F_e / b$
- What pushes the charges through resistance? Electric force implies a drop in V !
 $F_e = qE$
 $E = -\frac{\Delta V}{L}$

4/27/11 Physics 122

6

Units of power

- Since the units of work (energy) is the Joule, the unit of power is the Joule/second.
 - 1 Watt = 1 Joule/second (definition)
- Our analysis shows that current x voltage = power.
- 1 Watt = 1 Ampere x 1 Volt


$$P = I \Delta V$$

4/27/11 Physics 122

7

Electric circuit elements

- **Batteries** — devices that maintain a constant electrical pressure difference across their terminals (like a water pump that raises water to a certain height).
- **Resistances** — devices that have significant drag and oppose current. Pressure will drop across them.
- **Wires** — have very little resistance. We can ignore the drag in them (mostly — as long as there are other resistances present).

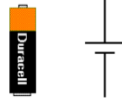

4/27/11

Physics 122

8

Foothold ideas (Kirchoff's Rules)

- **Flow Rule**
 - The total amount of current flowing into any point in a network equals the amount flowing out (no significant build-up of charge anywhere).
- **Potential Rule**
 - Following around any loop in an electrical network the potential has to come back to the same value (sum of drops = sum of rises).
- **Ohm's Rule**
 - When a current I passes through a resistance R , there is a voltage drop across the resistor of an amount $\Delta V = IR$



4/27/11

Physics 122

9

Very useful heuristic

- **The Constant Potential Trick (CPT)**
 - Along any part of a circuit with 0 resistance, then $\Delta V = 0$, i.e., the voltage is constant since in any circuit element

$$\Delta V = IR$$


4/27/11

Physics 122

10

What happens when we combine resistors?

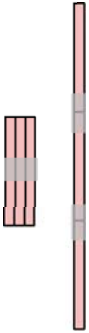- Consider increasing the width or the length of a resistor.
 - Analogy with air flow
 - Using the equation for resistance
 - Analyze in terms of potential drops and current flow



4/27/11
Physics 122
12

Series and Parallel Rules

- In series, the current through each element is the same.

$$\Delta V = \Delta V_A + \Delta V_B$$


$$IR_{eff} = IR_A + IR_B$$

$$R_{eff} = R_A + R_B$$
- In parallel, the pressure drop across each element is the same.

$$I = I_A + I_B$$

$$\frac{\Delta V}{R_{eff}} = \frac{\Delta V}{R_A} + \frac{\Delta V}{R_B}$$

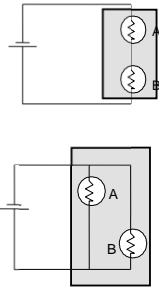
$$\frac{1}{R_{eff}} = \frac{1}{R_A} + \frac{1}{R_B}$$



4/27/11
Physics 122
13

Sample Problem

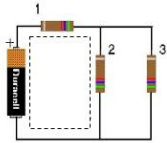
- The circuit diagram shown at the right contains a 1.5 Volt battery and three identical $50\ \Omega$ resistors. Find the current in and voltage drop across each of the resistors.



5/25/10
Physics 122
16

Sample Problem

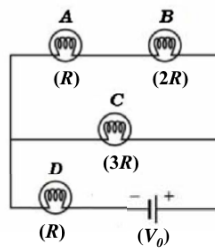- How do the currents in resistors A and B compare?
- How do the voltage drops across resistors A and B compare?
- How does the current in and voltage drop across resistor C compare to those in A and B?
- Find the current in resistor D.



$$I_0 = V_0/R$$


4/27/11

Physics 122

17

Sample Problem

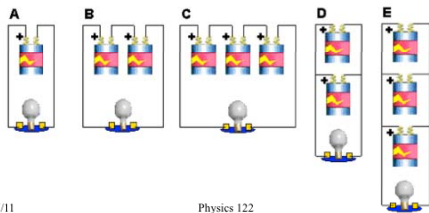- Identical batteries are connected in different arrangements to the same light bulb. Rank these arrangements on the basis of bulb brightness from the highest to the lowest.



4/27/11

Physics 122

18
