


April 29, 2011 Physics 122 Prof. E. F. Redish

■ **Theme Music:** Rustycycle
Capacitance

■ **Cartoon:** Bob Thaves
Frank & Ernest



4/29/11 Physics 122 1

Outline

■ Electric Circuits Examples


■ The Capacitor

- Example
- Charging
- Capacitor Equations

4/29/11 Physics 122 2

Sample Problem


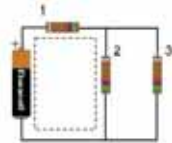
■ The circuit diagram shown at the right contains a 1.5 Volt battery and three identical $50\ \Omega$ resistors. Find the current in and voltage drop across each of the resistors.



4/29/11 Physics 122 5

Sample Problem

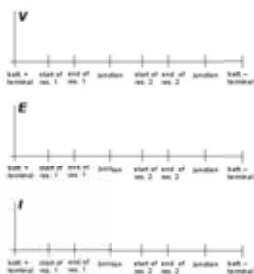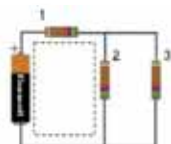- Track the voltage and electric field a test charge would measure as it followed the indicated loop through the circuit. Show the current one would measure as one went around that loop.



4/29/11

Physics 122

6

Capacitance

- What we see in the previous problem is the reflection of an explicit assumption we have made in our discussion of circuits so far:
 - that there is no charge build up anywhere in the circuit.
- But there are possibilities to build up small non-neutral regions of charge if they are carefully matched.


4/29/11

Physics 122

10

The Capacitor

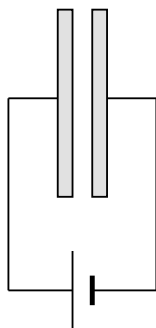- Suppose we hook two parallel conducting plates up to a battery. What happens?




4/29/11

Physics 122

11

Storing electrical energy: The capacitor

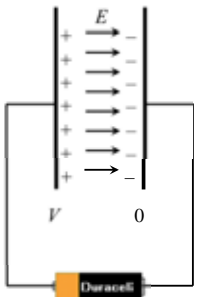
- Two parallel metal plates of area A separated by a distance d .
- Connect the plates to the two sides of a battery.



4/29/11 Physics 122 13

Charging a capacitor

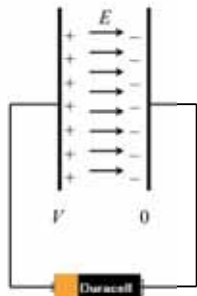- What is the potential difference between the plates?
- What is the field around the plates?
- How much charge is on each plate?



4/29/11 Physics 122 14

Capacitor Equations

$$\Delta V = E\Delta x = Ed$$

$$E = 4\pi k_c \sigma = 4\pi k_c \frac{Q}{A} \Rightarrow Q = \left(\frac{A}{4\pi k_c} \right) E$$

$$Q = \left(\frac{A}{4\pi k_c d} \right) \Delta V$$

$4\pi k_c$ is often written as " $1/\epsilon_0$ "

$$Q = C\Delta V$$

What does this "Q" stand for?

Physics 122 17

Dielectrics

- In electrical systems, we want to store as large a charge separation as we can, but creating potential differences is expensive. We would like to find ways of reducing ΔV while keeping Q the same.
- In biological systems, we often have charge separations, but they are almost always separated by spaces containing fluids – not by empty space.
- It turns out that the answer to the first problem is provided by the second observation.


4/29/11

Physics 122

20

Consider what happens with a conductor

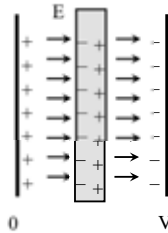- The potential difference is produced by adding up $E \Delta s$.
- If we can reduce E along the path, we can reduce ΔV .
- Inside a static conductor, there can be no E field. (Why not?)
- What happens if we put a conducting sheet between the plates?



4/29/11


Physics 122

21

Conductors

- Putting a conductor inside a capacitor eliminates the electric field inside the conductor.
- The distance, d' , used to calculate the ΔV is only the place where there is an E field, so putting the conductor in reduces the ΔV for a given charge.

$$C = \frac{1}{4\pi k_C} \frac{A}{d'}$$

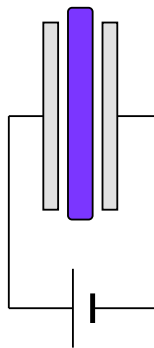


4/29/11

Physics 122

22

Consider what happens with an insulator

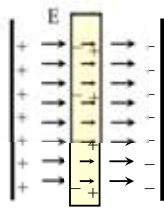- We know that charges separate even with an insulator.
- This reduces the field inside the material, just not to 0.
- The field reduction factor is defined to be κ .



$$E_{\text{inside material}} = \frac{1}{\kappa} E_{\text{if no material were there}}$$

4/29/11 Physics 122

23


Capacitors filled with an insulating material

$$E = \frac{1}{\kappa} \frac{\sigma}{\epsilon_0}$$

$$E = \frac{Q}{\kappa \epsilon_0 A}$$

$$\Delta V = Ed = \left(\frac{d}{\kappa \epsilon_0 A} \right) Q$$

$$C = \kappa \frac{\epsilon_0 A}{d}$$

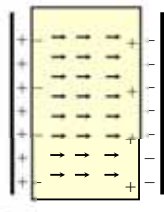


4/29/11 Physics 122

24

Dielectrics

- If a non-conductor is put between the plates, there is still some polarization reducing the field so the voltage required for a given charge is reduced, i.e., C is increased.
- The factor (assuming the space between the plates is filled) is called the dielectric constant, κ .
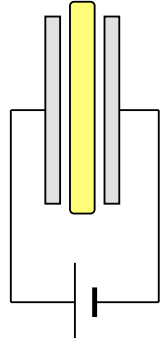
$$C = \kappa \frac{1}{4\pi k_C} \frac{A}{d}$$



4/29/11 Physics 122

25
