
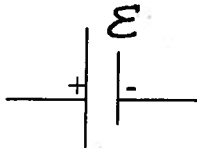


DEVICES - AC CIRCUITS

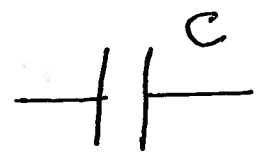
Battery Source of Coulomb \vec{E} -field
Output is *emf*: ϵ



Capacitor: Container for \vec{E} -field $C = \frac{Q}{V}$
Potential Energy $U_E = \frac{Q^2}{2C}$
 $\eta_E =$ Energy stored per $m^3 = \frac{1}{2} \epsilon_0 E^2$
 $\epsilon_0 = 9 \times 10^{-12} F/m$



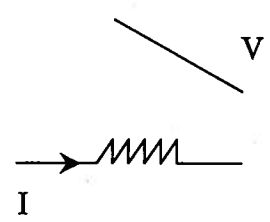Resistor: Represents that it costs energy to transport charge through a conductor




$$R = \frac{V}{I} \quad [J = \sigma E]$$

Power loss $P = I^2 R = \frac{V^2}{R}$

Inductor: A time varying current causes a Non-Coulomb \vec{E} -field, induced *emf*, $L = \frac{-\epsilon}{(\Delta i / \Delta t)}$

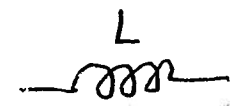Container for \vec{B} -field, Potential Energy $U_B = \frac{1}{2} Li^2$




$\eta_B =$ Energy stored per $m^3 = \frac{B^2}{2\mu_0}$

A.C. Generator: Wire loops of area A rotated at ω rad/s in a \vec{B} -field. Generates non-coulomb \vec{E} -field in the loops, produces an *emf*: $\epsilon = \omega NBA \sin(\omega t)$

Where $N = \#$ of turns in the loop. Hence *ac-generator*


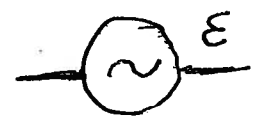
$\Phi_B = NBA \cos(\theta)$
where θ is angle between \hat{n} and \vec{B}



Rottn by ω rad/s makes $\theta = \omega t$, $\Phi_B = NBA \cos \omega t$
So $\frac{\Delta \Phi_B}{\Delta t} = - NBA \omega \sin \omega t$, $\epsilon = -\frac{\Delta \Phi_B}{\Delta t} = \omega NBA \sin \omega t$


I. RC with battery, close switch at $t=0$, current flows immediately, potential across C appears

later $\varepsilon = \frac{q}{C} + iR$

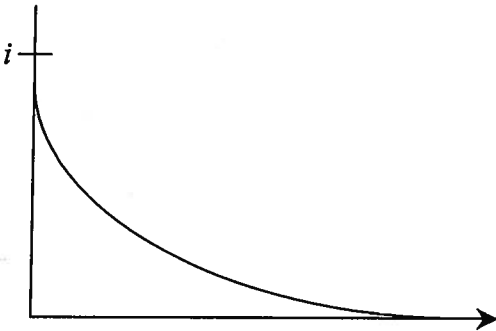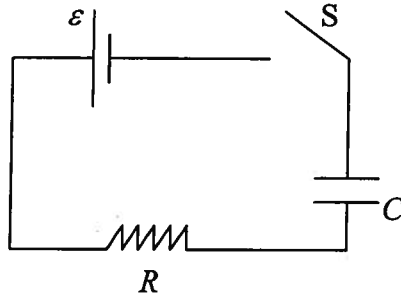

$$i = \frac{\varepsilon}{R} e^{-t/RC}$$



$$\tau = RC$$

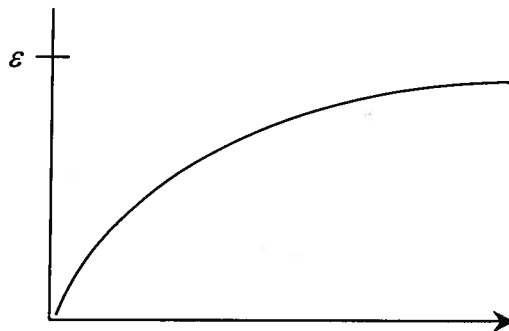

$$v_c = \varepsilon [1 - e^{-t/RC}]$$

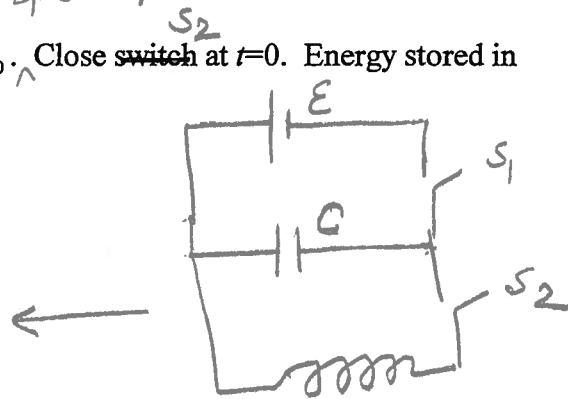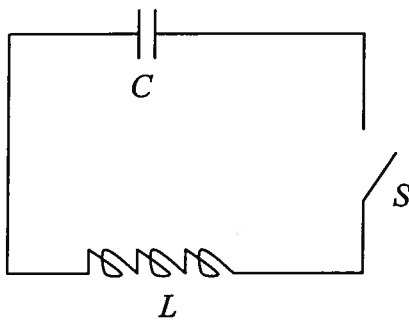III. LC-Circuit: Undamped Oscillator

Close S_1 , First charge C to Q_0 . Close switch at $t=0$. Energy stored in capacitor $U_E = \frac{Q_0^2}{2C}$




Charge begins to flow. Total Energy = (Energy in \vec{E} -field) + (Energy in \vec{B} -field)
 = (Energy in C) + (Energy in L)

$$\frac{Q_0^2}{2C} = \frac{q^2}{2C} + \frac{1}{2} L \left(\frac{\Delta q}{\Delta t} \right)^2$$

Recognize, similarity to spring-mass oscillator
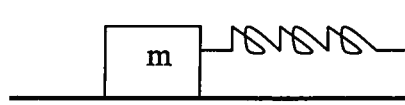
$$\frac{1}{2}kA^2 = \frac{1}{2}kx^2 + \frac{1}{2}m\left(\frac{\Delta x}{\Delta t}\right)^2$$



$$x \rightarrow q$$

$$x = A \cos \omega t$$

$$m \rightarrow L$$



$$\omega_0 = \sqrt{\frac{k}{m}}$$

$$k \rightarrow \frac{1}{C}$$


Now

$$q = Q_0 \cos \omega_0 t$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

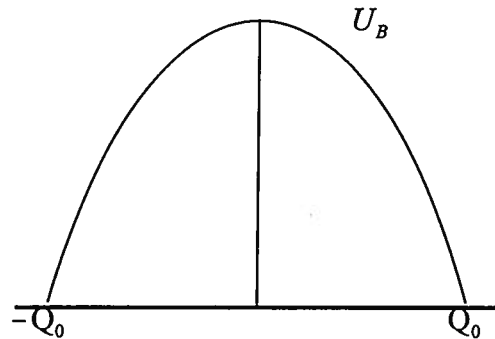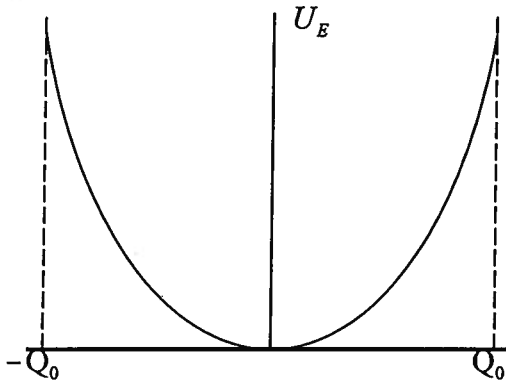


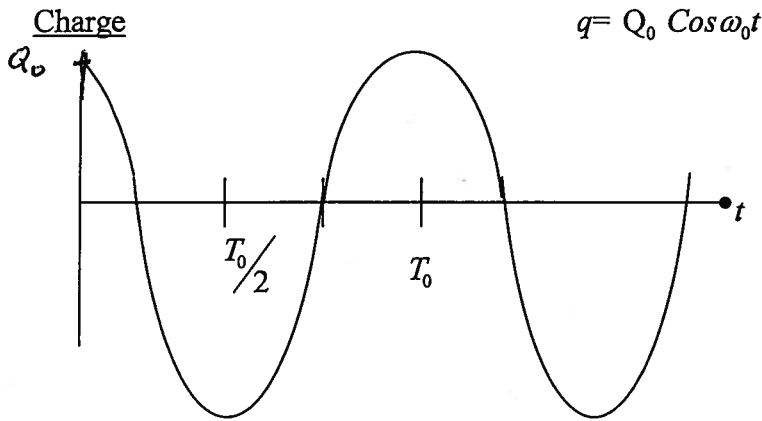\vec{E} -field collapses giving rise to \vec{B} -field and vice versa.




$$i = -Q_0 \omega_0 \sin \omega_0 t$$
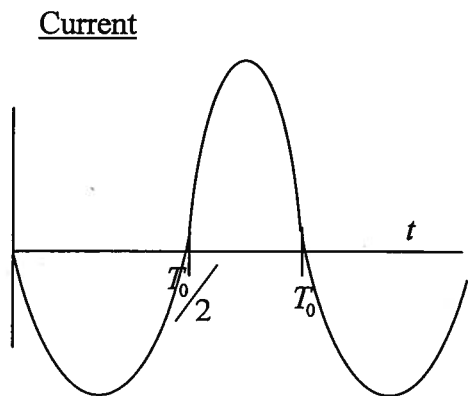
$$\text{Period } T = \frac{2\pi}{\omega_0}$$



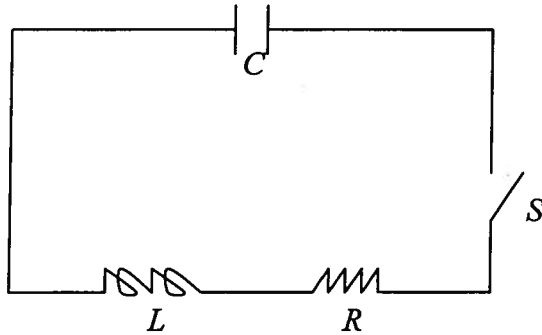IV. LCR-CIRCUIT: DAMPED OSCILLATOR.

At $t=0$, charge C to Q_0 close switch. Now driving i through R costs $i^2 R$ per second.



So $\left(\frac{q^2}{2C} + \frac{1}{2}Li^2\right)$ IS NOT CONSTANT

$$\frac{\Delta\left(\frac{q^2}{2C} + \frac{1}{2}Li^2\right)}{\Delta t} = -i^2 R$$


-ive sign on right because energy is being lost (R is getting warmer).

Now $q = Q_0 e^{-Rt/2L} \cos \omega t$

$$\omega = \omega_0 \left[1 - \frac{1}{(2\omega_0 \tau)^2} \right]^{1/2}$$

$$\tau = \frac{L}{R}$$

$$\omega_0 \tau = \text{Quality factor} = Q_e$$

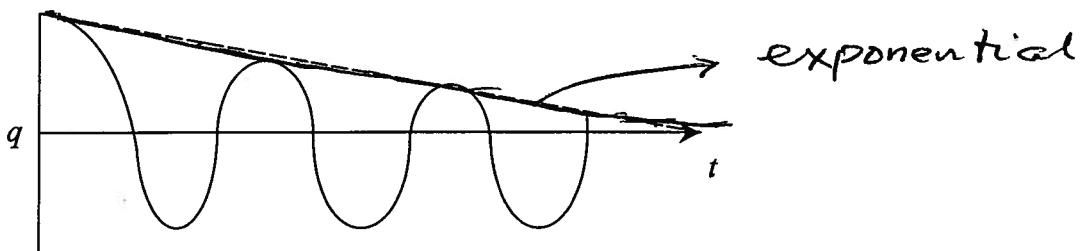


Note 1: smaller R , larger the duration for which the oscillations persist.

Note 2: R plays role of friction; as always energy lost goes to raise temperature. Electrical Equivalent of Heat.

CIRCUITS: AC

I. Resistor and Generator

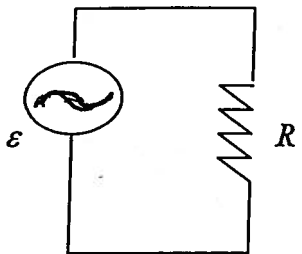

$$V_R = IR$$

so

If $\epsilon = \epsilon_0 \sin \omega t$

$$i = \frac{\epsilon_0}{R} \sin \omega t$$


Current and voltage are in phase.

Power

$$P(t) = iv$$

$$= \frac{\epsilon_0}{R} \sin^2 \omega t$$
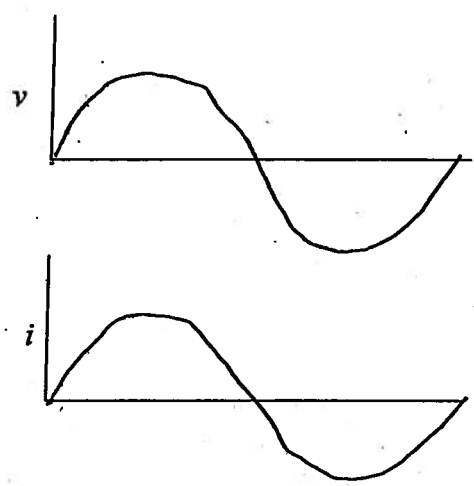
$$\langle \sin^2 \omega t \rangle = \frac{1}{2}$$



averaged over a cycle. $\langle P \rangle = \frac{\epsilon_0^2}{2R} = \frac{i_0 \epsilon_0}{2} = \frac{i_0^2 R}{2}$ and the power loss is as if R was connected to a battery ~~with~~ ^{whose} $\epsilon = \frac{\epsilon_0}{\sqrt{2}}$. In this sense one talks of $\frac{\epsilon_0}{\sqrt{2}}$ and $\frac{i_0}{\sqrt{2}}$ as root-mean-square or r.m.s. voltage and current.

R.m.s. voltage in our house, $V_{rms} = 115$ Volts
 $f = 60$ Hz
 $\omega = 377$ rad/sec
 $V_{max} \approx 155$ Volts