

## SOLUTIONS - 5 - FORMULAE

Battery  $\begin{array}{c} + \\ | \\ \text{E} \\ | \\ - \end{array}$  Capacitor  $C = \frac{Q}{V}$

Parallel Plate (air filled)  $C_0 = \frac{\epsilon_0 A}{d}$   $\vec{E}_0 = \frac{\sigma}{\epsilon_0} \hat{x}$

Parallel Plate (with dielectric)  $C_k = \frac{k \epsilon_0 A}{d}$   $\vec{E}_k = \left( \frac{\sigma - \sigma_b}{\epsilon_0} \right) \hat{x}$

$$E_k = \frac{E_0}{k}$$

dielectric const.  $k = \frac{\sigma}{\sigma - \sigma_b}$

Capacitors in series: Q's are common  
V's add

$$\text{Hence } \frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \quad \text{or } \frac{1}{C_s} = \sum \left( \frac{1}{C_i} \right)$$

Capacitors in parallel: V's are common  
Q's add

$$\text{Hence } C_p = C_1 + C_2 + C_3 \quad \text{or } C_p = \sum C_i$$

Energy stored in capacitor resides<sup>2</sup> in E-field.

Air filled  $W_E = \frac{Q^2}{2C_0} = \frac{Q^2}{2\epsilon_0} \quad \text{hence } \eta_E = \frac{1}{2} \epsilon_0 E_0^2$

With Dielectric  $W_E = \frac{Q^2}{2C_k} \quad \text{hence } \eta_E = \frac{1}{2} \epsilon_0 k E_k^2$

$\eta$  is energy per  $m^3$  of  $\vec{E}$  field

## FORMULAE - CHAPTER 17

Current  $I = \frac{\Delta Q}{\Delta t}$

Note: electrons carry -ive charge  
so electrons moving left yield  
current going right



$$I = \underset{\rightarrow}{J} \cdot \underset{\rightarrow}{A}$$

$$I = n_e e A v_d$$

Definition of  $R = (V/I)$

$$V = IR$$


$$R = \frac{\rho l}{A} = \frac{l}{\sigma A}$$

$$V = \frac{\rho J A}{\sigma A}$$

$$J = \sigma \frac{V}{l}$$

$$\underline{J} = \sigma \underline{E}$$

16-31 (a)

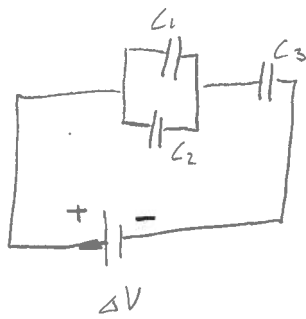

$$C_1 = 4.00 \mu\text{F}$$

$$C_2 = 2.00 \mu\text{F}$$


$$C_3 = 3.00 \mu\text{F}$$

$$\Delta V = 12 \text{ V}$$

$C_1$  and  $C_2$  are in parallel

$$C_{\text{eq}12} = C_1 + C_2 = 6.00 \mu\text{F}$$

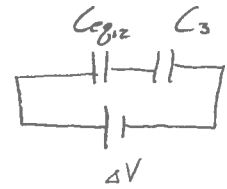$C_{\text{eq}12}$  and  $C_3$  are in series



$$\frac{1}{C_{\text{eq}123}} = \frac{1}{C_{\text{eq}12}} + \frac{1}{C_3} = \frac{1}{2.00 \mu\text{F}}$$

$$C_{\text{eq}123} = 2.00 \mu\text{F}$$

(b)

$$C_{\text{eq}12} = \frac{Q_{12}}{\Delta V_{12}}$$

$Q_{12} = Q_3$  for capacitors in series

$$C_3 = \frac{Q_3}{\Delta V_3}$$

$$\Delta V_{12} + \Delta V_3 = \Delta V$$

solve capacitance equations for respective  $\Delta V$  and add

$$\Rightarrow \frac{Q_3}{C_3} + \frac{Q_{12}}{C_{\text{eq}12}} = \Delta V$$

$$Q_3 = Q_{12} = \frac{C_3 C_{\text{eq}12}}{C_3 + C_{\text{eq}12}} \Delta V = 24.0 \mu\text{C}$$

$$\Delta V_3 = \frac{Q_3}{C_3} = 8.00 \text{ V}$$

$$C_1 = \frac{Q_1}{\Delta V_1}$$

$\Delta V_1 = \Delta V_2$  capacitors in parallel

$$C_2 = \frac{Q_2}{\Delta V_2}$$

$$Q_1 + Q_2 = Q_{12}$$

$$C_1 \Delta V_1 + C_2 \Delta V_2 = Q_{12}$$



$$\Delta V_1 = \Delta V_2 = \frac{Q_{12}}{C_1 + C_2} = 4.00 \text{ V}$$

$$Q_1 = C_1 \Delta V_1 = 16.0 \mu\text{C}$$

$$Q_2 = C_2 \Delta V_2 = 8.00 \mu\text{C}$$


16-37 FIRST CALCULATE CHARGE ON  $25\mu\text{F}$  and  $40\mu\text{F}$

$$Q = CV$$

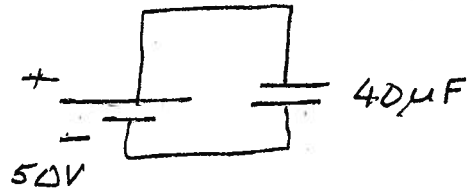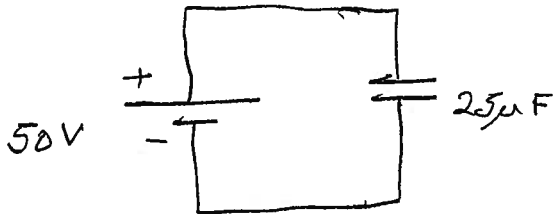

$$Q_{25} = (50 \times 25 \times 10^{-6}) \text{ C} \\ = 1.25 \times 10^{-3} \text{ C}$$

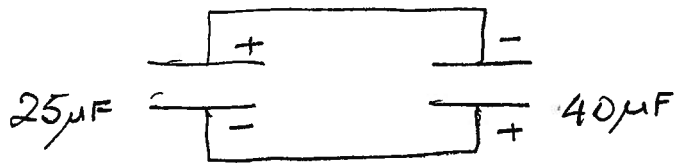
$$Q_{40} = (50 \times 40 \times 10^{-6}) \text{ C} \\ = 2.00 \times 10^{-3} \text{ C}$$



Note: + to -  
- to +.

Charge is conserved so Total charge now is  
 $Q_{40} - Q_{25} = (2 \times 10^{-3} - 1.25 \times 10^{-3}) \text{ C}$   
 $= 7.5 \times 10^{-4} \text{ C} = 750 \mu\text{C}$

and the capacitors look like

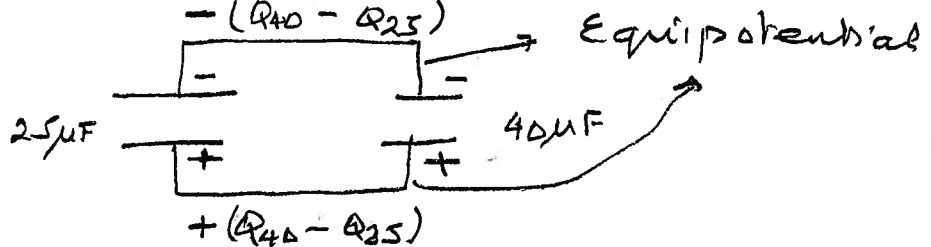

Because conductor is Equipotential  $V_{25} = V_{40}$


$$\frac{Q_{25}}{25 \times 10^{-6}} = \frac{Q_{40}}{40 \times 10^{-6}} = V_{25} = V_{40}$$

$$\frac{7.5 \times 10^{-4} - Q_{40}}{25 \times 10^{-6}} = \frac{Q_{40}}{40 \times 10^{-6}} \quad Q_{40} = 462 \mu\text{C}$$

$$Q_{25} = 750 - 462 \mu\text{C} = 288 \mu\text{C}$$

$$V_{40} = \frac{Q_{40}}{40} = 11.5 \text{ V}$$

1644

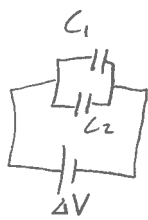

$$C_1 = 25.0 \mu\text{F}$$

$$C_2 = 5.00 \mu\text{F}$$

$$\Delta V = 100 \text{ V}$$


$$(a) \quad E = \frac{1}{2} C (\Delta V)^2$$

we want energy stored in both capacitors,  
so use equivalent capacitance

$$C_1 + C_2 = C_{\text{eq}} = 30.0 \mu\text{F} = 30.0 \times 10^{-6} \text{ F}$$

$$E = \frac{1}{2} (30.0 \times 10^{-6} \text{ F}) (100 \text{ V})^2 = 0.15 \text{ J}$$
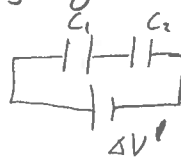
$$(b) \quad E = \frac{1}{2} C (\Delta V)^2$$



now  $E_{\text{tot}}$  is known (.15 J) and we

want the equivalent capacitance in series

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{25.0 \mu\text{F}} + \frac{1}{5.00 \mu\text{F}} = \frac{6}{25.0 \mu\text{F}}$$


$$C_{\text{eq}} = \frac{25.0 \mu\text{F}}{6} \approx 4.17 \mu\text{F} = 4.17 \times 10^{-6} \text{ F}$$

solve for  $\Delta V$

$$\sqrt{\frac{2E}{C}} = (\Delta V) = \sqrt{\frac{2(.15) \text{ J}}{4.17 \times 10^{-6} \text{ F}}} \approx 268 \text{ V}$$

H50

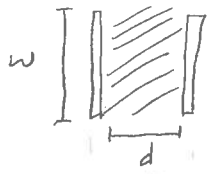$C = K \epsilon_0 \frac{A}{d}$  plate capacitor with dielectric



$$K = 3.70$$

$$C = 9.50 \times 10^{-8} \text{ F}$$

$$d = .0250 \text{ mm}$$

$$w = 7.00 \text{ cm}$$

width  $\cdot$  length = Area of each plate

$$w \cdot L = A$$

$$C = K \epsilon_0 \frac{w \cdot L}{d}$$

$$\Rightarrow L = \frac{C d}{K \epsilon_0 w}$$

$$L = \frac{(9.50 \times 10^{-8} \text{ F})(.0250 \times 10^{-3} \text{ m})}{(3.70)(8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2})(.07 \text{ m})} \approx 1.04 \text{ m}$$

16-54

$$C_p = C_1 + C_2 \rightarrow \textcircled{1}$$

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}, \quad C_s = \frac{C_1 C_2}{C_1 + C_2} \rightarrow \textcircled{2}$$

Multiply  $\textcircled{1}$  and  $\textcircled{2}$

$$C_s C_p = C_1 C_2, \quad C_1 = \frac{C_s C_p}{C_2}$$

substitute in  $\textcircled{1}$   $C_p = \frac{C_s C_p}{C_2} + C_2$

$$\text{or } C_p C_2 = C_s C_p + C_2^2$$


$$C_2^2 - C_p C_2 + C_s C_p = 0$$

Solve quadratic  $C_2 = \frac{C_p \pm \sqrt{C_p^2 - 4C_s C_p}}{2}$

$$C_1 = C_p - C_2 = \frac{2C_p - C_p \mp \sqrt{C_p^2 - 4C_s C_p}}{2}$$

$$= \frac{C_p \mp \sqrt{C_p^2 - 4C_s C_p}}{2}$$

16-57.

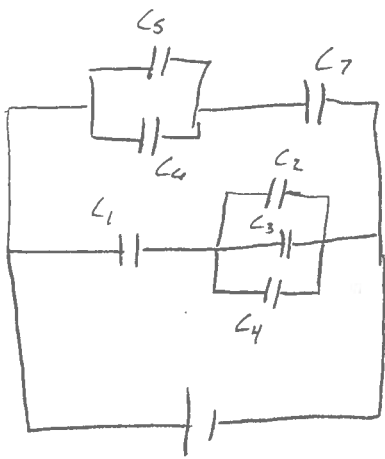

$$C_1 = 6.00 \mu F$$

$$C_2 = 2.00 \mu F$$

$$C_3 = 3.00 \mu F$$

$$C_4 = 7.00 \mu F$$


$$C_5 = 5.00 \mu F$$

$$C_6 = 4.00 \mu F$$

$$C_7 = 3.00 \mu F$$

This problem involves finding many equivalent capacitors. Start with the first parallel set
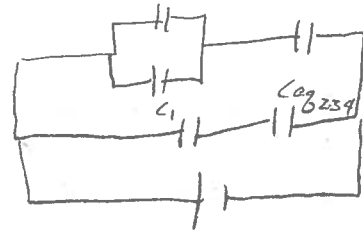
$$C_{eg234} = C_2 + C_3 + C_4 = 12.0 \mu F$$




$$\frac{1}{C_{eg1234}} = \frac{1}{C_1} + \frac{1}{C_{eg234}} = \frac{1}{4.00 \mu F}$$

$$C_{eg1234} = 4.00 \mu F$$




$$C_{eg56} = C_5 + C_6 = 9.00 \mu F$$

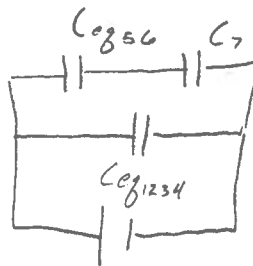

$$\frac{1}{C_{eg567}} = \frac{1}{C_{eg56}} + \frac{1}{C_7} = \frac{4}{9.00 \mu F}$$

$$C_{eg567} = 2.25 \mu F$$

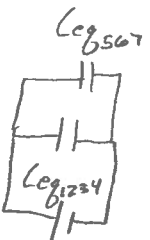

total equivalent capacitance  $C_{eg} = C_{eg567} + C_{eg1234} = 6.25 \mu F$

Ch. -17

17-1

$$I = \frac{\Delta Q}{\Delta t}$$

total charge  $\Delta Q =$  charge of electrons  $\cdot$  number of electrons

let  $n =$  number of electrons,  $e =$  charge of electron

$$I = \frac{en}{\Delta t} \Rightarrow n = \frac{I \Delta t}{e} = \frac{(80 \times 10^{-3} \text{ A})(600 \text{ s})}{1.6 \times 10^{-19} \text{ C}} = 3 \times 10^{20} \text{ electrons}$$

current  $\longrightarrow$   
 $\longleftarrow v_e \sim$  electron velocity

electrons move opposite current direction

17-5.

$\Delta Q = e \cdot 1$  one electron

$\Delta t$  can be found from distance and

velocity

distance traveled  $= 2\pi r$  (electron orbit)

$$2\pi r = vt \Rightarrow \Delta t = \frac{2\pi r}{v} = \frac{2\pi \cdot 5.29 \times 10^{-11} \text{ m}}{2.19 \times 10^6 \text{ m/s}} = 1.52 \times 10^{-16}$$

$$I = \frac{\Delta Q}{\Delta t} = \frac{1.60 \times 10^{-19}}{1.52 \times 10^{-16}} \approx 1.05 \text{ mA}$$






17-15

$$(a) \Delta V = IR$$
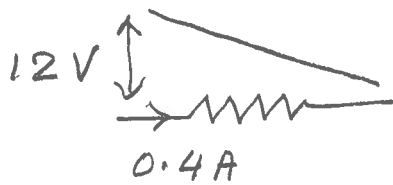
$$R = \frac{\Delta V}{I} = \frac{12V}{0.4A} = 30 \Omega$$



(b)

$$R = \rho \frac{l}{A} \quad \rho \equiv \text{resistivity}$$

$$A = \pi r^2 = \pi (.004m)^2 = 5.02 \times 10^{-6} m^2$$

$$l = 3.2 m$$

$$\rho = \frac{RA}{l} = \frac{30 \Omega \cdot 5.02 \times 10^{-6} m^2}{3.2 m} = 4.7 \times 10^{-4} \Omega m$$

17-19.

We need to know the resistivity of the wire to see how a changing length will effect the resistance

$$\rho = \frac{RA}{l} = \frac{1.0 \Omega \cdot \pi r_0^2}{L_0}$$

now wire is stretched so that  $r = 0.25 r_0$

How did the length change?

we had  $r_0^2 L_0$  cubic meters of material,

the amount of material cannot change during stretching, so  $r^2 L = r_0^2 L_0$

$$\Rightarrow L = \frac{r_0^2}{r^2} L_0$$

$$R = \rho \frac{L}{\pi r^2} = 1.0 \Omega \cdot \frac{\pi r_0^2}{L_0} \cdot \frac{r_0^2}{r^2} \cdot \frac{1}{\pi r^2} = \frac{1.0 \Omega r_0^4}{(.25 r_0)^4} = 256 \Omega$$