

## Solutions-6

### FORMULAE

### Chap 17

$$R = \frac{V}{I}$$

$$R = \frac{\rho l}{A} \quad \rho = \rho_0(1 + \alpha T)$$

$$R = R_0[1 + \alpha T]$$

$$P = I^2 R = \frac{V^2}{R}$$

### Chap 18

#### Kirchhoff Rules


Loop Rule: Potl. at any pt. is unique so

$$\sum_{\text{LOOP}} \Delta V = 0$$

Total change of potential in a loop is zero.

Junction Rule: Current is flux of charge, charge is conserved hence
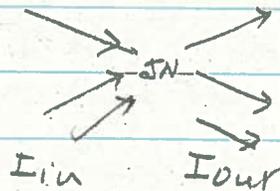
$$\sum I_{\text{out}} = \sum I_{\text{in}}$$



Resistors in series,  $I$  common,  $V$ 's ADD

$$R_s = \sum R_i$$

Resistor in parallel,  $V$  common,  $I$ 's ADD

$$\frac{1}{R_p} = \sum \frac{1}{R_i}$$

Problem 21.

$$T_1 = 58^\circ\text{C}$$

$$T_2 = -88^\circ\text{C}$$

$$\alpha = 3.9 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$$

$$I_1 = 1 \text{ A}$$

$$I_2 = ?$$

$$R = R_0 (1 + \alpha(T - T_0))$$

$$\frac{V}{I_1} = R_1$$

$$\frac{V}{I_2} = R_2$$

$$\therefore \frac{R_1}{R_2} = \frac{I_2}{I_1}$$

$$\therefore I_2 = I_1 \frac{R_0 (1 + \alpha(T_1 - T_0))}{R_0 (1 + \alpha(T_2 - T_0))} = \frac{1 + 3.9 \times 10^{-3} (58 - (-88))}{1 + 3.9 \times 10^{-3} (-88 - (-88))}$$

$$\therefore I_2 = 1.5894 \text{ A}$$

Problem 29.

$$a) R = \frac{\rho l}{A} = \frac{9.4 \times 10^{-7} \times 1}{\pi \times \left(\frac{1 \times 10^{-3}}{2}\right)^2} = \frac{9.4 \times 10^{-7}}{\pi \times 0.25 \times 10^{-6}} \approx 1.2 \Omega$$

$$b) \Delta R = \frac{\rho \Delta l}{A} = \frac{9.4 \times 10^{-7} \times 4 \times 10^{-4}}{\pi \times \left(\frac{1 \times 10^{-3}}{2}\right)^2} = 4.79 \times 10^{-4} \Omega$$

Problem 33.

For a single resistor  $R = \frac{V^2}{P} = \frac{120^2}{100} = 144 \Omega$ .

If  $n$  are connected in parallel, effective resistance  
 $= \frac{R}{n}$ .

And if current  $I$  passes through each,

$$\therefore I = \frac{V}{R} = \frac{120}{144} = 0.83$$

$$\therefore \text{Total current} = nI = n(0.83) < 15.$$

2

$$\therefore n < 17.85$$

$\therefore$  Almost 17 bulbs.

Problem 39.

$$\frac{P}{l} = 2.00 \text{ W/m}$$

$$\text{But } P = I^2 R = I^2 \left( \frac{\rho l}{A} \right) = \frac{I^2 \rho l}{\pi r^2}$$

$$\therefore r = \sqrt{\frac{I^2 \rho}{\pi (P/l)}} = \sqrt{\frac{9 \times 10^4 \times 1.7 \times 10^{-8}}{3.14 \times 2}} = 1.53 \times 10^{-4} \text{ m}$$

Problem 45

$$E_{\text{eff}} = 100 \times 11 = 1100 \text{ kWh}$$

$$E_{\text{con}} = 100 \times 40 = 4000 \text{ kWh}$$

$$\therefore E_{\text{con}} - E_{\text{eff}} = 2900 \text{ kWh}$$

$$\therefore \text{Money Saved} = \$232$$

Problem 52.

$$r = 1.1 \text{ cm} = 0.011 \text{ m} \quad l = 0.04 \text{ m}$$

$$I = 50 \text{ A}$$

$$V = IR = \frac{I \rho l}{A} = \frac{50 \times 1.7 \times 10^{-8} \times 0.04}{\pi \times 0.011^2} = \underline{\underline{8.948 \times 10^{-5} \text{ V}}}$$

Problem 1.


$$I(R+r) = \mathcal{E}$$

$$\therefore 117 \times 10^{-3} (72 + r) = 9.$$

$$\therefore r = \frac{9}{117 \times 10^{-3}} - 72 = 4.92 \Omega.$$

Problem 5

a)

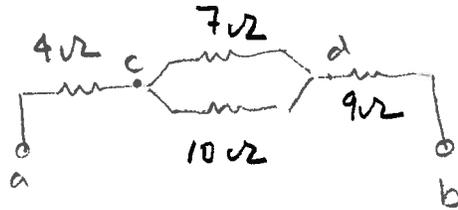

$$R_{\text{tot}} = 4 + \frac{7 \times 10}{7 + 10} + 9$$

$$= 17.12 \Omega$$

$$b) \quad I = \frac{V}{R_{\text{eq}}} = \frac{34}{17.12} = \underline{1.99 \text{ A}}. \quad \text{Current through } 4 \Omega \text{ \& } 9 \Omega.$$

$$\therefore \text{Potential at } c = 34 - 4 \times 1.99 \approx 26 \text{ V}.$$


$$D = 9 \times 1.99 \approx 18 \text{ V}.$$

$$\therefore \text{Current through } 7 \Omega = \frac{18}{7} = \underline{2.57 \text{ A}}.$$

$$10 \Omega = \frac{18}{10} = \underline{1.8 \text{ A}}.$$

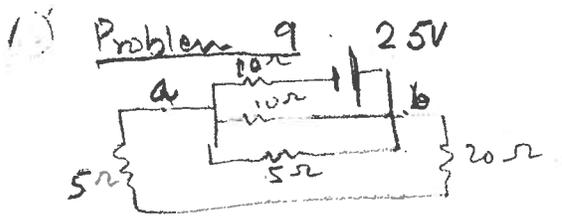Problem 7.

$$R_{\text{eq}} = 2R + \frac{R^2}{2R} = 2R + R = 3R.$$



$$\begin{aligned} \text{a) } R_{eq} &= 20 + 5 + \frac{1}{\frac{1}{10} + \frac{1}{10} + \frac{1}{5}} \\ &= 27.5 \Omega \end{aligned}$$

$$\therefore I = \frac{25}{27.5} = 0.91 \text{ A}$$

$$\text{b) } V_b = 25 \text{ V}$$

$$V_a = 25 - 0.91 \times 25 = 22.5 \text{ V}$$

Problem 13

The upper branch has  $R_{eq1} = 3 + \frac{1}{\frac{1}{6} + \frac{1}{6}}$

lower branch  $R_{eq2} = \frac{1}{\frac{1}{4} + \frac{1}{12}} + 2$

$$= 5 \Omega$$

$$\begin{aligned} \therefore R_{eq} &= 3 + \frac{1}{\frac{1}{6} + \frac{1}{5}} \\ &= 5.72 \Omega \end{aligned}$$

$$\therefore I = 3.14 \text{ A}$$

$$\begin{aligned} \therefore \text{Voltage across network} &= 18 - 3.14 \times 3 \\ &= 8.58 \end{aligned}$$

$$\therefore \text{Current through lower branch} = \frac{8.58}{5} = 1.716 \text{ A}$$


13-CONT'D

∴ Voltage across  $4\Omega, 12\Omega$  branch =  $8.58 - 1.718 \times 2$  5  
 $= 5.14 \text{ V.}$

$$\therefore I = \frac{5.14}{12}$$

$$I = 0.43 \text{ A}$$

Problem 21.

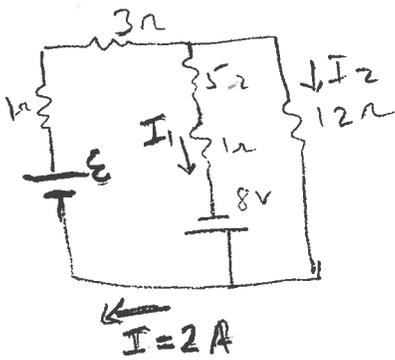

$$8 + \epsilon = (I \cdot 1 + I \cdot 3 + I_1 \cdot 5 + I_1 \cdot 1) \quad \text{--- (1)}$$

$$\epsilon = I \cdot 1 + 3 \cdot I + I_2 \cdot 12 \quad \text{--- (2)}$$

$$I_1 + I_2 = I \quad \text{--- (3)}$$

$$\begin{aligned} \text{(1) - (2), (3)} \Rightarrow 8 &= 6I_1 - 12(I - I_1) \\ &= 6I_1 - 24 + 12I_1 = -24 + 18I_1 \end{aligned}$$

$$\therefore I_1 = \frac{32}{18} = 1.78 \text{ A.}$$

$$\therefore I_2 = 0.22 \text{ A.}$$

$$\therefore \epsilon = 4 \times 2 + 12 \times 0.22$$

$$= 10.64 \text{ V.}$$

(1) Problem 33.

6

$$R = 1 \text{ M} \Omega \quad C = 5 \mu\text{F} \quad \mathcal{E} = 30 \text{ V.}$$

$$q = Q (1 - e^{-t/RC}) \quad ; \quad Q = C\mathcal{E}.$$

$$\therefore Q = 5 \times 30 \times 10^{-6} = 150 \mu\text{C}.$$

$$\therefore q = 150 \times 10^{-6} (1 - e^{-10/5})$$

$$q = 1.29 \times 10^{-4} \text{ C}$$

(11) Problem 40.

$$P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}.$$

$$R_{eq} = \frac{R}{2}.$$

$$\therefore R = \frac{120^2}{1200} = 12 \Omega.$$

$$\therefore I = \frac{120}{12} = 10 \text{ A}.$$

Yes you can operate them together.