

# SOLUTIONS - 10

Devices Battery  $\begin{array}{c} + \\ | \\ | \\ | \\ - \\ \hline \epsilon \end{array}$

Capacitor  $C = \frac{Q}{V}$     II-plate  $C = \frac{\epsilon_0 A}{d}$

Resistor  $R = \frac{V}{I}$      $R = \frac{\rho l}{A} = \frac{l}{\sigma A}$

Ideal Battery and R



close switch

Current flows from

+ to - outside and from - to + inside

battery - outside electrons flow


inside ions flow

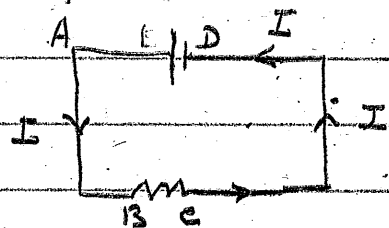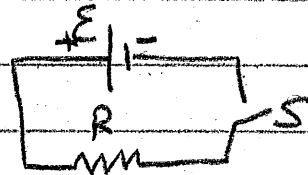

Potential varies as



$$I = \frac{\epsilon}{R}$$

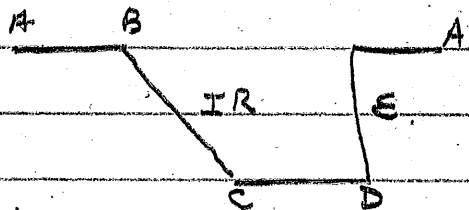Power loss in R  $P = \frac{\epsilon^2}{R}$



Real Battery has 'resistance inside'

Potential

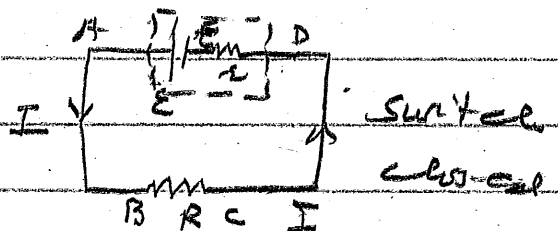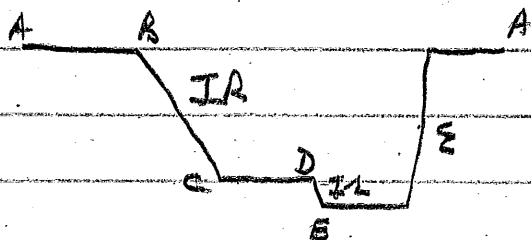

$$I = \frac{\epsilon}{(R+r)}$$


Power in R  $P = \left(\frac{\epsilon}{R+r}\right)^2 R$ .

Vary R  
Maximum

Power when

$$R = r$$


Battery resistance

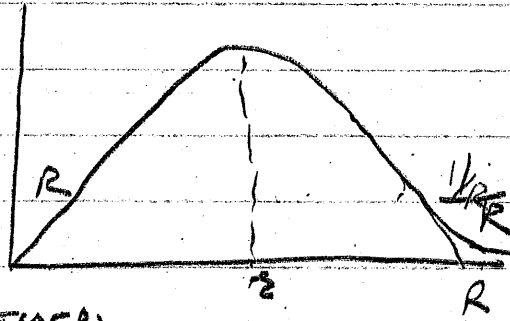

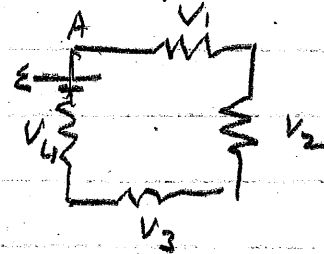
### Kirchhoff's laws

Loop Rule: Since potential at a point is unique, total change of potential around any closed loop must be zero

$$V_A - V_1 - V_2 - V_3 + \epsilon = V_A$$



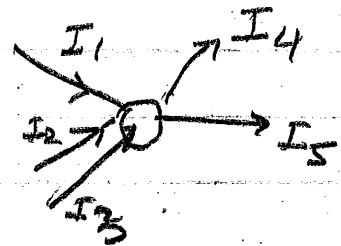
JUNCTION RULE: Current measures flux of charge, charge is conserved so at a junction total outgoing current must be equal to total incoming current



$$I_4 + I_5 = I_1 + I_2 + I_3$$

More than one capacitor


Series circuit

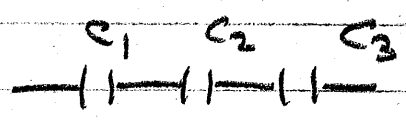

$\frac{1}{C_s} = \sum \frac{1}{C_i}$  charge is common  
V's add

Parallel circuit


$C_p = \sum C_i$   
V's common  
Q's add

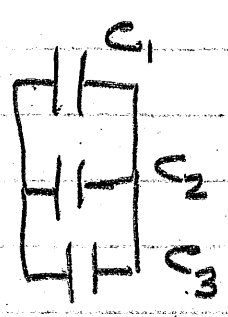

More than one resistor

Series


current is common  
V's add

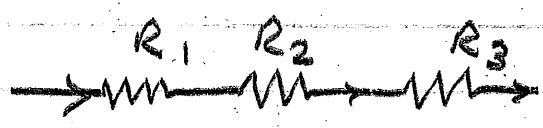

$R_s = \sum R_i$

Parallel

$I = I_1 + I_2 + I_3$

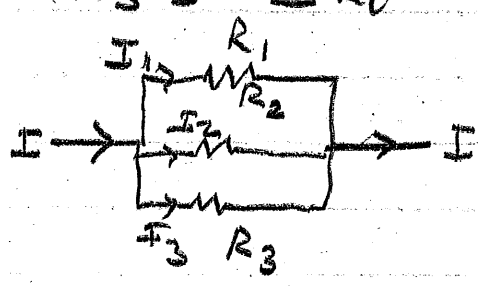

Potential drop


is common, currents add

$\frac{1}{R_p} = \sum \frac{1}{R_i}$

Charging / Discharging a Capacitor

At  $t=0$ , connect 1 to 2

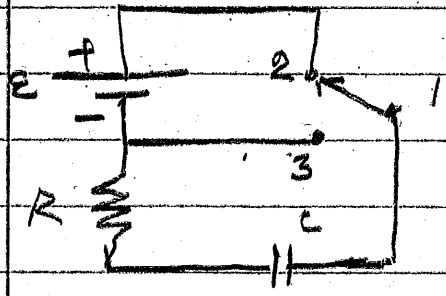the battery will start moving charges through the wires so charges will begin to accumulate on the plates of C and



current will flow through R. NO CURRENT FLOWS THROUGH C AT ANY TIME.

At  $t=0$


$$E - I_0 R = 0 \quad I_0 = \frac{E}{R}$$

a short time later capacitor has charge on it

$$E = iR + \frac{q}{C} \quad i = \frac{1}{R} \left( E - \frac{q}{C} \right)$$

$i$  is less than  $I_0$ .

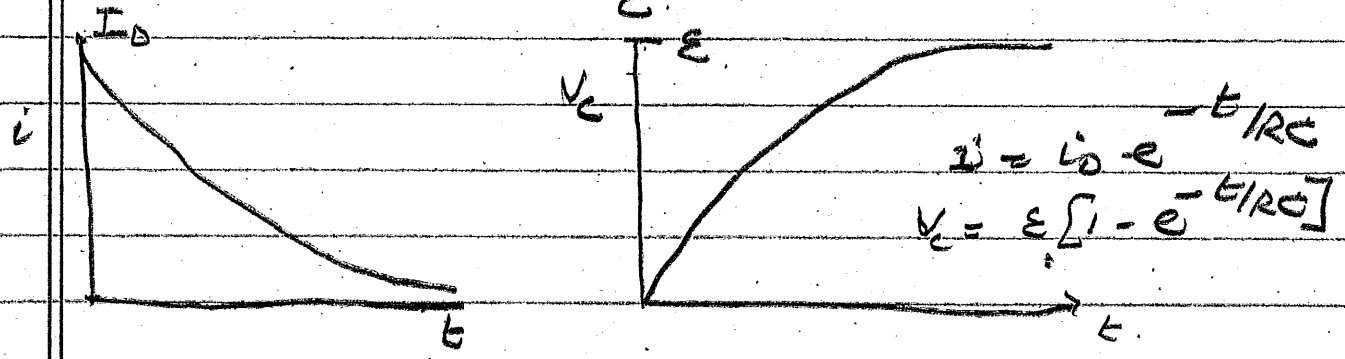A long time later capacitor is fully charge  $E = \frac{Q}{C}$ ,  $i = 0$ .




If later you connect 1 to 3, capacitor discharges through R.
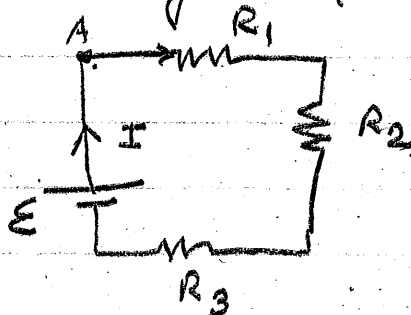
## S-25 Kirchhoff's "Laws"

Loop Rule Since we are dealing with conservative forces potential at any point is unique, hence total change of potential around any closed loop must be zero.


$$V_A - IR_1 - IR_2 - IR_3 + \mathcal{E} = V_A$$



Note:  $V$  drops if you go along  $I$ ; rises if you go against  $I$ .
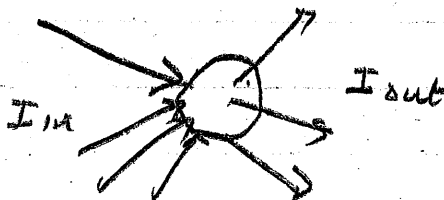
## JUNCTION RULE

Current measures flux of charge and charge is conserved so at a junction the total outgoing current must equal the total incoming current.



$$\sum I_{out} = \sum I_{in}$$

S-26 RC

$$R = \frac{V}{I}, \quad C = \frac{Q}{V}$$

$$\text{So } RC = \frac{V}{I} \cdot \frac{Q}{V} = \frac{Q}{IT} \rightarrow T^1$$

So RC has dimensions of time

S-27  $T$  is controlled by both

$R$  and  $C$ : Charging a capacitor requires transfer of charge from the battery to the capacitor plates.

The current must pass through  $R$  so

$R$  controls the rate of transfer. The

quantity of charge needed to complete


the process is controlled by  $C$ .

Hence  $R$  and  $C$  both appear in

the time constant.

23.5

Find the current

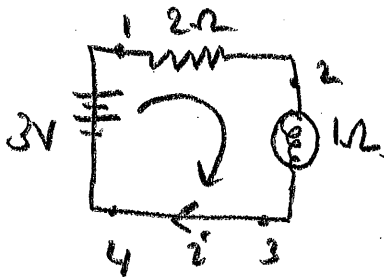

$$(a) 3V - 2\Omega i - 1\Omega i = 0$$

$$\Rightarrow \underline{i = 1A}$$

$$\Delta V_{12} = V_2 - V_1 = -i(2\Omega) = -(1A)(2\Omega) = -2V$$


$$\Delta V_{23} = V_3 - V_2 = -i(1\Omega) = -(1A)(1\Omega) = -1V$$

$$\Delta V_{34} = V_4 - V_3 = 0V$$

(b)  $\Delta V_{12} = V_2 - V_1 = 0V$  (no current flows)

$$\Delta V_{23} = V_3 - V_2 = -3V$$

$$\Delta V_{34} = V_4 - V_3 = 0V$$

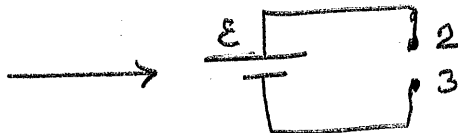

23.12 Resistivities are in Table 22.1 [p. 732]

$$R_{\text{copper}} = \frac{(1.7 \times 10^{-8} \Omega \cdot \text{m})(0.2 \text{ m})}{\pi(0.5 \times 10^{-3} \text{ m})^2}$$



b/c  $R = \frac{\rho \cdot l}{A}$

$$R_{\text{iron}} = \frac{(9.7 \times 10^{-8} \Omega \cdot \text{m})(0.6 \text{ m})}{\pi(0.5 \times 10^{-3} \text{ m})^2}$$

Since two wires are in series  $R_{\text{total}} = R_{\text{copper}} + R_{\text{iron}}$


$$R_{\text{total}} = 4.33 \times 10^{-3} \Omega + 74.1 \times 10^{-3} \Omega = 78.4 \times 10^{-3} \Omega = 78 \text{ m}\Omega$$

23.17

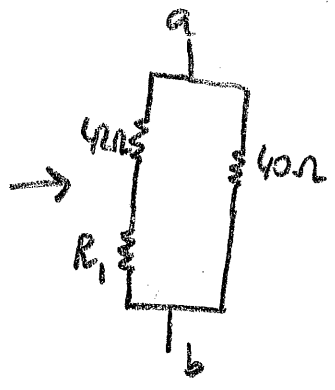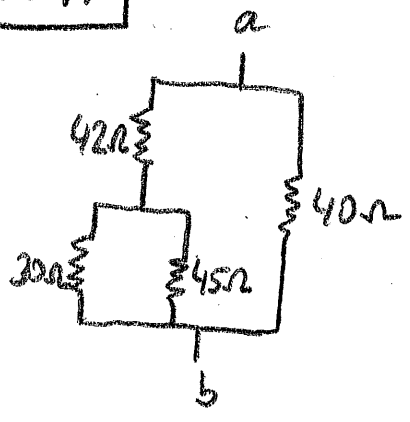


$$R_1 = \left( \frac{1}{30\Omega} + \frac{1}{45\Omega} \right)^{-1} \text{ (parallel)}$$

$$= 18\Omega$$

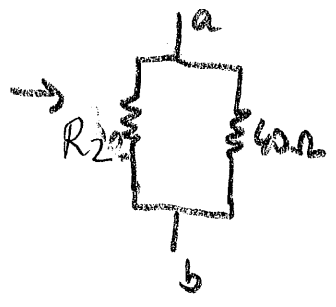

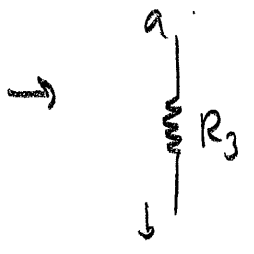
$$R_2 = 42\Omega + 18\Omega = 60\Omega \text{ (series)}$$



$$R_3 = \left( \frac{1}{60\Omega} + \frac{1}{40\Omega} \right)^{-1} = 24\Omega \text{ equivalent resistance.}$$



23.22

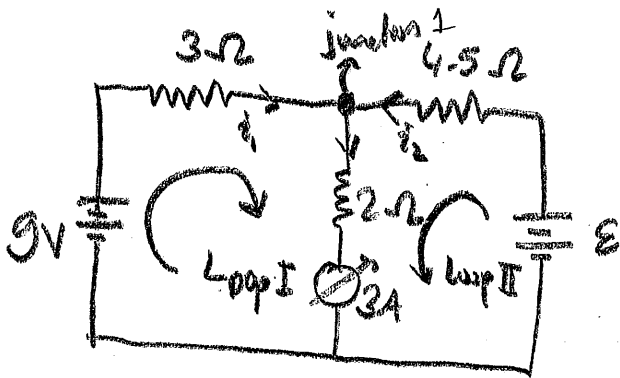

Loop I:  $9V - i_1 \cdot 3\Omega - 2\Omega \cdot 3A = 0$  (1)

Loop II:  $\varepsilon - 4.5\Omega i_2 - 2\Omega \cdot 3A = 0$  (2)

and junction 1:  $i_1 + i_2 = 3A$  (3)

3 unknowns  $\varepsilon, i_1, i_2$ , 3 equations (1), (2) and (3)

plug (3) in (1)

$9V - (3A - i_2) \cdot 3\Omega - 6V = 0$

$3V - 9V + 3\Omega i_2 = 0$

$3\Omega i_2 = 6V \Rightarrow i_2 = \frac{6V}{3\Omega} = 2A$

find  $\varepsilon$  using (1) and (3)

$\varepsilon - (4.5\Omega)(2A) - (2\Omega)(3A) = 0$


$\varepsilon - 9V - 6V = 0 \Rightarrow \varepsilon = 15V$

find  $i_1$  via (3)

$i_1 + i_2 = 3A$

$i_1 = 3A - i_2 = 3A - 2A = 1A$

23.34

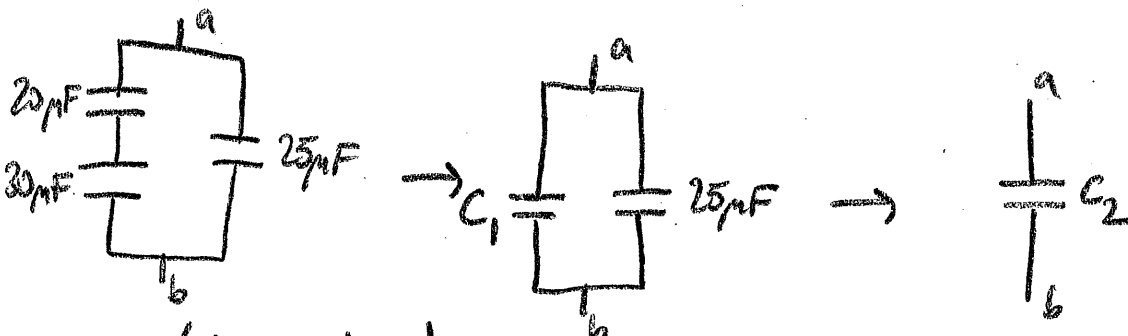

$C_1 = \left( \frac{1}{25\mu F} + \frac{1}{30\mu F} \right)^{-1} = 12\mu F$   
(series)

$C_2 = C_1 + 25\mu F = 12\mu F + 25\mu F = 37\mu F$  (parallel)