


SOLUTIONS - II

Devices: Battery $\begin{matrix} + \\ | \\ - \end{matrix} \quad \mathcal{E}$


Capacitor $C = \frac{Q}{V}$, II-plate $C_0 = \frac{\epsilon_0 A}{d}$, $U_E = \frac{Q^2}{2C_0}$

$$U_E = \frac{1}{2} \epsilon_0 E^2$$

Many Capacitors

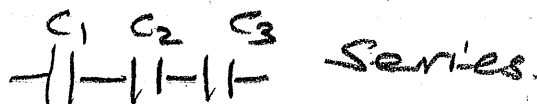


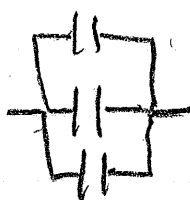Q - Common $\frac{1}{C_s} = \sum \frac{1}{C_i}$
 U 's add




V Common, Q 's add
 $C_p = \sum C_i$

Resistor

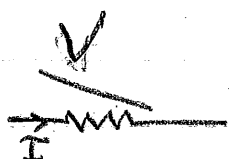


$R = \frac{V}{I}$, $R = \frac{l}{\sigma A}$, $I = \sigma A E$ $J = \sigma E$

Many Resistors

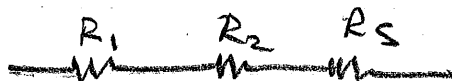


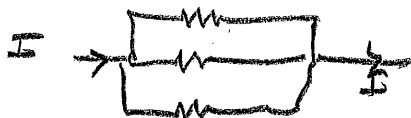Series
 I common
 V 's add.
 $R_s = \sum R_i$



V - common
 I 's add.
 $\frac{1}{R_p} = \sum \frac{1}{R_i}$

Capacitor - Resistor - Battery.

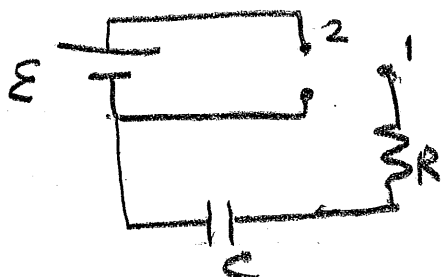

$t = 0$ 1 \rightarrow 2 Charging
 $i = \frac{\mathcal{E}}{R} e^{-t/RC}$, $V_C = \mathcal{E} [1 - e^{-t/RC}]$

$t \rightarrow 0$ 1 - 3 Discharging
 $i = \frac{\mathcal{E}}{R} e^{-t/RC}$ $V_C = \mathcal{E} e^{-t/RC}$

Note NO CURRENT EVER FLOWS BETWEEN CAPACITOR PLATES

$$q = EC[1 - e^{-t/RC}] \quad \tau = RC.$$

POWER LOSS IN RESISTOR

$$P = I^2 R = \frac{V^2}{R}$$

FORCE ON MOVING CHARGE due to \vec{B} .

$$\vec{F}_B = q[\vec{v} \times \vec{B}]$$

Charge moves in a PLANE perpendicular to \vec{B} . Motion is circular


$$\vec{v} = v\hat{x} \text{ at } t=0 \text{ when}$$

$$\vec{B} = -B\hat{z} \text{ turned on}$$

$$\vec{F}_B = -qvB\hat{z}$$

provides

$$\vec{F}_c = -\frac{Mv^2}{R}\hat{z}$$

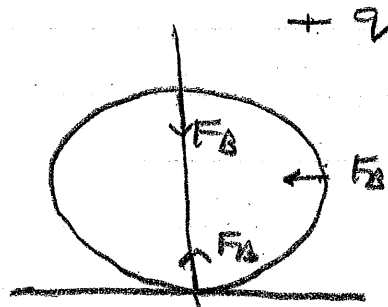

$$\text{So } R = \frac{Mv}{qB}, \text{ angular velocity } \frac{v}{R} = \frac{qB}{M} = \omega$$

Direction of \vec{v} is parallel or antiparallel to \vec{B} .


Ampere's law

$$\sum \vec{B} \cdot d\vec{A} = \mu_0 \sum I_i$$

chap 23

37. Want to charge capacitor
to 87% of \mathcal{E}
in 8 sec.

$$V_c = \mathcal{E} [1 - e^{-t/RC}]$$

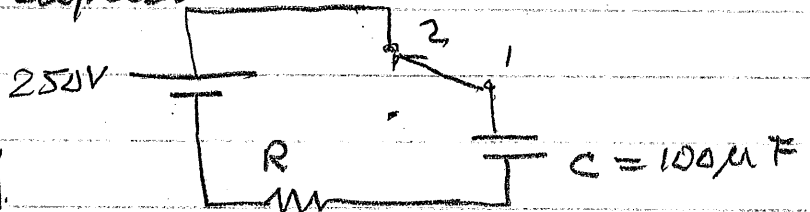

$$0.87 \mathcal{E} = \mathcal{E} [1 - e^{-t/RC}]$$

$$\mathcal{E} e^{-t/RC} = 0.13 \mathcal{E}$$

$$\ln e^{-t/RC} = \ln 0.13 = -2.04$$

$$\frac{t}{RC} = 2.04$$

$$R = \frac{2.04}{2.04} = \frac{8}{2.04 \times 10^{-4}}$$

$$= 4 \times 10^4 \Omega$$

39. Discharge

$$V_c = \mathcal{E} e^{-t/RC}$$

$$q = \mathcal{E} C e^{-t/RC} = Q e^{-t/RC}$$

$$C = 10^{-5} \text{ F}$$

$$R = 10^3 \Omega$$

$$Q = 20 \mu\text{C}$$

$$q = 10 \mu\text{C}$$

$$10 = 20 e^{-t/RC}$$

$$0.5 = e^{-t/RC}$$

$$-0.69 = -t/RC$$


$$t = 0.69 \times R \times C$$

$$= 0.69 \times 10^3 \times 10^{-5} = \underline{6.9 \text{ ms}}$$

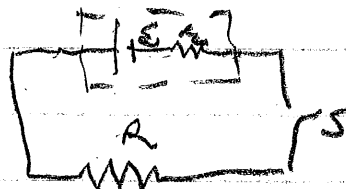48. $\mathcal{E} = 1.5 \text{ V}$

$$r = 1 \Omega$$

else
switch $I = \frac{\mathcal{E}}{R+r}$, $P = \left(\frac{\mathcal{E}}{R+r}\right)^2 R$



48
Contd.

$R = 0.25 \Omega$	$P = \left(\frac{1.5}{1.25}\right)^2 0.25 = 0.36 \text{ W}$
$R = 0.5 \Omega$	$P = \left(\frac{1.5}{1.5}\right)^2 0.5 = 0.5 \text{ W}$
$R = 1.0 \Omega$	$P = \left(\frac{1.5}{2}\right)^2 1 = 0.56 \text{ W}$
$R = 2.0 \Omega$	$P = \left(\frac{1.5}{3}\right)^2 2 = 0.5 \text{ W}$
$R = 4.0 \Omega$	$P = \left(\frac{1.5}{5}\right)^2 4 = 0.36 \text{ W}$

65 Discharging
 $RC = 10 \text{ ms}$

$$q = Q e^{-t/RC}$$

$$u_E = \frac{q^2}{2C} = \frac{Q^2}{2C} e^{-\frac{2t}{RC}}$$

To get $q = \frac{Q}{2}$ $e^{-t/RC} = 0.5$ $\frac{t}{RC} = 0.69$


$t = 6.9 \text{ ms}$

$$q^2 = \frac{Q^2}{2} e^{-2t/RC} = 0.5$$


$$\frac{2t}{RC} = 0.69$$

$t = 3.45 \text{ ms}$

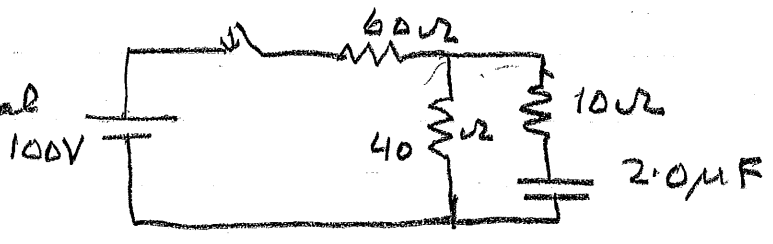70 a When the switch was closed potential across R_1 is $C = 2.0 \mu\text{F}$ is 40 V



7 ND
Current
inside C

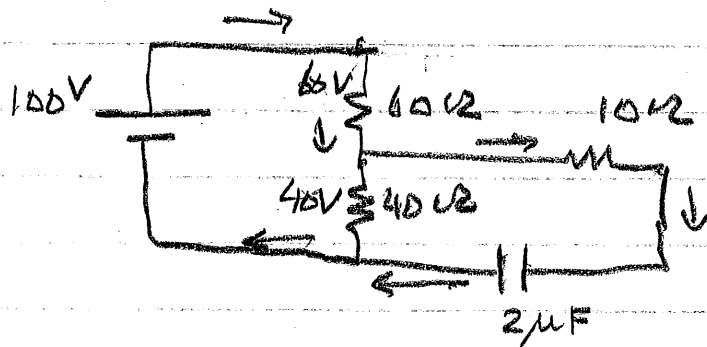

$$\text{So } Q(2) = 40 \times 2 \times \mu\text{F} = 80 \mu\text{C}.$$

b) When switch opens capacitor discharges through $40\Omega + 10\Omega = 50\Omega$
 $R = 50\Omega$
 $C = 2 \times 10^{-6} \text{F}$

$$q = Q e^{-t/RC}$$

$$0.1 = e^{-t/RC}$$

$$-2.3 = -t/RC$$

$$t = 2.3RC = 2.3 \times 50 \times 2 \times 10^{-6} \text{sec}$$

$$= 230 \mu\text{sec}.$$


5-28 In an \vec{E} field a stationary charge experiences a force. In a \vec{B} field a moving charge experiences a force perpendicular to its velocity at all times.

$$\vec{F}_E = q \vec{E} \quad \vec{F}_B = q [\vec{v} \times \vec{B}]$$

S-29 (i) Since the force $\vec{F}_B = q[\vec{v} \times \vec{B}]$, it is always perpendicular to the displacement and therefore does NO work.

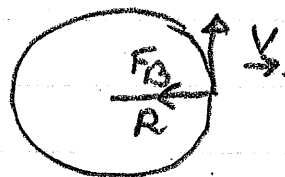(ii) The force $\vec{F}_B = -qvB\hat{z}$ provides the centripetal force $\vec{F}_c = -\frac{Mv^2}{R}\hat{z}$.

hence $\frac{Mv^2}{R} = qvB$
 angular velocity $\omega = \frac{v}{R} = \frac{qB}{M}$



is independent of v .



S-30 Take Δl || y-axis

at pt A $\vec{r} = r\hat{x}$
 $\Delta l \times \vec{r}$ is along $-\hat{z}$

at pt B $\vec{r} = -r\hat{z}$
 $\Delta l \times \vec{r}$ is along $-\hat{x}$

at pt C $\vec{r} = -r\hat{x}$
 $\Delta l \times \vec{r}$ is along $+\hat{z}$

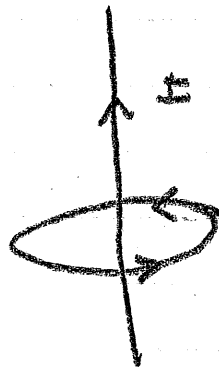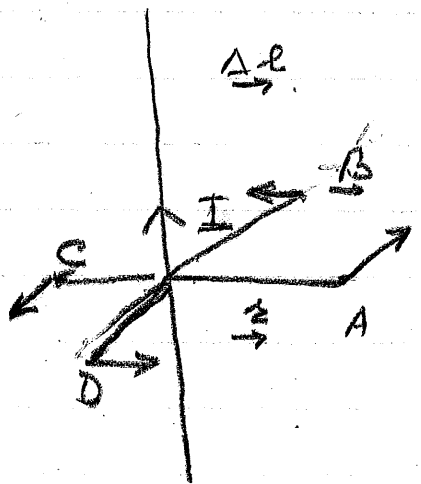at pt D $\vec{r} = +r\hat{z}$
 $\Delta l \times \vec{r}$ is along $+\hat{x}$



\vec{r} vector \vec{B} circulates around I .

S-31 we have cylindrical

symmetry about the
y-axis. Hence \vec{B} can
be function of r only
& must circulate
around I .

Let us choose for
a closed loop a circle
of radius r centered
at I . Magnitude of
 B is same on all
points of circle. \vec{B} is
tangent to circle so

$$\sum_c \vec{B} \cdot d\vec{l} = (B \cdot 2\pi r)$$

By ampere's law

$$\sum_c \vec{B} \cdot d\vec{l} = \mu_0 \sum I_i = \mu_0 I \quad (I \text{ is the only current})$$

So

$$B \cdot 2\pi r = \mu_0 I$$

$$B = \frac{\mu_0 I}{2\pi r} \hat{\phi}$$

a azimuthal angle.

