

Answers Week 10

10-1 Mechanical System: (i) Pull mass to A, store potential energy $\frac{1}{2}kA^2$. (ii) Release mass, it will reduce its potential energy until $x = 0$, when all the energy is kinetic. (iii) It will use its kinetic energy to go to $x = -A$ where Energy is again all potential. Hence oscillation occurs with $x = A \cos \omega t$, $\omega = \sqrt{\frac{k}{M}}$

Electrical System: (i) Charge capacitor, store energy $\frac{Q^2}{2C}$ in \underline{E} -field. (ii) Open S_1 , close S_2 . Capacitor sets up current in L, \underline{E} -field in C collapses all the energy is in the \underline{B} field in L. (iii) Current through L recharges C until $\underline{B} \rightarrow 0$. Hence, charge oscillation occurs

$$q = Q \cos \omega t, \quad \omega = \frac{1}{\sqrt{LC}}$$

10-3 (i) If current increases by a factor of 2, X is a capacitor because $i_c = \varepsilon_m W C \cos \omega t$

(ii) If current reduces by a factor of 2, X is an inductor because $i_c = -\frac{\varepsilon_m}{W L} \cos \omega t$.

10-5 (155 - 163) V

10-7 $C = 5.31 \times 10^{-8}$ F

10-9 Power $P_w(t) = i(t) \varepsilon(t)$

$$= i_m \varepsilon_m [\sin^2 \omega t \cos \phi + \sin \omega t \cos \omega t \sin \phi]$$

$$\langle (P_w) \rangle = \frac{i_m \varepsilon_m}{2} \cos \phi = \frac{\varepsilon_m^2}{2Z} \cos \phi = \frac{\varepsilon_m^2}{2R} \cos^2 \phi$$

$$\text{Because } \cos \phi = \frac{R}{Z}$$

10-11 Conduction Current: FLUX OF CHARGE IN A CONDUCTOR $I_C = n_e e A V_D$.
Displacement Current: RATE OF CHANGE OF FLUX OF E as a function of

time $i_D = \varepsilon_o \frac{\Delta \phi_E}{\Delta t}$.