

EXERCISES-8

FORMULAE :

CURRENT

$$I = \lim_{\Delta t \rightarrow 0} \left(\frac{\Delta Q}{\Delta t} \right)$$

$$I = n_e e A v_d$$

$$n_e = \frac{6.02 \times 10^{23}}{\text{molar mass}} \times \text{density}$$

$$I = \underline{J \cdot A}$$



$$R = \frac{V}{I}$$

$$R = \frac{\rho l}{A}$$

$$R_s = \sum R_i$$


$$P_w = I^2 R = \frac{V^2}{R}$$

$$\frac{1}{R_p} = \sum \frac{1}{R_i}$$

1 → 2
charging

$$i = \frac{\epsilon}{R} e^{-t/RC}$$

$$V_c = \epsilon [1 - e^{-t/RC}]$$

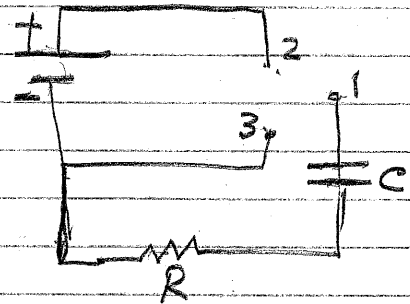

1 → 3
Discharging

$$i = -\frac{\epsilon}{R} e^{-t/RC}$$

$$V_c = \epsilon e^{-t/RC}$$

NO CURRENT
INSIDE C AT
ANY TIME!

KIRCHHOFF'S RULES

JUNCTION RULE

$$\sum I_{out} = \sum I_{in}$$


LOOP RULE

$$\sum_{Loop} \Delta V = 0$$


EE-1 You are given a length of wire whose resistance 100Ω . Given a source of EMF = $45V$ will you get more power from it if you use the wire as is or split it in two halves and connect them across the source in parallel?

Single wire
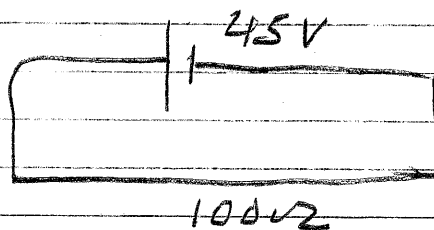
$$P_W = \frac{V^2}{R} = \frac{45^2}{100} \text{ Watts} \\ = 20.25 \text{ W}$$


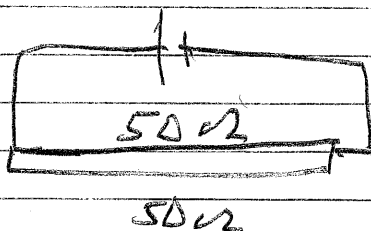
$$\frac{1}{R_p} = \sum \frac{1}{R_i} \\ = \left(\frac{1}{50} + \frac{1}{50} \right) \Omega^{-1} \\ R_p = 25\Omega$$




$$P_W = \frac{V^2}{R} = \frac{45^2}{25} = 81 \text{ W}$$

↑
FOUR TIMES MORE

EE-2 Two light bulbs one of resistance R_1 and the other of resistance $R_2 < R_1$ are connected either (i) in series or (ii) parallel, which bulb is brighter in either case?

Brightness depends on power absorbed in bulb.

(i) Series

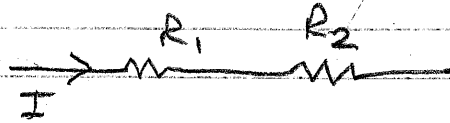


Both bulbs have same current so

$$I^2 R_1 > I^2 R_2$$

↓
Brighter

(ii) In parallel

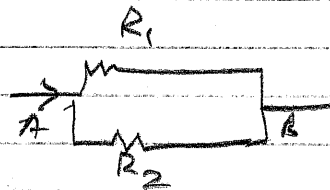

$$I_1 R_1 = I_2 R_2 = V$$

$$P_W = \frac{V^2}{R^2} = \frac{I^2 R^2}{R^2}$$

So

$$\frac{V}{R_2^2} > \frac{V}{R_1^2}$$

↓
Brighter

E8-3 The circuit of

a flashing lamp is


shown. $\mathcal{E} = 95\text{V}$,

$C = 0.15\mu\text{F}$. You want the

lamp to flash every 0.5 sec and it needs

72V to flash. What value of R would you

use?

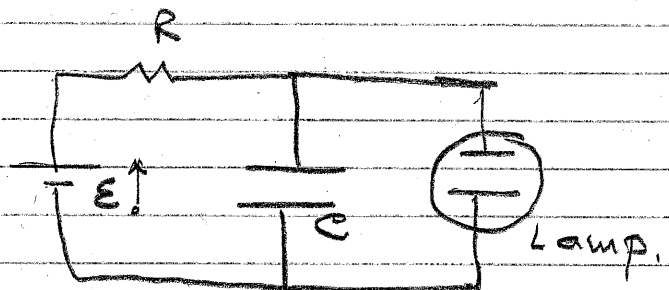

Once the lamp flashes, C is discharged

Immediately, to cause the next flash

C must charge up to 72V so

$$72V = 95V [1 - e^{-t/RC}]$$

where

$$t = 0.55 \text{ sec}$$

$$C = 0.15 \mu\text{F}$$

$$72 = 95 \left[1 - e^{-\frac{0.5}{RC}} \right]$$

$$23 = 95 e^{-\frac{0.5}{RC}}$$

$$\frac{23}{95} = e^{-\frac{0.5}{RC}}$$

$$\ln\left(\frac{23}{95}\right) = -\frac{0.5}{RC}$$

$$-1.418 = -\frac{0.5}{RC}$$

$$R = \frac{0.5}{1.418 \times 0.15 \times 10^{-6}} \Omega$$
$$= 2.35 \times 10^6 \Omega$$

E8-4 Arguably, the resistance of a cell wall

is $0.5 \times 10^9 \Omega$. Considering that the potential

difference can be 0.75 mV how many sodium

ions cross the wall per sec. Na^+ has a charge

of $1.6 \times 10^{-19} \text{ C}$.


$$I = \frac{V}{R} = \frac{0.75 \times 10^{-3}}{0.5 \times 10^9} = 1.5 \times 10^{-12} \text{ amp}$$

$$\# \text{ of ions} = \frac{1.5 \times 10^{-12} \text{ C/s}}{1.6 \times 10^{-19}} \approx 10^7 \text{ ions/sec.}$$

E8-5 Consider the circuit, $C = 60 \mu\text{F}$

$R = 2 \times 10^5 \Omega$. The

initial stored
energy in

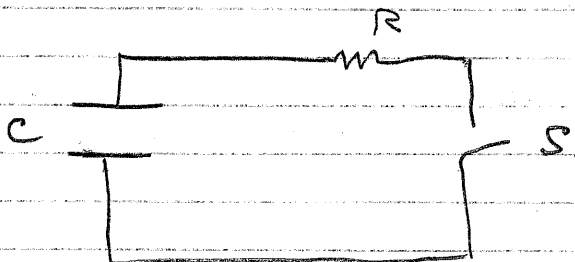

C is 60 mJ when S is closed at $t=0$. At
what time will the stored energy
be 32 mJ ?

The energy stored is

$$U_E = \frac{1}{2} C V_C^2$$

and V_C varies as

$$V_C = V_C(0) e^{-t/RC}$$

We need

$$\frac{V_C(t)}{V_C(0)} = \sqrt{\frac{32}{60}} = 0.73$$

and

$$0.73 = e^{-t/RC}$$

so

$$-0.31 = -t/RC$$

$$t = 0.31 \times 6 \times 10^{-5} \times 2 \times 10^5$$

$$= 3.77 \text{ secs.}$$