

Outline

- Circuits
- Nernst Potential

Office hours Thursday after spring break 4-5.30

Units

- Current (I) **Ampere** = Coulomb/sec
- Voltage (V) **Volt** = Joule/Coulomb
- E-Field (E) Newton/Coulomb = Volt/meter
- Resistance (R) **Ohm** = Volt/Ampere
- Capacitance (C) **Farad** = Volt/Coulomb
- Power (P) **Watt** = Joule/sec

Resistivity and Conductance


- The resistance factor in Ohm's Law separates into a geometrical part (L/A) times a part independent of the size and shape but dependent on the material. This coefficient is called the *resistivity* of the material (ρ).
- Its reciprocal (g) is called *conductivity*. (*The reciprocal of the resistance is called the conductance (G).*)

$$R = \rho \frac{L}{A} = \frac{1}{g} \frac{L}{A} = \frac{1}{G}$$

Analogy: Water flow

- Water flow is a useful analogy to electric currents because water
 - can divide
 - is conserved and cannot be compressed.

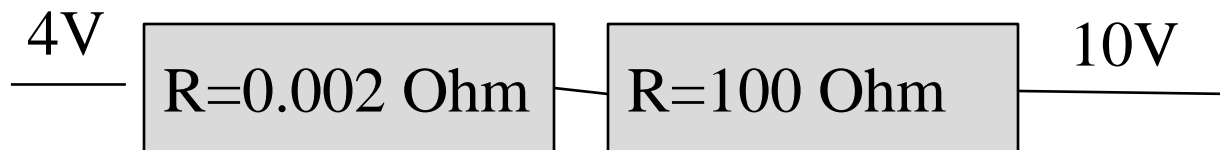Sketch a water analogue for the following circuit



Very useful heuristic

- Wires have very small resistance (e.g. 1 foot of 13 gauge wire has a resistance of 0.002 Ohm)
This R is generally negligibly small compared to other resistances in the circuit through which current flows, so we can approximate it as zero resistance.
- **The Constant Potential Corollary (CPC)**
 - Along any part of a circuit with 0 resistance, then $\Delta V = 0$, i.e., the voltage is constant

Foothold ideas: Kirchhoff's principles




1. **Flow rule:** The total amount of current flowing into any volume in an electrical network equals the amount flowing out.
2. **Ohm's law:** in a resistor, $DV = IR$
3. **Loop rule:** Following around any loop in an electrical network the potential has to come back to the same value (sum of drops = sum of rises).



In the two cases shown here a battery is connected up to a box containing some identical bulbs. The battery maintains a constant potential difference \mathcal{V}_0 across its terminals.

Which bulbs will be brighter?

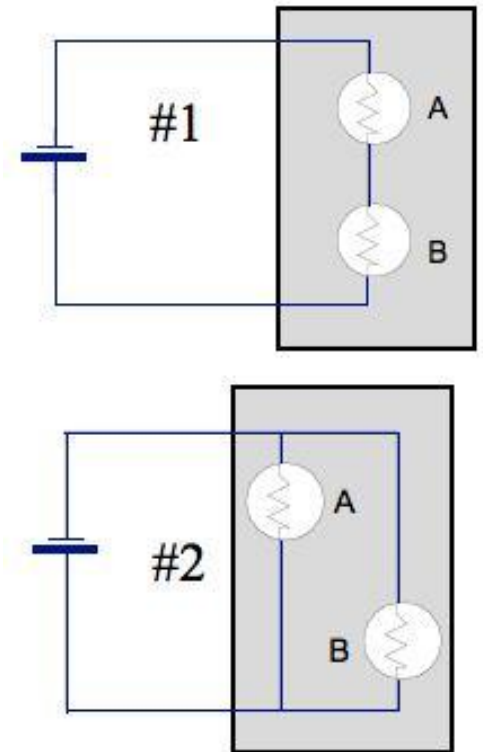
1. A in #1
2. B in #1
3. A and B in #1 (equal)
4. A in #2
5. B in #2
6. A and B in #2 (equal)
7. All 4 equal
8. Other





This circuit has two identical light bulbs burning with equal brightness and a single 12 V battery. When the switch is closed, the brightness of bulb A

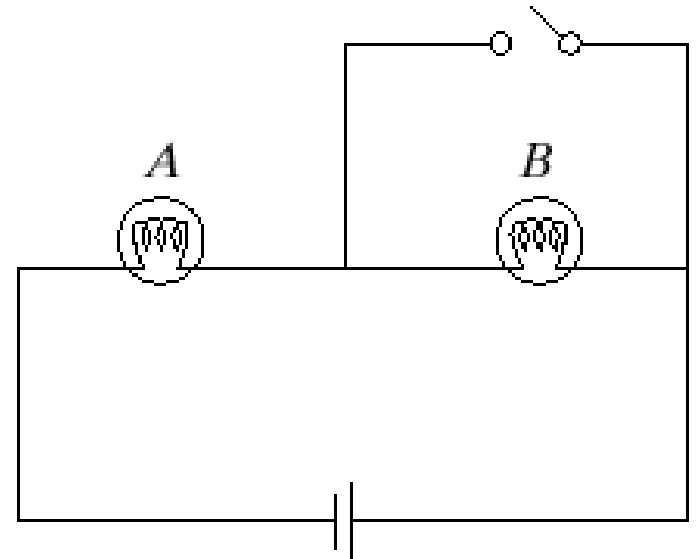
1. increases
2. decreases
3. decreases to 0
4. remains the same





This circuit has two identical light bulbs burning with equal brightness and a single 12 V battery. When the switch is closed, the brightness of bulb B

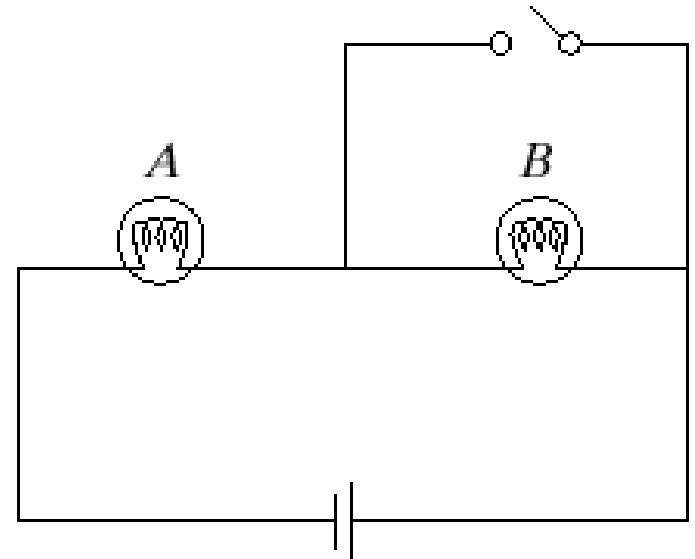1. increases
2. decreases
3. decreases to 0
4. remains the same



Electric Power

- The rate at which electric energy is depleted from a battery or dissipated (into heat or light) in a resistor is

$$Power = IDV$$



This circuit has two identical light bulbs burning with equal brightness and a single 12 V battery. When the switch is closed, the **power dissipated by the elements in the circuit**

1. increases
2. decreases
3. decreases to 0
4. remains the same

