



■ **Theme Music: Benny Goodman**
AC/DC Current

■ **Cartoon: Bob Thaves**
Frank & Ernest



Electric circuit elements

- Batteries — devices that maintain a constant electrical pressure difference across their terminals (like a water pump that raises water to a certain height).
- Resistances — devices that have significant drag and oppose current. Pressure will drop across them.
- Capacitors — devices that can maintain a separation of charge if there is a potential difference maintained across the,
- Wires — have very little resistance. We can ignore the drag in them (mostly — as long as there are other resistances present).

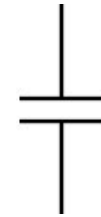 

Foothold ideas: Kirchhoff's principles



1. ***Flow rule***: The total amount of current flowing into any volume in an electrical network equals the amount flowing out.
2. ***Ohm's law***: in a resistor, $\Delta V = IR$
3. ***Loop rule***: Following around any loop in an electrical network the potential has to come back to the same value (sum of drops = sum of rises).

Very useful heuristic

- The Constant Potential Corollary (CPC)
 - Along any part of a circuit with 0 resistance, then $\Delta V = 0$, i.e., the voltage is constant since in any circuit element

$$\Delta V = IR$$

$$R = 0 \Rightarrow \Delta V = 0$$

(even if $I \neq 0$)

Electric Power

- The rate at which electric energy is depleted from a battery or dissipated (into heat or light) in a resistor is

$$Power = I\Delta V$$


Units

- Current (I) **Ampere** = Coulomb/sec
- Voltage (V) **Volt** = Joule/Coulomb
- E-Field (E) **Newton/Coulomb** = Volt/meter
- Resistance (R) **Ohm** = Volt/Ampere
- Capacitance (C) **Farad** = Volt/Coulomb
- Power (P) **Watt** = Joule/sec

Series and parallel

■ Series

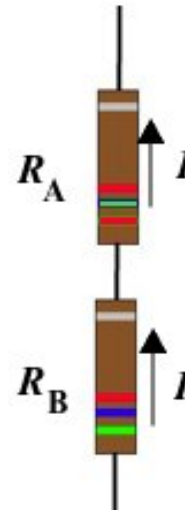- Same current flows through both devices




$$I = \frac{\Delta V_A}{R_A} = \frac{\Delta V_B}{R_B}$$

$$\frac{\Delta V_A}{\Delta V_B} = \frac{R_A}{R_B}$$

$$\begin{aligned}\Delta V &= \Delta V_A + \Delta V_B \\ &= I(R_A + R_B)\end{aligned}$$

■ Parallel

- Same voltage drop across both devices

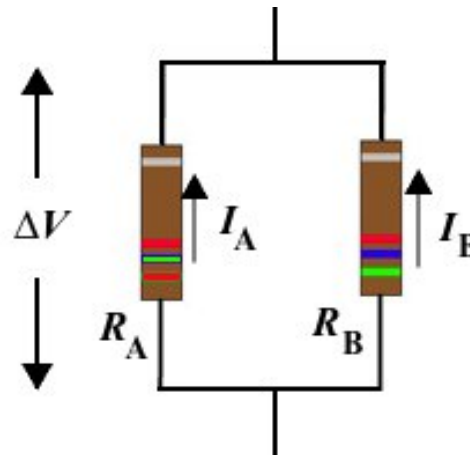

$$\Delta V = I_A R_A = I_B R_B$$

$$\frac{I_A}{I_B} = \frac{R_B}{R_A}$$

$$I = I_A + I_B$$

$$= \Delta V \left(\frac{1}{R_A} + \frac{1}{R_B} \right)$$