

March 15, 2013

Physics 132

Prof. E. F. Redish

■ **Theme Music: Benny Goodman**
AC/DC Current

■ **Cartoon: Bob Thaves**
Frank & Ernest




© Thaves/Dist. by NEA, Inc.
3/15/13

Physics 132

1

Electric circuit elements

- **Batteries** — devices that maintain a constant electrical pressure difference across their terminals (like a water pump that raises water to a certain height).
- **Resistances** — devices that have significant drag and oppose current. Pressure will drop across them.
- **Capacitors** — devices that can maintain a separation of charge if there is a potential difference maintained across the,
- **Wires** — have very little resistance. We can ignore the drag in them (mostly — as long as there are other resistances present).

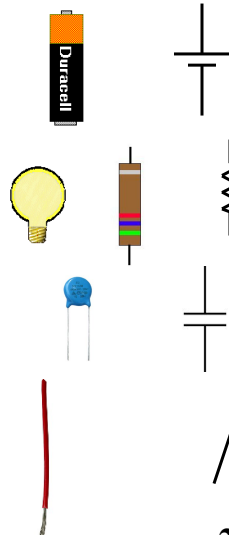

3/15/13

Physics 132

2

Foothold ideas: Kirchhoff's principles



1. **Flow rule:** The total amount of current flowing into any volume in an electrical network equals the amount flowing out.
2. **Ohm's law:** in a resistor, $\Delta V = IR$
3. **Loop rule:** Following around any loop in an electrical network the potential has to come back to the same value (sum of drops = sum of rises).

3/15/13

Physics 132

3

Very useful heuristic

- The Constant Potential Corollary (CPC)
 - Along any part of a circuit with 0 resistance, then $\Delta V = 0$, i.e., the voltage is constant since in any circuit element

$$\Delta V = IR$$

$$R = 0 \Rightarrow \Delta V = 0$$

(even if $I \neq 0$)

3/15/13

Physics 132

4

Electric Power

- The rate at which electric energy is depleted from a battery or dissipated (into heat or light) in a resistor is

$$Power = I\Delta V$$

3/15/13

Physics 132

5

Units

- Current (I) **Ampere** = Coulomb/sec
- Voltage (V) **Volt** = Joule/Coulomb
- E-Field (E) Newton/Coulomb = Volt/meter
- Resistance (R) **Ohm** = Volt/Ampere
- Capacitance (C) **Farad** = Volt/Coulomb
- Power (P) **Watt** = Joule/sec

3/15/13


Physics 132

6

Series and parallel

■ Series

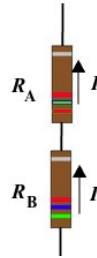- Same current flows through both devices



$$I = \frac{\Delta V_A}{R_A} = \frac{\Delta V_B}{R_B}$$


$$\frac{\Delta V_A}{\Delta V_B} = \frac{R_A}{R_B}$$

$$\Delta V = \Delta V_A + \Delta V_B$$

$$= I(R_A + R_B)$$

■ Parallel

- Same voltage drop across both devices

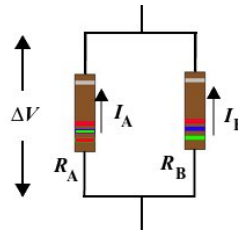

$$\Delta V = I_A R_A = I_B R_B$$

$$\frac{I_A}{I_B} = \frac{R_B}{R_A}$$

$$I = I_A + I_B$$

$$= \Delta V \left(\frac{1}{R_A} + \frac{1}{R_B} \right)$$

3/15/13