


March 15, 2013 Physics 132 Prof. E. F. Redish

■ **Theme Music:** Benny Goodman
AC/DC Current


■ **Cartoon:** Bob Thaves
Frank & Ernest



© Thaves/Diet by NEA, Inc. 3/15/13 Physics 132 1

Electric circuit elements


- **Batteries** — devices that maintain a constant electrical pressure difference across their terminals (like a water pump that raises water to a certain height).
- **Resistances** — devices that have significant drag and oppose current. Pressure will drop across them.
- **Capacitors** — devices that can maintain a separation of charge if there is a potential difference maintained across the,
- **Wires** — have very little resistance. We can ignore the drag in them (mostly — as long as there are other resistances present).

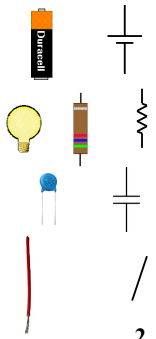

3/15/13 Physics 132 2

Foothold ideas: Kirchhoff's principles

1. **Flow rule:** The total amount of current flowing into any volume in an electrical network equals the amount flowing out.
2. **Ohm's law:** in a resistor, $\Delta V = IR$
3. **Loop rule:** Following around any loop in an electrical network the potential has to come back to the same value (sum of drops = sum of rises).



3/15/13 Physics 132 3

Very useful heuristic

- The Constant Potential Corollary (CPC)
 - Along any part of a circuit with 0 resistance, then $\Delta V = 0$, i.e., the voltage is constant since in any circuit element

$$\Delta V = IR$$

$$R = 0 \Rightarrow \Delta V = 0$$

(even if $I \neq 0$)

3/15/13 Physics 132 4

Electric Power

- The rate at which electric energy is depleted from a battery or dissipated (into heat or light) in a resistor is

$$Power = I\Delta V$$

3/15/13 Physics 132 5

Units


■ Current (I)	Ampere = Coulomb/sec
■ Voltage (V)	Volt = Joule/Coulomb
■ E-Field (E)	Newton/Coulomb = Volt/meter
■ Resistance (R)	Ohm = Volt/Ampere
■ Capacitance (C)	Farad = Volt/Coulomb
■ Power (P)	Watt = Joule/sec

3/15/13 Physics 132 6

Series and parallel

■ **Series**

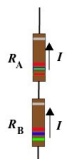– Same current flows through both devices




$$I = \frac{\Delta V_A}{R_A} = \frac{\Delta V_B}{R_B}$$

$$\frac{\Delta V_A}{\Delta V_B} = \frac{R_A}{R_B}$$

$$\Delta V = \Delta V_A + \Delta V_B = I(R_A + R_B)$$

■ **Parallel**

– Same voltage drop across both devices

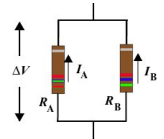

$$\Delta V = I_A R_A = I_B R_B$$

$$\frac{I_A}{I_B} = \frac{R_B}{R_A}$$

$$I = I_A + I_B = \Delta V \left(\frac{1}{R_A} + \frac{1}{R_B} \right)$$

3/15/13
