

# Lecture 38

- Real batteries
- Resistors in Parallel
- Example of Resistor Circuits
- Grounding

# Real Batteries

- terminal (user) voltage

$$\Delta V_{bat} = E - I r$$

- for resistor connected:

$$I = \frac{E}{R_{eq}} = \frac{E}{R + r}$$

$$\Delta V_R = I R = \frac{R}{R + r} E$$


$$\Delta V_{bat} = E - I r;$$

$$\Delta V_R = \Delta V_{bat} = E$$

- replace high by zero resistance  $\rightarrow I_{short} = \frac{E}{r}$   
( $\infty$  for ideal,  $r = 0$ )

- maximum possible current battery can produce



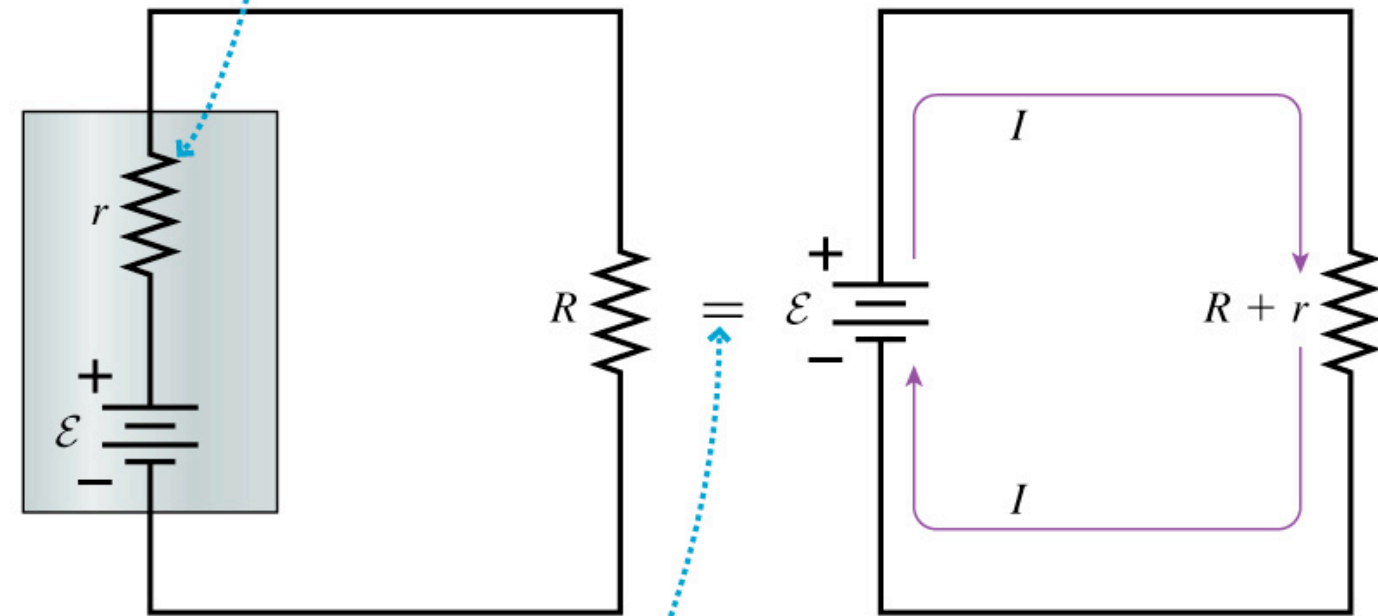
Although physically separated, the internal resistance  $r$  is electrically in series with  $R$ .



This means the two circuits are equivalent.

## Short Circuit

This wire is shorting out the battery.

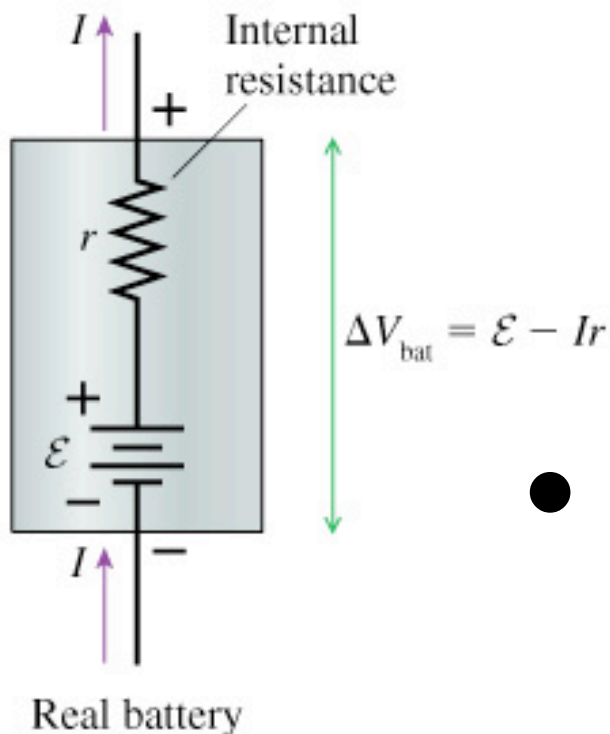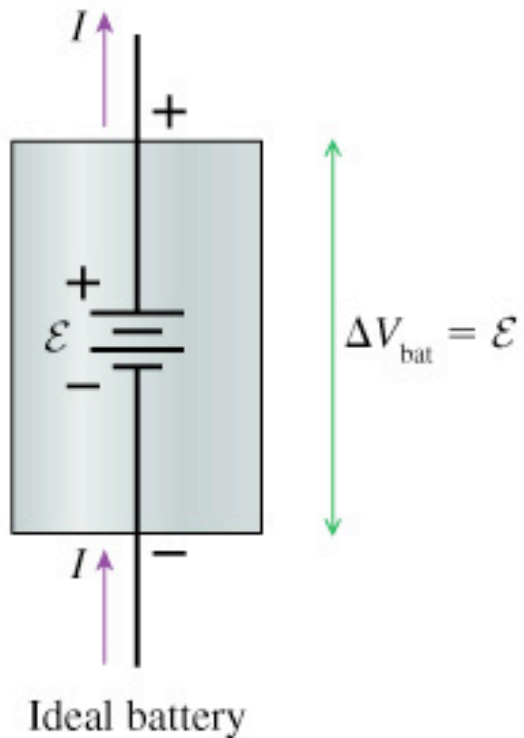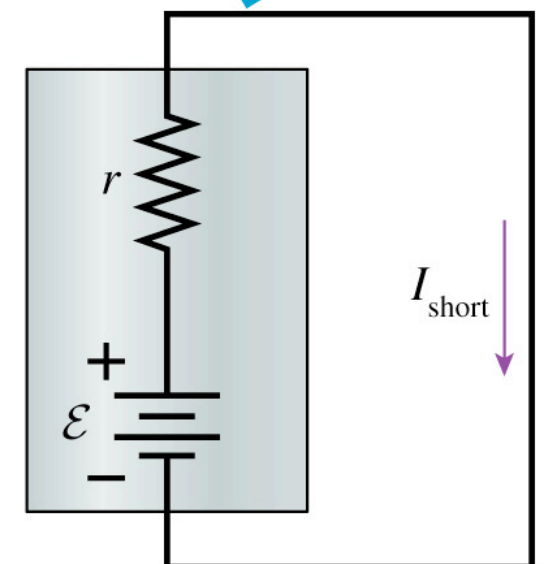

# Parallel Resistors

- potential differences same:

$$\Delta V_1 = \Delta V_2 = \dots = V_{cd}$$

- Kirchhoff's junction law:  $I = I_1 + I_2$

- Ohm's law:

$$I = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2} = \Delta V_{cd} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$


- Replace by equivalent resistance:

$$R_{cd} = \frac{\Delta V_{cd}}{I} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)^{-1} \quad (\text{parallel resistors})$$

- Identical resistors ( $R_1 = R_2$ ):  $R_{series\ eq} = 2R$ ;  $R_{parallel\ eq} = \frac{R}{2}$
- In general,  $R_{eq} < R_1$  or  $R_2$ ...in parallel

(a) Two resistors in parallel

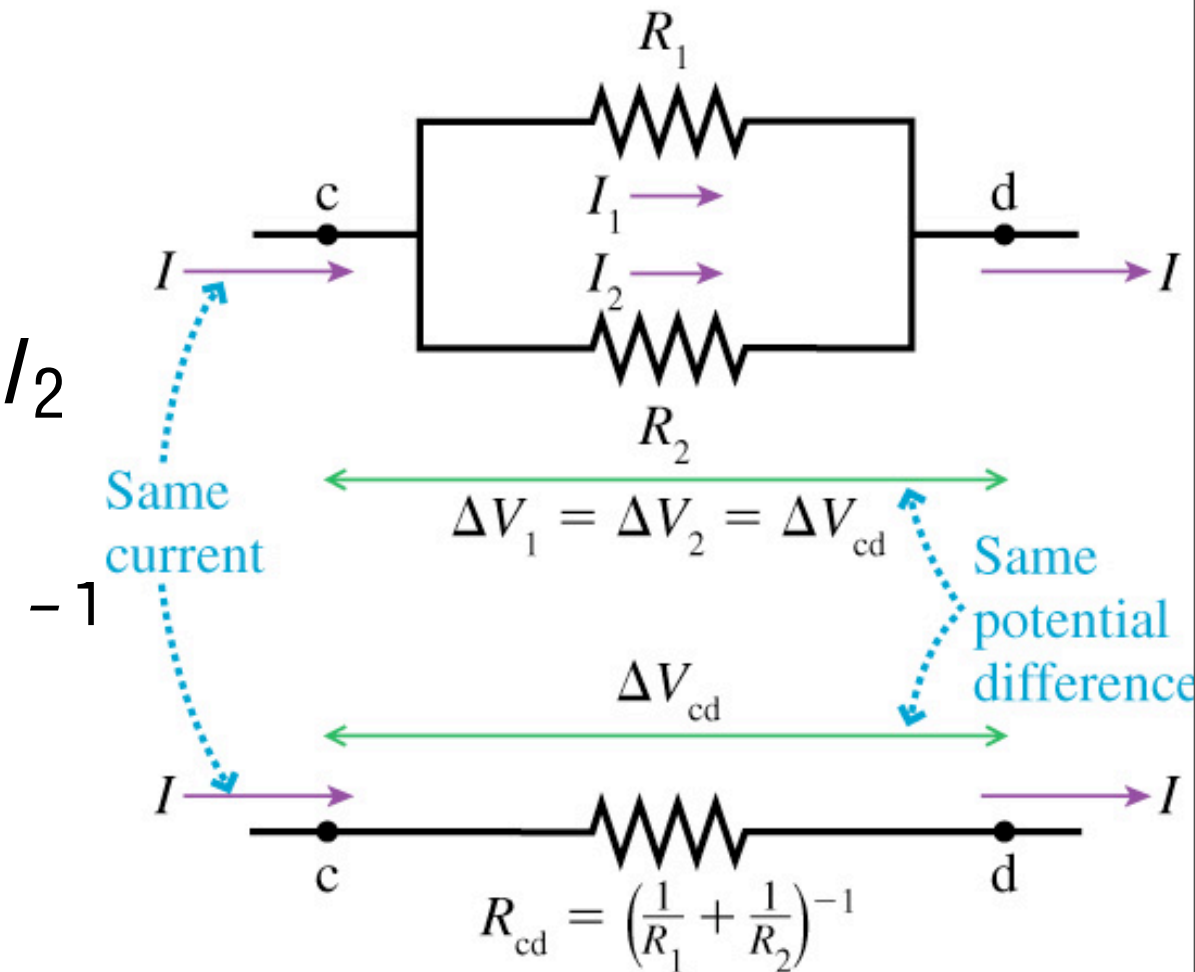

(b) An equivalent resistor

Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

# Voltmeters

- measure potential difference across circuit element (place in parallel; don't need to break connections, unlike for ammeter)



- total resistance:  $R_{eq} = \frac{1}{R} + \frac{1}{R_{voltmeter}}$

- in order not to change voltage:

$$R_{voltmeter} \gg R \text{ (ideally, } \infty)$$

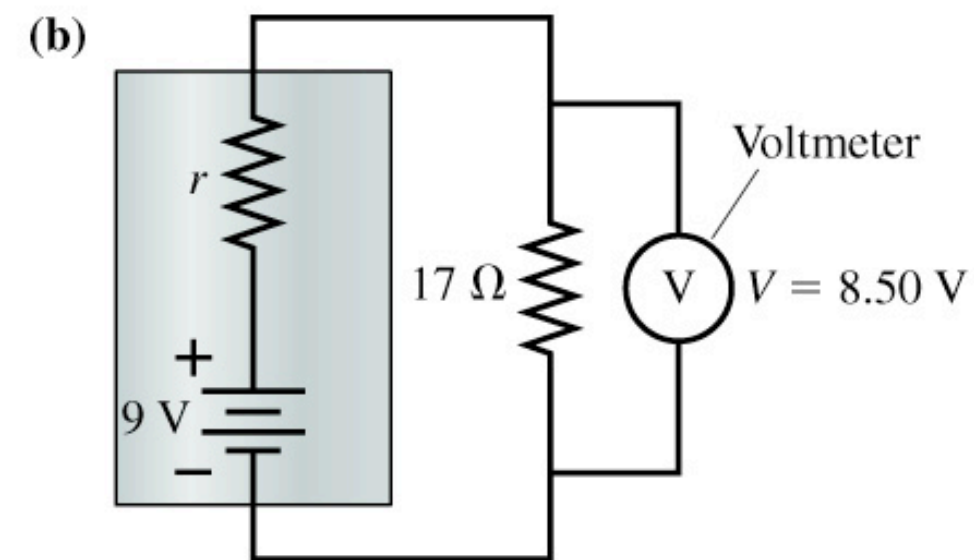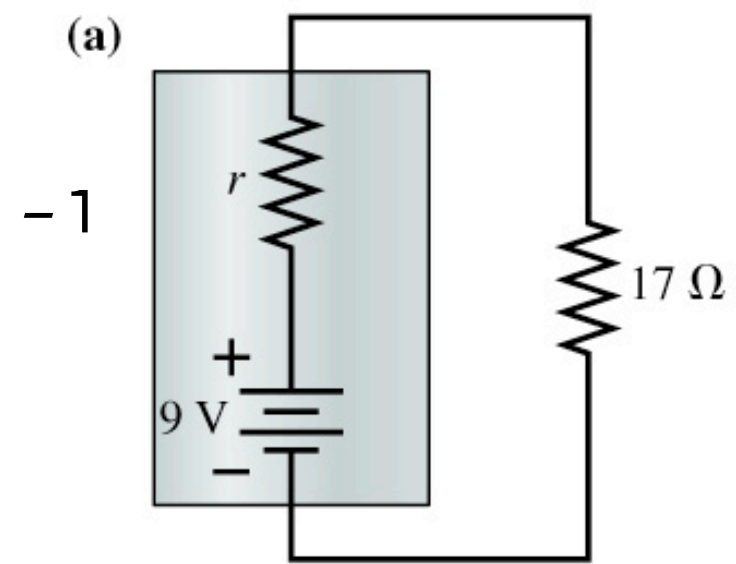
## Strategy for Resistor Circuits

- assume ideal wires, batteries
- use Kirchhoff's laws and rules for series and parallel resistors
- reduce to equivalent resistor (basic circuit)
- rebuild using current same for series and potential difference same for parallel



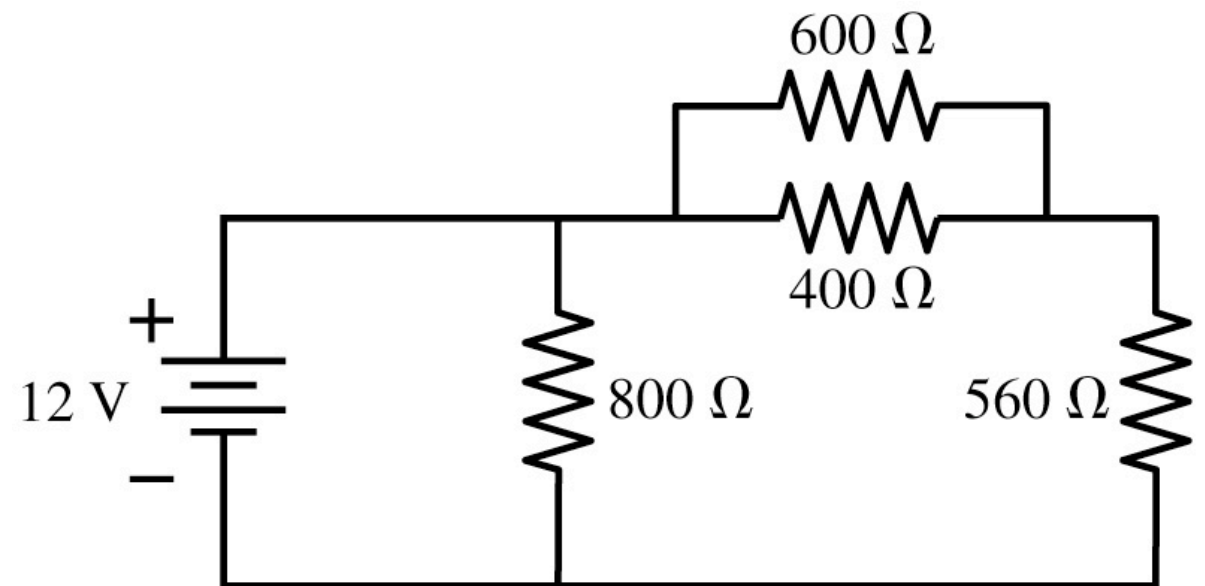
# Example of Resistor Circuit


- Find  $I$  and  $\Delta V$  for each resistor



(a) Break down the circuit

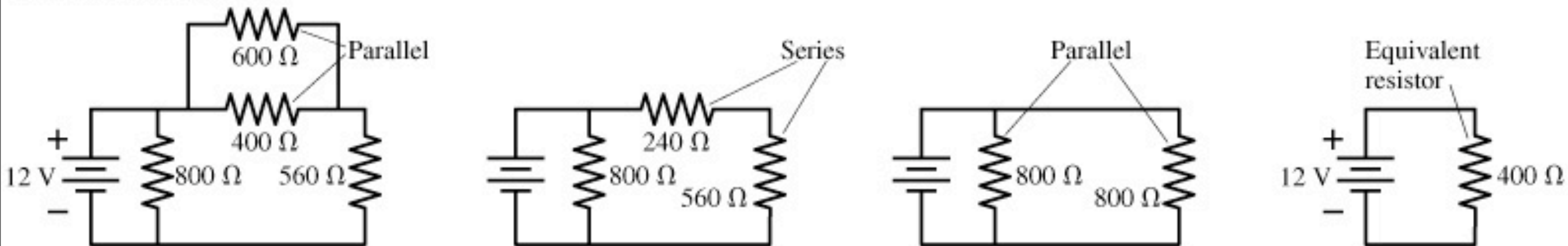


(b) Rebuild the circuit

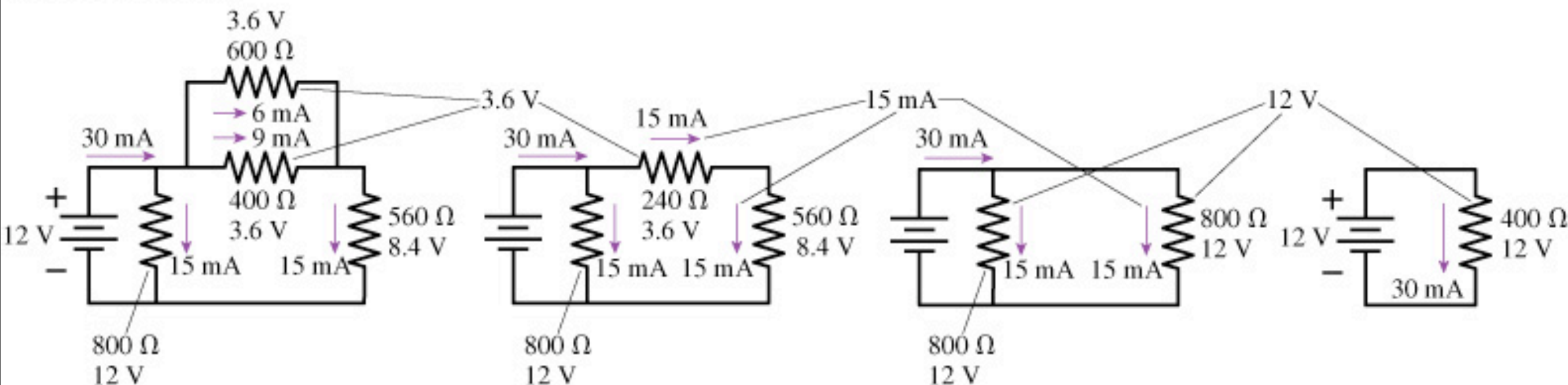



- so far, potential difference,  $\Delta V$  (physically meaningful), enters Ohm's law (no need to establish zero point)
- need common reference point for connecting 2 circuits
- grounding: connect 1 point in circuit to earth ( $V_{earth} = 0$ ) by ideal wire: no return wire (no current); wire is equipotential  $\rightarrow$  point in circuit has earth's potential  $\rightarrow$  specific value of potential at each point
- does not change how circuit functions... unless malfunction/breaking of circuit (enclose circuit in grounded case insulated from circuit): case comes in contact with circuit ( $\rightarrow$  touching would have caused electrocution)  $\rightarrow$  current thru' wire (fuse blows...)

# Grounding

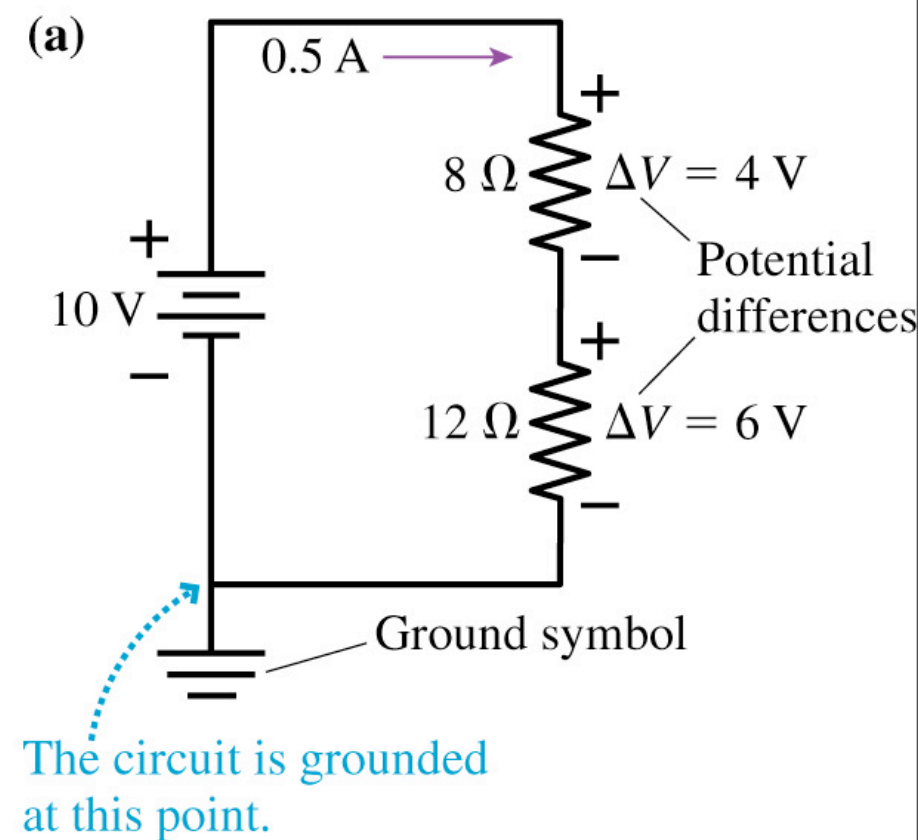

Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

