

HW 4 Solutions

$$32.4 \quad L = \mu_0 n^2 A \ell \quad \text{so} \quad n = \sqrt{\frac{L}{\mu_0 A \ell}} = \boxed{7.80 \times 10^3 \text{ turns/m}}$$


$$32.11 \quad |\mathcal{E}| = L \frac{dI}{dt} = (90.0 \times 10^{-3}) \frac{d}{dt}(t^2 - 6t) \text{ V}$$

$$(a) \quad \text{At } t = 1.00 \text{ s, } \mathcal{E} = \boxed{360 \text{ mV}}$$

$$(b) \quad \text{At } t = 4.00 \text{ s, } \mathcal{E} = \boxed{180 \text{ mV}}$$

$$(c) \quad \mathcal{E} = (90.0 \times 10^{-3})(2t - 6) = 0 \quad \text{when} \quad \boxed{t = 3.00 \text{ s}}$$
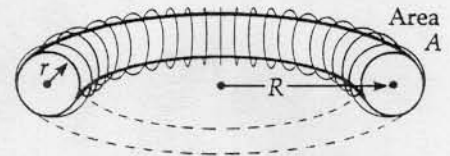
$$32.14 \quad L = \frac{N\Phi_B}{I} = \frac{NBA}{I} \approx \frac{NA}{I} \cdot \frac{\mu_0 NI}{2\pi R} = \boxed{\frac{\mu_0 N^2 A}{2\pi R}}$$



$$32.16 \quad I = \frac{\mathcal{E}}{R}(1 - e^{-Rt/L})$$

$$0.900 \frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R} [1 - e^{-R(3.00 \text{ s})/2.50 \text{ H}}]$$

$$\exp\left(-\frac{R(3.00 \text{ s})}{2.50 \text{ H}}\right) = 0.100$$

$$R = \frac{2.50 \text{ H}}{3.00 \text{ s}} \ln 10.0 = \boxed{1.92 \Omega}$$


$$32.24 \quad I = I_{\max}(1 - e^{-t/\tau})$$

$$0.980 = 1 - e^{-3.00 \times 10^{-3}/\tau}$$

$$0.0200 = e^{-3.00 \times 10^{-3}/\tau}$$

$$\tau = -\frac{3.00 \times 10^{-3}}{\ln(0.0200)} = 7.67 \times 10^{-4} \text{ s}$$
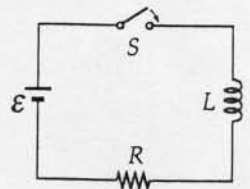
$$\tau = L/R, \text{ so } L = \tau R = (7.67 \times 10^{-4})(10.0) = \boxed{7.67 \text{ mH}}$$




32.25

Name the currents as shown. By Kirchoff's laws:

$$I_1 = I_2 + I_3 \quad (1)$$

$$+10.0 \text{ V} - 4.00 I_1 - 4.00 I_2 = 0 \quad (2)$$
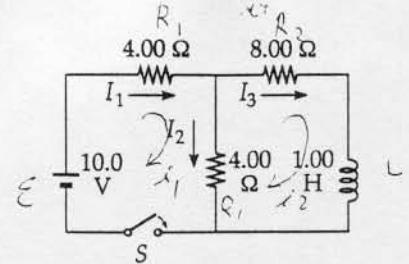
$$+10.0 \text{ V} - 4.00 I_1 - 8.00 I_3 - (1.00) \frac{dI_3}{dt} = 0 \quad (3)$$



From (1) and (2), $+10.0 - 4.00 I_1 - 4.00 I_1 + 4.00 I_3 = 0$ and $I_1 = 0.500 I_3 + 1.25 \text{ A}$

Then (3) becomes $10.0 \text{ V} - 4.00(0.500 I_3 + 1.25 \text{ A}) - 8.00 I_3 - (1.00) \frac{dI_3}{dt} = 0$

$$(1.00 \text{ H}) \left(\frac{dI_3}{dt} \right) + (10.0 \Omega) I_3 = 5.00 \text{ V}$$

We solve the differential equation using Equations 32.6 and 32.7:

$$I_3(t) = \frac{5.00 \text{ V}}{10.0 \Omega} \left[1 - e^{-(10.0 \Omega)t/1.00 \text{ H}} \right] = (0.500 \text{ A}) \left[1 - e^{-10t/s} \right]$$

$$I_1 = 1.25 + 0.500 I_3 = 1.50 \text{ A} - (0.250 \text{ A}) e^{-10t/s}$$


\sqrt{R}

32.28 (a) $I = \frac{\mathcal{E}}{R} = \frac{12.0 \text{ V}}{12.0 \Omega} = 1.00 \text{ A}$

(b) Initial current is 1.00 A, $\Delta V_{12} = (1.00 \text{ A})(12.00 \Omega) = 12.0 \text{ V}$

$$\Delta V_{1200} = (1.00 \text{ A})(1200 \Omega) = 1.20 \text{ kV}$$

$$\Delta V_L = 1.21 \text{ kV}$$

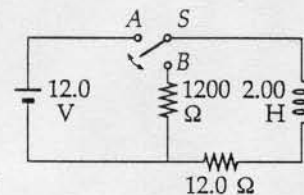

(c) $I = I_{\max} e^{-Rt/L}$: $\frac{dI}{dt} = -I_{\max} \frac{R}{L} e^{-Rt/L}$ and $-L \frac{dI}{dt} = \Delta V_L = I_{\max} R e^{-Rt/L}$

Solving $12.0 \text{ V} = (1212 \text{ V}) e^{-1212t/2.00}$ so $9.90 \times 10^{-3} = e^{-606t}$


Thus, $t = 7.62 \text{ ms}$

32.31 $L = \frac{N\Phi_B}{I} = \frac{200(3.70 \times 10^{-4})}{1.75} = 42.3 \text{ mH}$ so $U = \frac{1}{2} LI^2 = \frac{1}{2} (0.423 \text{ H})(1.75 \text{ A})^2 = 0.0648 \text{ J}$

*32.36 (a) $U = \frac{1}{2} LI^2 = \frac{1}{2} (4.00 \text{ H})(0.500 \text{ A})^2 = 0.500 \text{ J}$

(b) $\frac{dU}{dt} = LI \frac{dI}{dt} = \mathcal{E}I - I^2 R$
 $L \frac{dI}{dt} = \mathcal{E}I - I^2 R$
 $\frac{dU}{dt} = \mathcal{E}I - I^2 R = 4.00 \text{ J/s} = 4.00 \text{ W}$

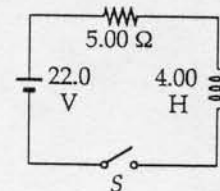(c) $\mathcal{P} = (\Delta V)I = (22.0 \text{ V})(0.500 \text{ A}) = 11.0 \text{ W}$



$$32.42 \quad M = \left| \frac{\mathcal{E}_2}{dI_1/dt} \right| = \frac{96.0 \text{ mV}}{1.20 \text{ A/s}} = \boxed{80.0 \text{ mH}}$$

$$32.52 \quad f = \frac{1}{2\pi\sqrt{LC}} : L = \frac{1}{(2\pi f)^2 C} = \frac{1}{(2\pi \cdot 120)^2 (8.00 \times 10^{-6})} = \boxed{0.220 \text{ H}}$$

$$32.56 \quad (a) \quad \omega_d = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} = \sqrt{\frac{1}{(2.20 \times 10^{-3})(1.80 \times 10^{-6})} - \left(\frac{7.60}{2(2.20 \times 10^{-3})}\right)^2} = 1.58 \times 10^4 \text{ rad/s}$$

$$\text{Therefore, } f_d = \frac{\omega_d}{2\pi} = \boxed{2.51 \text{ kHz}}$$

$$(b) \quad R_c = \sqrt{\frac{4L}{C}} = \boxed{69.9 \Omega}$$