

# HW 5 Solutions

$$33.2 \quad \Delta V_{\text{rms}} = \frac{170 \text{ V}}{\sqrt{2}} = 120 \text{ V}$$

$$(a) \quad \mathcal{P} = \frac{(\Delta V_{\text{rms}})^2}{R} \rightarrow R = \frac{(120 \text{ V})^2}{75.0 \text{ W}} = \boxed{193 \Omega}$$

$$(b) \quad R = \frac{(120 \text{ V})^2}{100 \text{ W}} = \boxed{144 \Omega}$$

33.6  $\mathcal{P} = I_{\text{rms}}(\Delta V_{\text{rms}})$  and  $\Delta V_{\text{rms}} = 120 \text{ V}$  for each bulb (parallel circuit), so:

$$I_1 = I_2 = \frac{\mathcal{P}_1}{\Delta V_{\text{rms}}} = \frac{150 \text{ W}}{120 \text{ V}} = \boxed{1.25 \text{ A}}, \text{ and } R_1 = \frac{\Delta V_{\text{rms}}}{I_1} = \frac{120 \text{ V}}{1.25 \text{ A}} = \boxed{96.0 \Omega} = R_2$$

$$I_3 = \frac{\mathcal{P}_3}{\Delta V_{\text{rms}}} = \frac{100 \text{ W}}{120 \text{ V}} = \boxed{0.833 \text{ A}}, \text{ and } R_3 = \frac{\Delta V_{\text{rms}}}{I_3} = \frac{120 \text{ V}}{0.833 \text{ A}} = \boxed{144 \Omega}$$

$$33.9 \quad (a) \quad X_L = \frac{\Delta V_{\text{max}}}{I_{\text{max}}} = \frac{100}{7.50} = 13.3 \Omega$$

$$L = \frac{X_L}{\omega} = \frac{13.3}{2\pi(50.0)} = 0.0424 \text{ H} = \boxed{42.4 \text{ mH}}$$

$$(b) \quad X_L = \frac{\Delta V_{\text{max}}}{I_{\text{max}}} = \frac{100}{2.50} = 40.0 \Omega$$

$$\omega = \frac{X_L}{L} = \frac{40.0}{42.4 \times 10^{-3}} = \boxed{942 \text{ rad/s}}$$

$$33.16 \quad Q_{\text{max}} = C(\Delta V_{\text{max}}) = C[\sqrt{2}(\Delta V_{\text{rms}})] = \boxed{\sqrt{2}C(\Delta V_{\text{rms}})}$$

$$33.18 \quad X_C = \frac{1}{\omega C} = \frac{1}{2\pi(60.0/\text{s})(1.00 \times 10^{-3} \text{ C/V})} = 2.65 \Omega$$

$v_C(t) = \Delta V_{\text{max}} \sin \omega t$ , to be zero at  $t = 0$

$$i_C = \frac{\Delta V_{\text{max}}}{X_C} \sin(\omega t + \phi) = \frac{\sqrt{2}(120 \text{ V})}{2.65 \Omega} \sin\left[2\pi \frac{60 \text{ s}^{-1}}{180 \text{ s}^{-1}} + 90.0^\circ\right] = (64.0 \text{ A}) \sin(120^\circ + 90.0^\circ) = \boxed{-32.0 \text{ A}}$$

$$33.20 \quad \omega L = \frac{1}{\omega C} \rightarrow \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(57.0 \times 10^{-6})(57.0 \times 10^{-6})}} = 1.75 \times 10^4 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = \boxed{2.79 \text{ kHz}}$$

$$33.24 \quad X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(60.0 \text{ Hz})(20.0 \times 10^{-12} \text{ F})} = 1.33 \times 10^8 \Omega$$

$$Z = \sqrt{(50.0 \times 10^3 \Omega)^2 + (1.33 \times 10^8 \Omega)^2} = 1.33 \times 10^8 \Omega$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{Z} = \frac{5000 \text{ V}}{1.33 \times 10^8 \Omega} = 3.77 \times 10^{-5} \text{ A}$$

$$(\Delta V_{\text{rms}})_{\text{body}} = I_{\text{rms}} R_{\text{body}} = (3.77 \times 10^{-5} \text{ A})(50.0 \times 10^3 \Omega) = \boxed{1.88 \text{ V}}$$

$$33.30 \quad Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \text{or} \quad (X_L - X_C) = \sqrt{Z^2 - R^2}$$

$$(X_L - X_C) = \sqrt{(75.0 \Omega)^2 - (45.0 \Omega)^2} = 60.0 \Omega$$

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{60.0 \Omega}{45.0 \Omega}\right) = 53.1^\circ$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{Z} = \frac{210 \text{ V}}{75.0 \Omega} = 2.80 \text{ A}$$

$$\mathcal{P} = (\Delta V_{\text{rms}}) I_{\text{rms}} \cos \phi = (210 \text{ V})(2.80 \text{ A}) \cos(53.1^\circ) = \boxed{353 \text{ W}}$$

$$33.38 \quad L = 20.0 \text{ mH}, C = 1.00 \times 10^{-7}, R = 20.0 \Omega, \Delta V_{\text{max}} = 100 \text{ V}$$

$$(a) \quad \text{The resonant frequency for a series } -RLC \text{ circuit is } f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \boxed{3.56 \text{ kHz}}$$

$$(b) \quad \text{At resonance, } I_{\text{max}} = \frac{\Delta V_{\text{max}}}{R} = \boxed{5.00 \text{ A}}$$

$$(c) \quad \text{From Equation 33.36, } Q = \frac{\omega_0 L}{R} = \boxed{22.4}$$

$$(d) \quad \Delta V_{L,\text{max}} = X_L I_{\text{max}} = \omega_0 L I_{\text{max}} = \boxed{2.24 \text{ kV}}$$

$$33.44 \quad (a) \quad (\Delta V_{2,\text{rms}}) = \frac{N_2}{N_1} (\Delta V_{1,\text{rms}}) \quad N_2 = \frac{(2200)(80)}{110} = \boxed{1600 \text{ windings}}$$

$$(b) \quad I_{1,\text{rms}} (\Delta V_{1,\text{rms}}) = I_{2,\text{rms}} (\Delta V_{2,\text{rms}}) \quad I_{1,\text{rms}} = \frac{(1.50)(2200)}{110} = \boxed{30.0 \text{ A}}$$

$$(c) \quad 0.950 I_{1,\text{rms}} (\Delta V_{1,\text{rms}}) = I_{2,\text{rms}} (\Delta V_{2,\text{rms}}) \quad I_{1,\text{rms}} = \frac{(1.20)(2200)}{110(0.950)} = \boxed{25.3 \text{ A}}$$

33.48

For the filter circuit,

$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{X_C}{\sqrt{R^2 + X_C^2}}$$

(a) At  $f = 600 \text{ Hz}$ ,

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(600 \text{ Hz})(8.00 \times 10^{-9} \text{ F})} = 3.32 \times 10^4 \Omega$$

and

$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{3.32 \times 10^4 \Omega}{\sqrt{(90.0 \Omega)^2 + (3.32 \times 10^4 \Omega)^2}} \approx \boxed{1.00}$$

(b) At  $f = 600 \text{ kHz}$ ,

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(600 \times 10^3 \text{ Hz})(8.00 \times 10^{-9} \text{ F})} = 33.2 \Omega$$

and

$$\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{33.2 \Omega}{\sqrt{(90.0 \Omega)^2 + (33.2 \Omega)^2}} = \boxed{0.346}$$

33.65 (a) From Equation 33.39,

$$\frac{N_1}{N_2} = \frac{\Delta V_1}{\Delta V_2}$$

Let output impedance

$$Z_1 = \frac{\Delta V_1}{I_1}$$

and the input impedance

$$Z_2 = \frac{\Delta V_2}{I_2}$$

so that

$$\frac{N_1}{N_2} = \frac{Z_1 I_1}{Z_2 I_2}$$

But from Eq. 33.40,

$$\frac{I_1}{I_2} = \frac{\Delta V_2}{\Delta V_1} = \frac{N_2}{N_1}$$

So, combining with the previous result we have

$$\boxed{\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}}}$$

(b)  $\frac{N_1}{N_2} = \sqrt{\frac{Z_1}{Z_2}} = \sqrt{\frac{8000}{8.00}} = \boxed{31.6}$