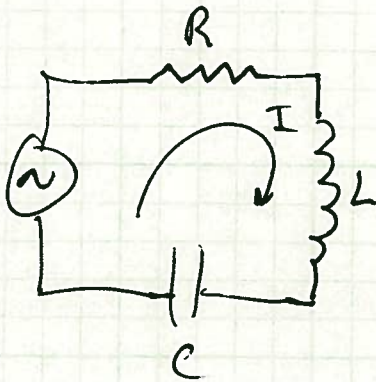



Driven RLC (series) circuit

$V_S = V_0 e^{i\omega t}$




Only one current phasor: \vec{I}
(this circuit has only one current).

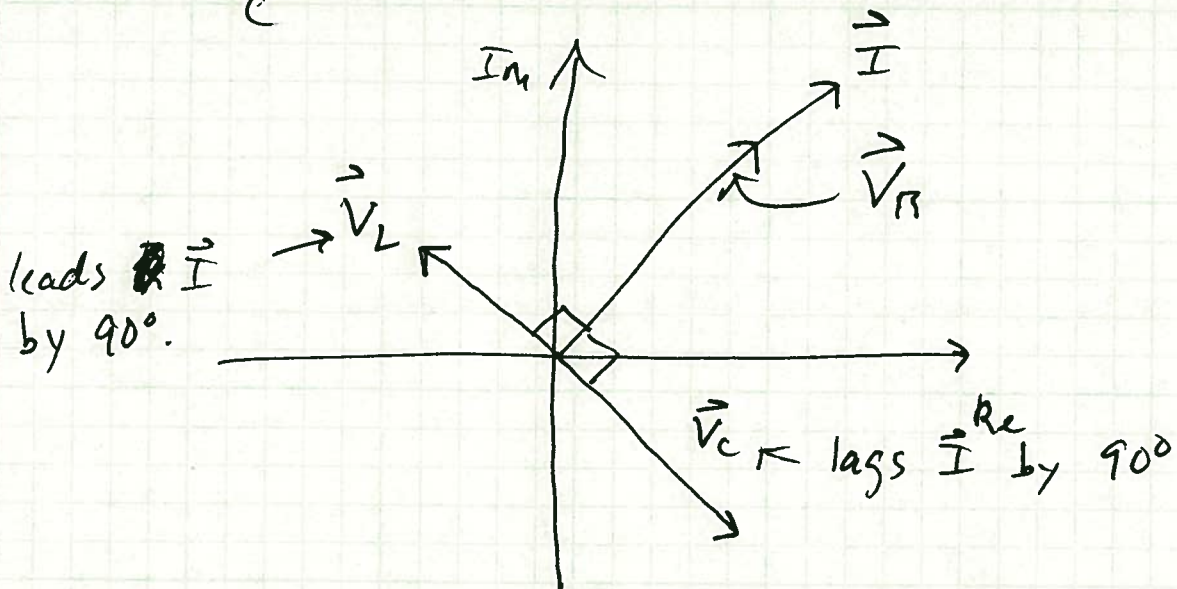Voltage phasors can be drawn relative to \vec{I} : $\vec{V}_R, \vec{V}_L, \vec{V}_C$



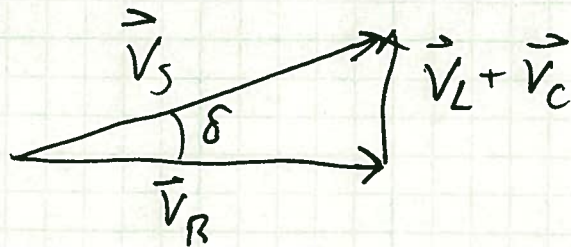Voltage Loop Rule: $\vec{V}_S = \vec{V}_R + \vec{V}_L + \vec{V}_C$



Phase shift:

$$\delta = \tan^{-1} \left[\frac{|\vec{V}_L + \vec{V}_C|}{|\vec{V}_R|} \right] = \tan^{-1} \left[\frac{i\omega L I_0 - \frac{i I_0}{\omega C}}{R I_0} \right]$$

$$= \tan^{-1} \left(\frac{|i\omega L I_0 - \frac{iI_0}{\omega C}|}{|R I_0|} \right) \quad \text{--- } |i\omega L I_0 - \frac{iI_0}{\omega C}| \quad (2)$$

$$= I_0 \left| i\omega L - \frac{i}{\omega C} \right|$$

$$= I_0 (\omega L - \frac{1}{\omega C})$$

$\hookrightarrow |R I_0| = R I_0$


~~$\neq \tan^{-1}$~~

$$= \tan^{-1} \left[\frac{I_0 (\omega L - \frac{1}{\omega C})}{I_0 (R)} \right], \text{ or, using } \omega_0^2 = \frac{1}{LC}$$

and $\gamma = \frac{R}{L}$,

$$\delta = \tan^{-1} \left[\frac{\omega^2 - \omega_0^2}{\omega \gamma} \right]$$

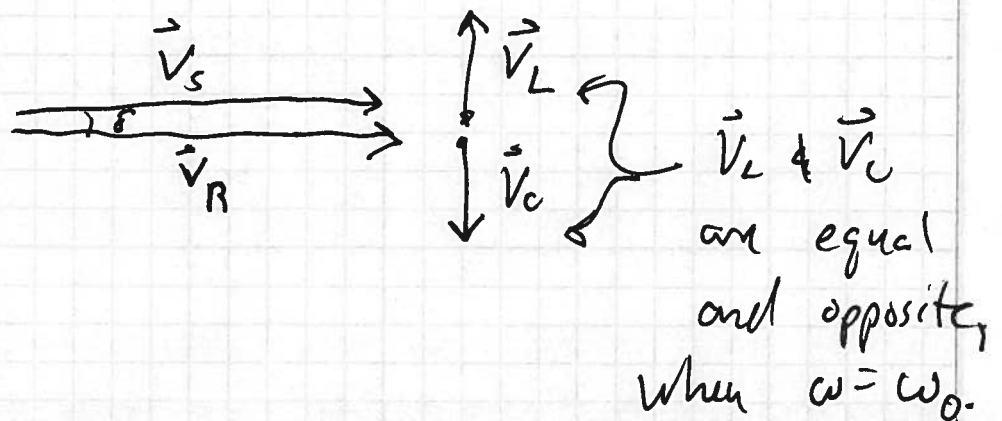What does this mean? Well, if we choose to drive the circuit with frequency $\omega = \omega_0$, then the phase difference between \vec{V}_S and V_R is zero. Then the phasor diagram looks like:




Conversely, suppose we choose $\omega = \text{very, very large}$.

Then $\vec{V}_C = \left(\frac{-i}{\omega C}\right) \vec{I} \approx \emptyset$

and $\vec{V}_L = (i\omega L) \vec{I} \approx \text{large}$, and the

phasor diagram is

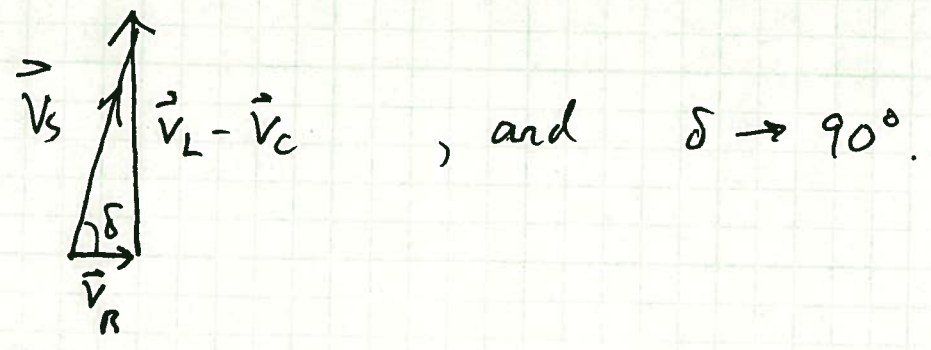


~~When does the~~

Question

At what driving frequency is the current maximal?

Answer: \vec{I} is maximal when \vec{V}_R is maximal, since $\vec{V}_R = \vec{I}R$. But $|\vec{V}_R|$ can never be larger than $|\vec{V}_S|$; since they have to add to zero in ~~that~~

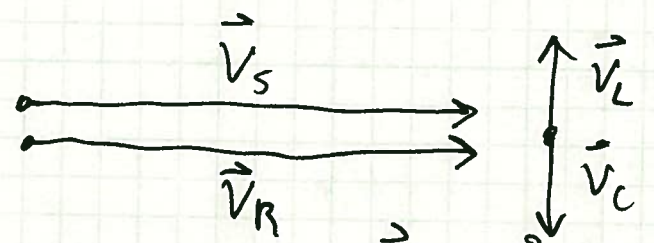

This happens when $\vec{V}_L + \vec{V}_C = \emptyset$


or $(i\omega L)I_0 + \left(\frac{-i}{\omega C}\right)I_0 = \emptyset$

or $\omega^2 = \frac{1}{LC}$

$\omega = \frac{1}{\sqrt{LC}} = \omega_0$

← condition for maximal current.

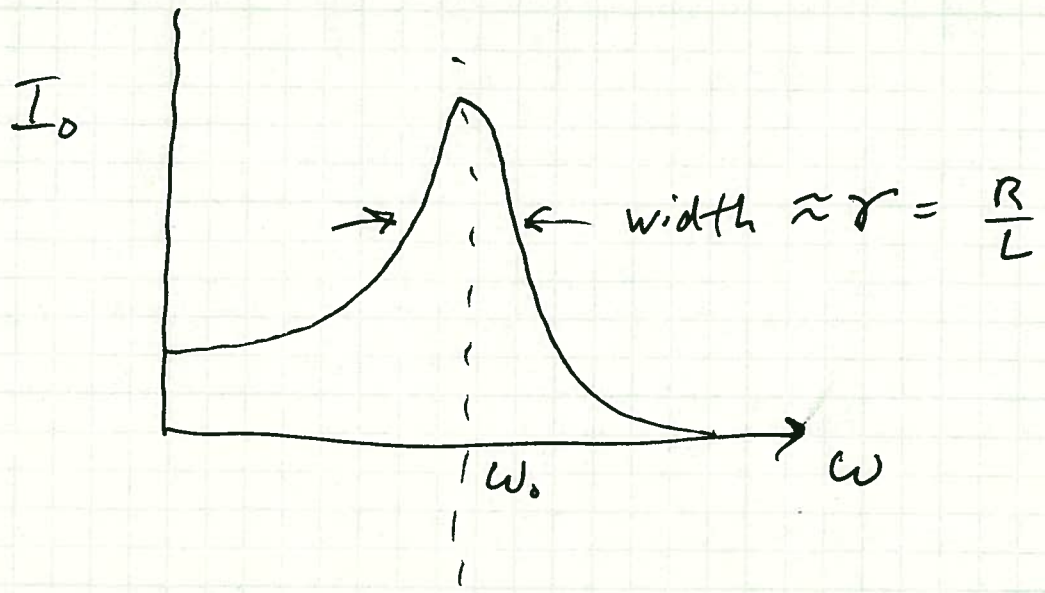The amplitude of the current displays a resonance near $\omega = \omega_0$:



Series and Parallel impedance


We have the following rules for impedances in AC circuits:

- ① Resistor : $V = I Z_R$, where $Z_R = R$
 - ② Capacitor : $V = I Z_C$, where $Z = \frac{-i}{\omega C}$
 - ③ Inductor : $V = I Z_L$, where $Z_L = i\omega L$
- phase shift between V & I

IF we combine two elements in series, then the total voltage drop is

$$\vec{V}_{total} = \vec{I}Z_1 + \vec{I}Z_2 \leftarrow \text{because } Z_1 \text{ \& } Z_2 \text{ share the same } \vec{I}$$

$$= \vec{I}(Z_1 + Z_2)$$

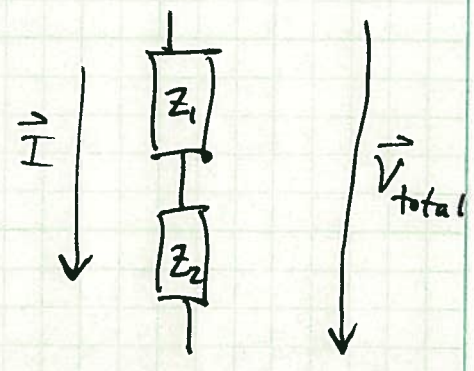


$\therefore \vec{V}_{total} = \vec{I}(Z_{\text{series}})$ where $Z_{\text{series}} = Z_1 + Z_2$.

\therefore The impedance of two elements in series is the simple sum of Z_1 & Z_2 .

IF we combine two elements in parallel, then the total current is ^{voltage drop}

$$\vec{V}_{total} = \vec{I}_1 Z_1 \quad \text{and}$$

$$\vec{V}_{total} = \vec{I}_2 Z_2$$

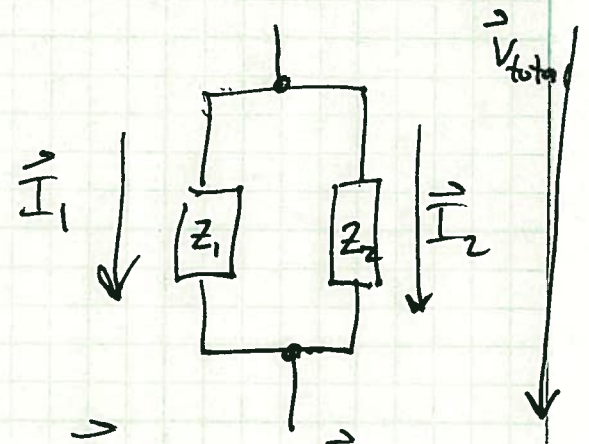

The total current is

$$\vec{I}_{total} = \vec{I}_1 + \vec{I}_2 = \frac{\vec{V}_{total}}{Z_1} + \frac{\vec{V}_{total}}{Z_2}$$

$$\therefore \vec{V}_{total} = \vec{I}_{total} \left(\frac{1}{Z_1^{-1} + Z_2^{-1}} \right)$$

$\vec{V}_{total} = \vec{I}_{total} Z_{\text{parallel}}$, where $Z_{\text{parallel}} = \frac{1}{Z_1^{-1} + Z_2^{-1}}$

∴


$$Z_{series} = Z_1 + Z_2$$

$$Z_{parallel} = \frac{1}{Z_1^{-1} + Z_2^{-1}}$$

Example RL ~~par.~~ Series circuit (driven)

AMPAD

V_S

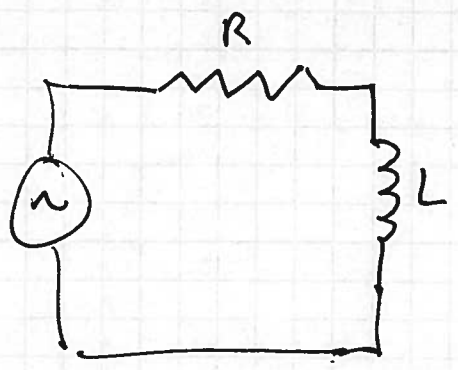

$$Z_{total} = Z_R + Z_L$$

$$Z_{total} = R + i\omega L$$

$$\therefore \vec{V}_S = \vec{I}_{total} Z_{total}$$

$$\vec{V}_S = \vec{I}_{total} (R + i\omega L)$$


∴ phase difference between \vec{V}_S & \vec{I}_{total} :

$$\delta = \text{phase of } (R + i\omega L) = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

∴ magnitude of current:

$$|\vec{I}_{total}| = I_0 = \frac{|\vec{V}_S| \leftarrow V_0}{|R + i\omega L|} = \frac{V_0}{\sqrt{R^2 + (\omega L)^2}}$$

Example RL parallel circuit (driven)

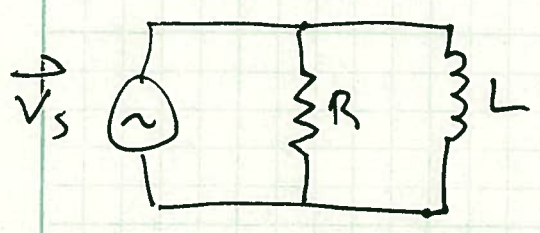


$$Z_{total} = \frac{1}{Z_R^{-1} + Z_L^{-1}}$$

$$= \frac{1}{R^{-1} + (i\omega L)^{-1}}$$

$$= \frac{(R\omega L) \times (\omega L + iR)}{(\omega L - iR) \times (\omega L + iR)}$$

$$= \left(\frac{R\omega L^2}{(\omega L)^2 + R^2} \right) (\omega + i\frac{R}{L})$$

or

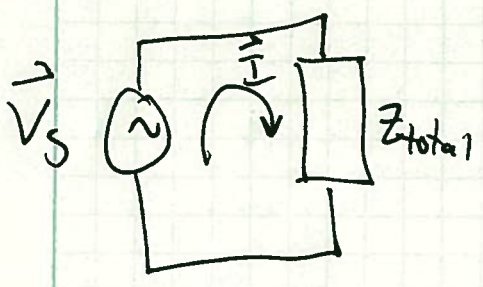

$$Z_{total} = \left(\frac{R\omega L^2}{(\omega L)^2 + R^2} \right) (\omega + i\tau)$$

$$\therefore \vec{V}_{s_{total}} = \vec{I}_{total} \left[\left(\frac{R\omega L^2}{(\omega L)^2 + R^2} \right) (\omega + i\tau) \right] \quad \text{where } \tau = \frac{R}{L}$$

Phase difference between \vec{V}_s & \vec{I}_{total} .


$$\delta = \tan^{-1} \left(\frac{\tau}{\omega} \right) \leftarrow \text{For very high } \omega, \delta \rightarrow \phi, \text{ like a resistor}$$

\leftarrow For very low ω , $\delta \rightarrow 90^\circ$, like an inductor.

Exam 1 Review

Simple Harmonic Oscillator (no damping)
(no driving force)

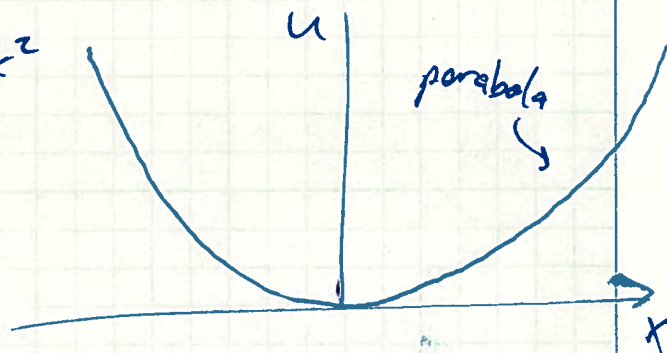$F = -kx \Rightarrow U = \frac{1}{2} kx^2$



Eg. of motion:


$\ddot{x} + \frac{k}{m}x = 0$

Defn $\omega_0^2 = k/m$
 Solution: $x = A e^{i(\omega_0 t + \delta)}$
 ↑
 natural frequency.

A, δ determined by initial conditions

Small Oscillations: Near a stable equilibrium, almost any potential function is approximately quadratic.

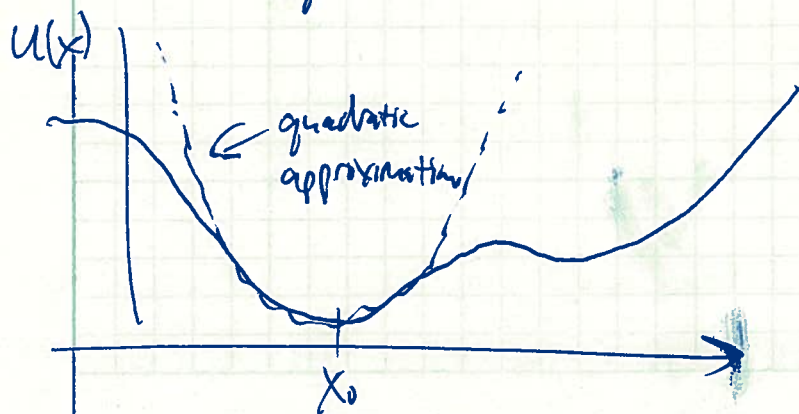$U(x_0 + a) \approx U(x_0) + U'(x_0)a + \frac{1}{2}U''(x_0)a^2 + \dots$
 ↑ ↑ displacement
 equilibrium



$U'(x_0) = 0$ since x_0 is an equilibrium point.

2

Frequency of small oscillations: $\omega_0 \approx \sqrt{\frac{U''(x_0)}{m}}$

near an equilibrium.

Plan Pendulum: $U = mgl(1 - \cos \theta)$

$\Rightarrow \omega_0 = \sqrt{g/l}$

Complex Numbers


$z = x + iy = Ae^{i\theta}$

~~A~~ $A = \sqrt{x^2 + y^2}$, $\theta = \tan^{-1}(y/x)$

$x = A \cos \theta$, $y = A \sin \theta$

$e^{i\theta} = \cos(\theta) + i \sin(\theta)$ Euler Formula

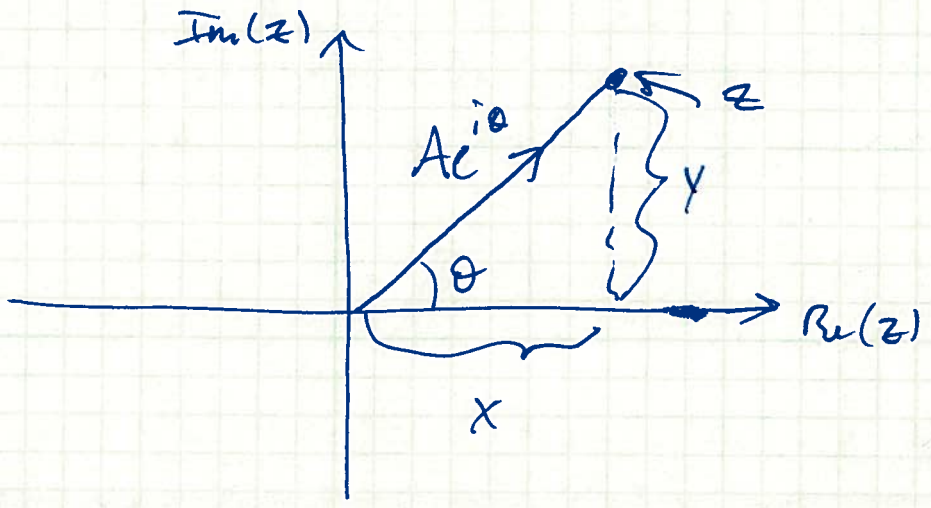$x = \frac{e^{i\theta} + e^{-i\theta}}{2}$, $y = \frac{e^{i\theta} - e^{-i\theta}}{2}$



$$z^* = \text{Complex conjugate} = x - iy \quad (\text{if } z = x + iy)$$

$$= Ae^{-i\theta} \quad (\text{if } z = Ae^{i\theta})$$

Division:

$$\frac{1}{x + iy} = \frac{(x - iy)}{(x + iy)(x - iy)} = \frac{x - iy}{x^2 + y^2}$$

Also:


$$zz^* = (x + iy)(x - iy) = x^2 + y^2 = A^2$$

Also:

$$e^{i\pi/2} = i$$

Also:

$$e^{i\pi} = -1$$

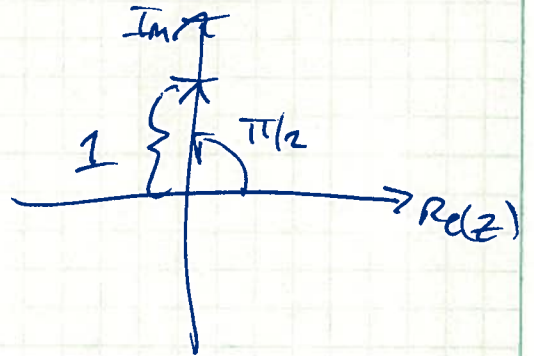

Also: $e^{i\pi} + 1 = 0$ ← nice algebraic equation.

Forced Oscillator

Eq of Motion

$$\ddot{x} + \omega_0^2 x = \frac{F(t)}{m} \quad \text{If } F(t) = F_0 e^{i\omega t}$$

$$\ddot{x} + \omega_0^2 x = \frac{F_0}{m} e^{i\omega t}$$

\uparrow natural frequency
 \uparrow driving frequency

Also Add damping: $F_{drag} = -bv = -b\dot{x}$

\uparrow
some constant

$$\ddot{x} + \gamma \dot{x} + \omega_0^2 x = \frac{F_0}{m} e^{i\omega t}$$

where $\gamma \equiv \frac{b}{m}$

$$\omega_0^2 = \frac{k}{m}$$

Solution:

Steady-state (Long-term) Solution:

$$x(t) = A_{\neq}(\omega) e^{i(\omega t + \phi(\omega))}$$


no free parameters

where $A_{\neq}(\omega) = \frac{F_0/m}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega\gamma)^2}}$

$$\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega\gamma)^2}$$

and $\phi_{\neq}(\omega) = -\tan^{-1} \left[\frac{\omega\gamma}{\omega_0^2 - \omega^2} \right]$

ω_{\neq} = driving frequency

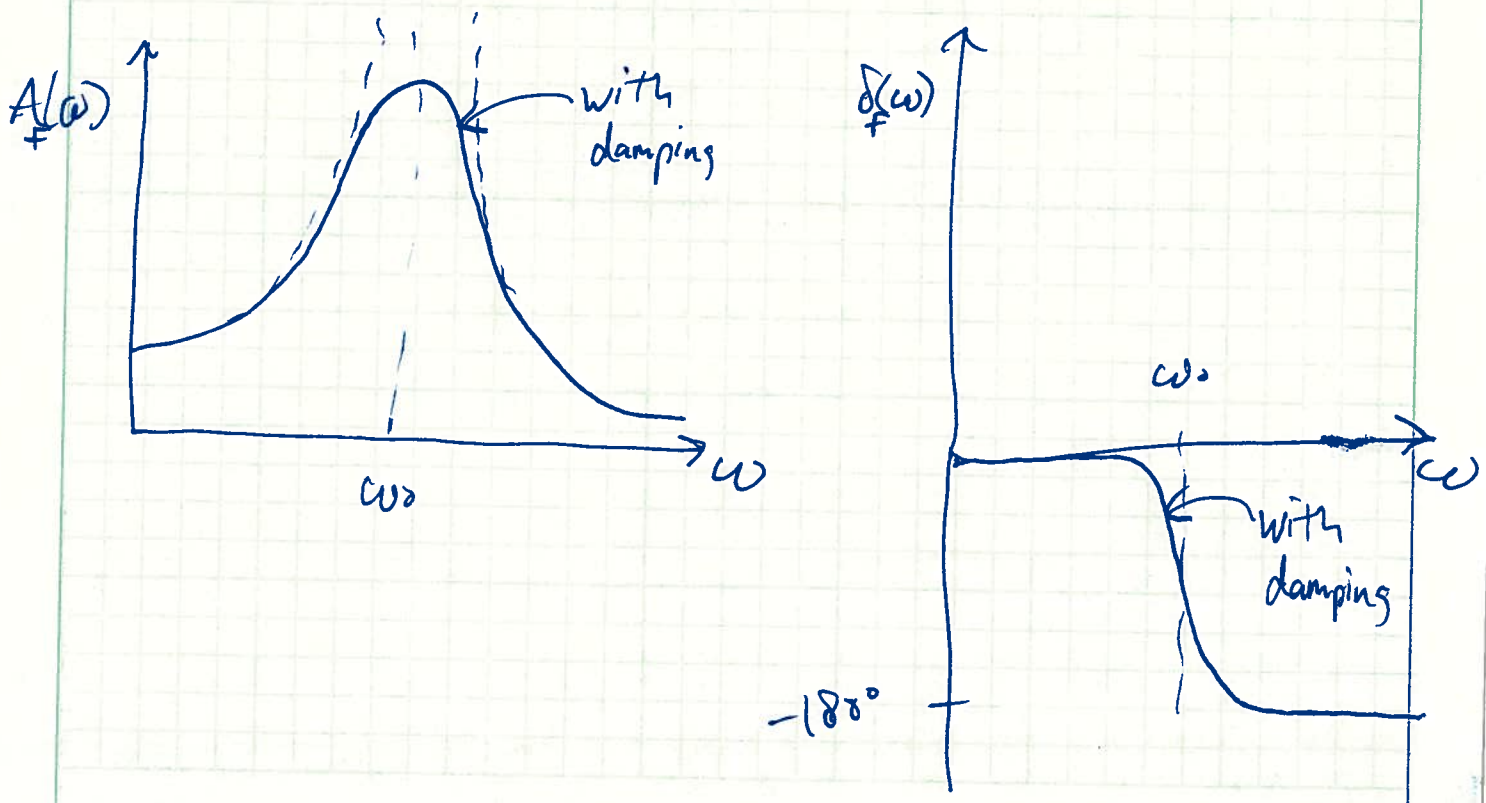

(Short-term)

Including the transient solution (Short-term Behavior):

$$x(t) = A(\omega_f) e^{i(\omega_f t + \phi_f(\omega_f))} + B e^{-\gamma/2 t} e^{i(\omega_d t + \delta_d)}$$

$$\omega_d = \text{damped frequency} = \sqrt{\omega_0^2 - \gamma^2/4}$$

B & δ_d = Free parameters, determined by initial conditions.

Special case: Damped oscillator, no forcing function

Then $F_0 = 0$, $A(\omega_f) = 0$,

$$\text{and } x(t) = B e^{-\gamma/2 t} e^{i(\omega_d t + \delta_d)}$$

↑
damping factor

Energy

- Mechanical Oscillators: $KE = \frac{1}{2} m \dot{x}^2$
 $U = \frac{1}{2} k x^2$

- Electrical Oscillators: $U_E = \int_{\text{all space}} \frac{1}{2} \epsilon_0 |\vec{E}|^2 dV$

for capacitors $\rightarrow = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$

$$U_B = \int_{\text{all space}} \frac{1}{2\mu_0} |\vec{B}|^2 dV$$

for inductors $\rightarrow = \frac{1}{2} LI^2$

Energy loss $Q = \frac{\omega_0}{\gamma} = \text{unitless}$ & very large for lightly damped oscillators.

For lightly damped oscillators

$$Q = \frac{\text{Fraction of energy lost in time } t = \frac{1}{\omega_0}}{\text{Fraction of energy loss in one period}} = \frac{2\pi}{\text{Fraction of energy loss in one period}}$$

Energy loss: $E(t) = E_0 e^{-\gamma t} = KE(t) + U(t)$ for mechanical oscillators
 $= U_E(t) + U_B(t)$ for electrical oscillators

AC circuits

Voltage rules:

$ V_C = \left \frac{1}{C} Q \right $	Capacitor
$ V_L = \left L \frac{dI}{dt} \right $	Inductor
$ V_R = IR $	Resistor

Simple LC circuit: $\omega_0 = \frac{1}{\sqrt{LC}}$ (simple harmonic oscillator)

Impedances:

$$Z_R = R$$

$$Z_L = i\omega L$$


$$Z_C = \frac{-i}{\omega C}$$

Series Combination: $Z_{\text{series}} = Z_1 + Z_2$

Parallel Combination: $Z_{\text{parallel}} = \left[(Z_1)^{-1} + (Z_2)^{-1} \right]^{-1}$

For any element or combination of elements,
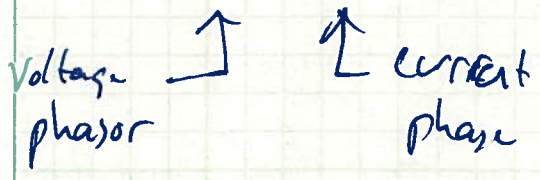
$$\vec{V} = \vec{I} Z \leftarrow \text{impedance, possibly complex.}$$



~~if~~ In general Z is complex, which means that there is a phase offset between \vec{V} & \vec{I} .

The ~~ratio~~ ratio of $\frac{V_0}{I_0} = |Z|$.

$$\vec{V}_L = \vec{I}_L (i\omega L)$$

↑ this means V_L leads I_L by 90° .

$$\vec{V}_C = \vec{I}_C \left(\frac{-i}{\omega C}\right)$$

↑ this means V_C lags I_C by 90°

Phasor Diagrams show the geometric relationships between \vec{V} & \vec{I} for a circuit.

This can be very useful when combined with a sum rule like $\vec{V}_{total} = \vec{V}_1 + \vec{V}_2$ or $\vec{I}_{total} = \vec{I}_1 + \vec{I}_2$

