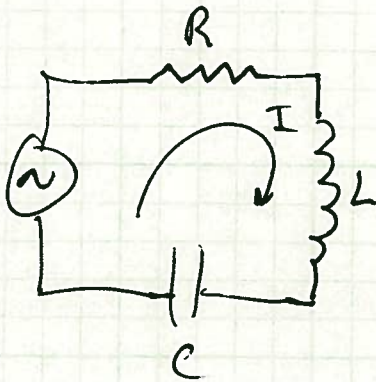



Driven RLC (series) circuit

$V_S = V_0 e^{i\omega t}$




Only one current phasor: \vec{I}
(this circuit has only one current).

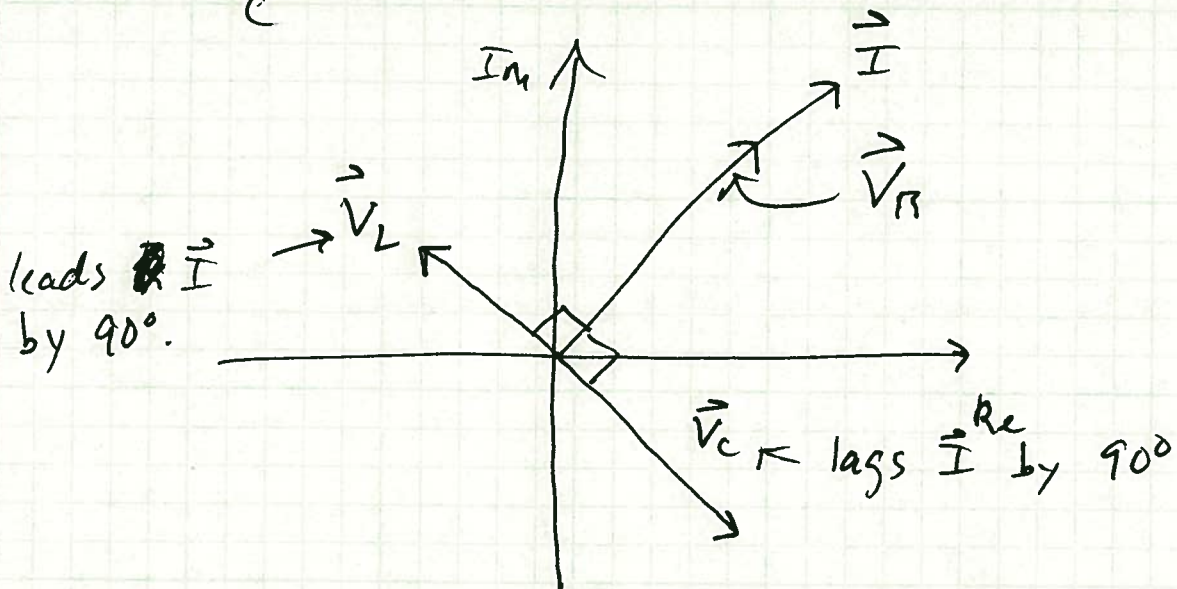Voltage phasors can be drawn relative to \vec{I} : $\vec{V}_R, \vec{V}_L, \vec{V}_C$



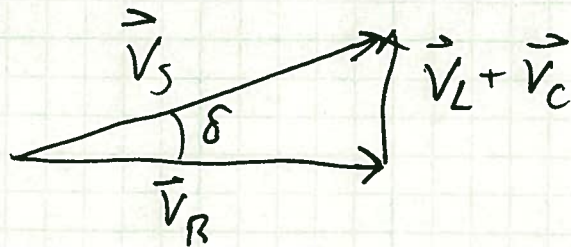Voltage Loop Rule: $\vec{V}_S = \vec{V}_R + \vec{V}_L + \vec{V}_C$



Phase shift:

$$\delta = \tan^{-1} \left[\frac{|\vec{V}_L + \vec{V}_C|}{|\vec{V}_R|} \right] = \tan^{-1} \left[\frac{i\omega L I_0 - \frac{i I_0}{\omega C}}{R I_0} \right]$$

$$= \tan^{-1} \left(\frac{|i\omega L I_0 - \frac{iI_0}{\omega C}|}{|R I_0|} \right) \quad \text{--- } |i\omega L I_0 - \frac{iI_0}{\omega C}| \quad (2)$$

$$= I_0 \left| i\omega L - \frac{i}{\omega C} \right|$$

$$= I_0 (\omega L - \frac{1}{\omega C})$$

$\hookrightarrow |R I_0| = R I_0$


~~$\neq \tan^{-1}$~~

$$= \tan^{-1} \left[\frac{I_0 (\omega L - \frac{1}{\omega C})}{I_0 (R)} \right], \text{ or, using } \omega_0^2 = \frac{1}{LC}$$

and $\gamma = \frac{R}{L}$,

$$\delta = \tan^{-1} \left[\frac{\omega^2 - \omega_0^2}{\omega \gamma} \right]$$

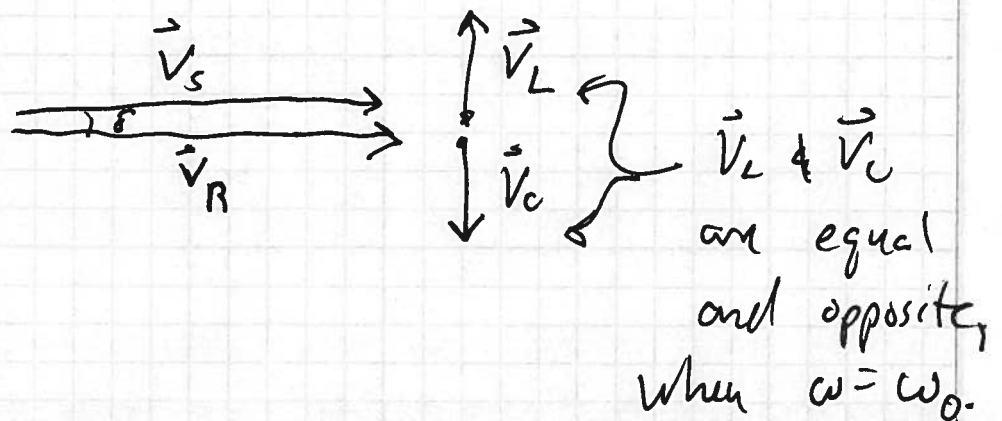What does this mean? Well, if we choose to drive the circuit with frequency $\omega = \omega_0$, then the phase difference between \vec{V}_S and V_R is zero. Then the phasor diagram looks like:




Conversely, suppose we choose $\omega = \text{very, very large}$.

Then $\vec{V}_C = \left(\frac{-i}{\omega C}\right) \vec{I} \approx \emptyset$

and $\vec{V}_L = (i\omega L) \vec{I} \approx \text{large}$, and the

phasor diagram is

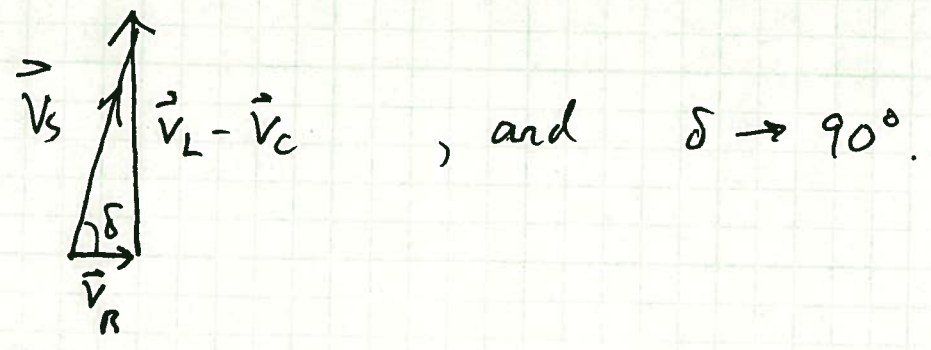


~~When does the~~

Question

At what driving frequency is the current maximal?

Answer: \vec{I} is maximal when \vec{V}_R is maximal, since $\vec{V}_R = \vec{I}R$. But $|\vec{V}_R|$ can never be larger than $|\vec{V}_s|$; since they have to add to zero in ~~that~~

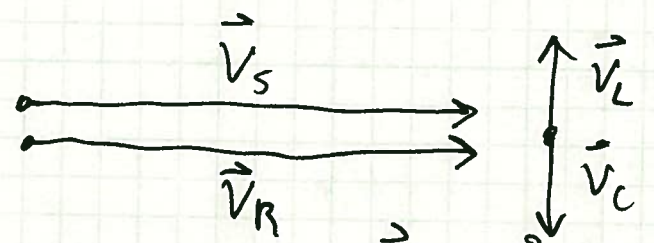

This happens when $\vec{V}_L + \vec{V}_C = \emptyset$


or $(i\omega L)I_0 + \left(\frac{-i}{\omega C}\right)I_0 = \emptyset$

or $\omega^2 = \frac{1}{LC}$

$\omega = \frac{1}{\sqrt{LC}} = \omega_0$

← condition for maximal current.

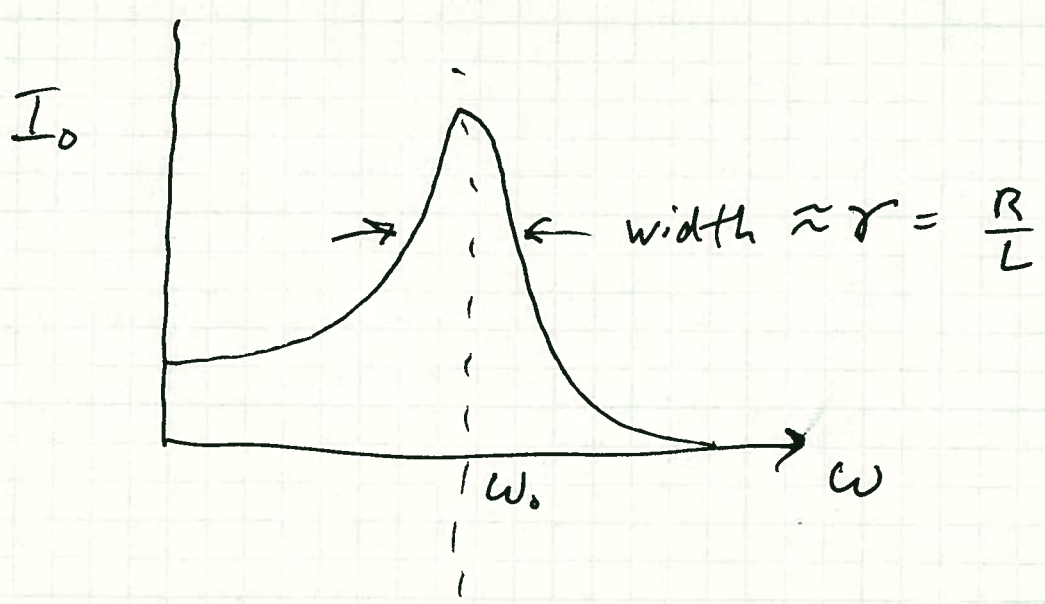The amplitude of the current displays a resonance near $\omega = \omega_0$:



Series and Parallel impedance


We have the following rules for impedances in AC circuits:

- ① Resistor: $V = I Z_R$, where $Z_R = R$
 - ② Capacitor: $V = I Z_C$, where $Z = \frac{-i}{\omega C}$
 - ③ Inductor: $V = I Z_L$, where $Z_L = i\omega L$
- phase shift between V & I

IF we combine two elements in series, then the total voltage drop is

$$\vec{V}_{total} = \vec{I}Z_1 + \vec{I}Z_2 \leftarrow \text{because } Z_1 \text{ \& } Z_2 \text{ share the same } \vec{I}$$

$$= \vec{I}(Z_1 + Z_2)$$

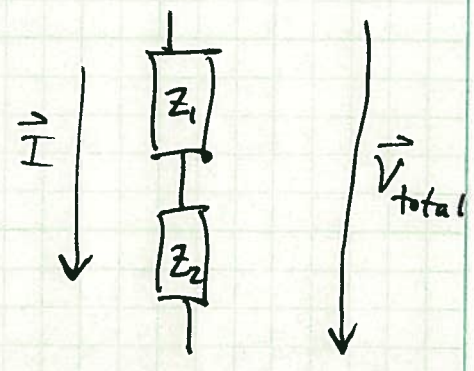


$\therefore \vec{V}_{total} = \vec{I}(Z_{\text{series}})$ where $Z_{\text{series}} = Z_1 + Z_2$.

\therefore The impedance of two elements in series is the simple sum of Z_1 & Z_2 .

IF we combine two elements in parallel, then the total current is ^{voltage drop}

$$\vec{V}_{total} = \vec{I}_1 Z_1 \quad \text{and}$$

$$\vec{V}_{total} = \vec{I}_2 Z_2$$

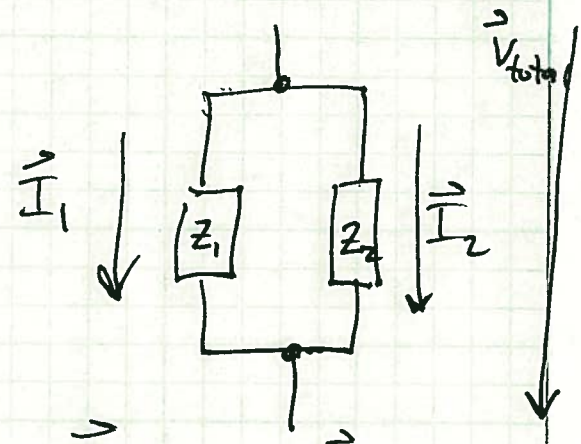

The total current is

$$\vec{I}_{total} = \vec{I}_1 + \vec{I}_2 = \frac{\vec{V}_{total}}{Z_1} + \frac{\vec{V}_{total}}{Z_2}$$

$$\therefore \vec{V}_{total} = \vec{I}_{total} \left(\frac{1}{Z_1^{-1} + Z_2^{-1}} \right)$$

$\vec{V}_{total} = \vec{I}_{total} Z_{\text{parallel}}$, where $Z_{\text{parallel}} = \frac{1}{Z_1^{-1} + Z_2^{-1}}$

∴


$$Z_{series} = Z_1 + Z_2$$

$$Z_{parallel} = \frac{1}{Z_1^{-1} + Z_2^{-1}}$$

Example RL ~~par.~~ Series circuit (driven)

AMPAD

V_S

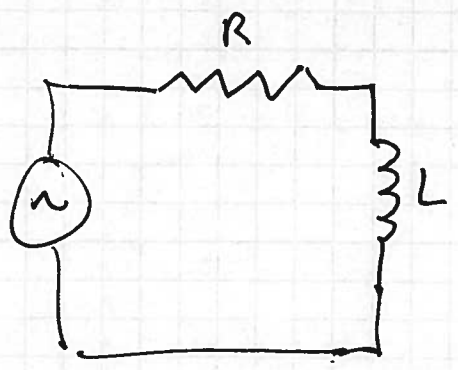

$$Z_{total} = Z_R + Z_L$$

$$Z_{total} = R + i\omega L$$

$$\therefore \vec{V}_S = \vec{I}_{total} Z_{total}$$

$$\vec{V}_S = \vec{I}_{total} (R + i\omega L)$$


∴ phase difference between \vec{V}_S & \vec{I}_{total} :

$$\delta = \text{phase of } (R + i\omega L) = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

∴ magnitude of current:

$$|\vec{I}_{total}| = I_0 = \frac{|\vec{V}_S| \leftarrow V_0}{|R + i\omega L|} = \frac{V_0}{\sqrt{R^2 + (\omega L)^2}}$$

Example RL parallel circuit (driven)

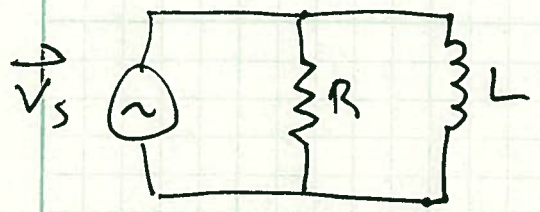


$$Z_{total} = \frac{1}{Z_R^{-1} + Z_L^{-1}}$$

$$= \frac{1}{R^{-1} + (i\omega L)^{-1}}$$

$$= \frac{(R\omega L) \times (\omega L + iR)}{(\omega L - iR) \times (\omega L + iR)}$$

$$= \left(\frac{R\omega L^2}{(\omega L)^2 + R^2} \right) (\omega + i\frac{R}{L})$$

or

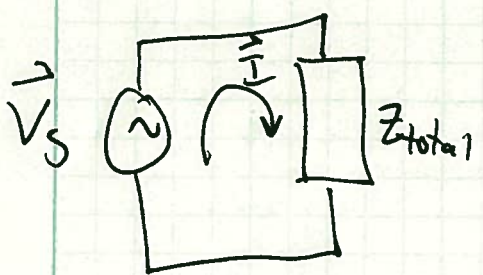

$$Z_{total} = \left(\frac{R\omega L^2}{(\omega L)^2 + R^2} \right) (\omega + i\tau)$$

$$\therefore \vec{V}_{s_{total}} = \vec{I}_{total} \left[\left(\frac{R\omega L^2}{(\omega L)^2 + R^2} \right) (\omega + i\tau) \right] \quad \text{where } \tau = \frac{R}{L}$$

Phase difference between \vec{V}_s & \vec{I}_{total} .

$$\delta = \tan^{-1}\left(\frac{\tau}{\omega}\right) \leftarrow \text{For very high } \omega, \delta \rightarrow \phi, \text{ like a resistor}$$

\leftarrow For very low ω , $\delta \rightarrow 90^\circ$, like an inductor.

Transients

We've studied the steady-state behavior of harmonic oscillators \Rightarrow how they behave once they settle down into a repeating pattern

Ex: Simple Harmonic Oscillator, no damping:

$$\ddot{x} + \omega_0^2 x = 0 \Rightarrow \text{Soln: } x(t) = A e^{i(\omega_0 t + \delta)},$$

A, δ determined by initial conditions

Ex: Simple Harmonic Oscillator with damping:

$$\ddot{x} + \gamma \dot{x} + \omega_0^2 x = 0 \Rightarrow \text{Soln: } x(t) = B e^{-\gamma/2 t} e^{i(\omega_d t + \delta_d)}$$

B, δ_d determined by initial conditions. (Also, to recover the no-damping case, just set $\gamma = 0$.)

$\omega_d = \sqrt{\omega_0^2 - \gamma^2/4}$

damped solution

Ex: Forced Oscillator with damping:

$$\ddot{x} + \gamma \dot{x} + \omega_0^2 x = \frac{F_0}{m} e^{i\omega_f t}$$

ω_f forcing frequency

$$\text{Solution: } x(t) = A e^{i(\omega_f t + \delta_f)}$$

forced solution

$\omega =$ forcing frequency

$$A(\omega_f) = \frac{F_0/m}{\sqrt{(\omega_0^2 - \omega_f^2)^2 + (\omega_f \gamma)^2}}, \quad \delta(\omega_f) = -\tan^{-1} \left[\frac{\omega_f \gamma}{(\omega_0^2 - \omega_f^2)} \right]$$

~~Why~~ Notes: Our forced oscillator solution has no free parameters. Why not? ~~Do~~ Do the initial conditions play no role in the solution?

Answer: The initial conditions ~~determine~~ ~~the~~ play a role in the short-term behavior, but their influence or effect dies out as time goes forward. Our solution is the long term behavior only.

⇒ The long-term behavior does not depend on the initial conditions.

⇒ The short term behavior does.

Question: How can we study the short term behavior of a forced oscillator?

Answer: ~~Notice that our Eq. of Motion is linear.~~

~~$$m\ddot{x} + \gamma\dot{x} + kx = \frac{F_0}{m} e^{i\omega t}$$~~

~~This means that if we find two different solutions, we can add them to get another solution:~~

~~Let ~~the~~ $x_{Ann}(t)$ be Ann's solution.~~

~~and $x_{Bob}(t)$ be Bob's solution.~~

Answer: Just add to our solution the related solution of a damped oscillator: (where $F_0 = 0$).

$$X(t) = X_F(t) + X_d(t)$$

$\underbrace{A(\omega_f) e^{i(\omega_f t + \delta_f)}}_{\text{long-term behavior, no free parameters}}$
 $+$
 $\underbrace{B e^{-\gamma t/2} e^{i(\omega_d t + \delta_d)}}_{\text{short-term behavior, 2 free parameters } B \text{ \& } \delta_d}$

forced solution

AMPAD

"Short term solution" = "complementary solution" or "complementary function"

"Long-term solution" = "particular solution" = "transient solution"

But does our solution work? Try it:

$$\ddot{X} + \gamma \dot{X} + \omega_0^2 X \stackrel{?}{=} \frac{F_0}{m} e^{i\omega t}$$

Substitute $X = X_F + X_d$

$$\left(\ddot{X}_F + \ddot{X}_d \right) + \gamma \left(\dot{X}_F + \dot{X}_d \right) + \omega_0^2 \left(X_F + X_d \right) \stackrel{?}{=} \frac{F_0}{m} e^{i\omega t}$$

$$\left(\ddot{X}_d + \gamma \dot{X}_d + \omega_0^2 X_d \right) + \left(\ddot{X}_F + \gamma \dot{X}_F + \omega_0^2 X_F \right) \stackrel{?}{=} \frac{F_0}{m} e^{i\omega t}$$

But by definition, X_d satisfies $\ddot{X}_d + \gamma \dot{X}_d + \omega_0^2 X_d = 0$

Therefore

$$\ddot{X}_F + \gamma \dot{X}_F + \omega_0^2 X_F \stackrel{?}{=} \frac{F_0}{m} e^{i\omega t}$$

Is this true?
Answer Yes! By definition

So our ~~equation~~ solution is

$$x(t) = A(\omega_f) e^{i(\omega_f t + \delta_f(\omega_f))} + B e^{-\gamma/2 t} e^{i(\omega_d t + \delta_d)}$$

and its real part is

$$x(t) = A(\omega_f) \cos(\omega_f t + \delta_f(\omega_f)) + B e^{-\gamma/2 t} \cos(\omega_d t + \delta_d)$$

where $A(\omega_f) = \frac{F_0/m}{\sqrt{(\omega_0^2 - \omega_f^2)^2 + (\omega_f \gamma)^2}}$, $\delta(\omega_f) = -\tan^{-1} \left(\frac{\omega_f \gamma}{\omega_0^2 - \omega_f^2} \right)$

$$\omega_d = \sqrt{\omega_0^2 - \gamma^2/4}$$

and B and δ_d are determined by initial conditions

In general ~~we~~ we can find B & δ_d to satisfy any initial conditions, and the result is usually very complicated in the short term.

In the long term, the damping term dies out due to the $(e^{-\gamma/2 t})$ factor, and we are left with the steady state solution.

Simple Special Case.

Suppose we start with $x = \phi$ and $\dot{x} = \dot{\phi}$ at $t = 0$, and we drive the oscillator at the resonant frequency: $\omega_f = \omega_0$.

Also, assume damping is very small, so $\omega_d \approx \omega_0$.

$$\omega_d = \sqrt{\omega_0^2 - \frac{r^2}{4}} \approx \omega_0$$

↑
assume
small
compared
to ω_0
(high Q
assumption)

Then the solution is

$$A(\omega_f) = A(\omega_0) = \frac{F_0}{m\omega_0 T}$$

$$\tan(\delta(\omega_f)) = \frac{-\omega_0 r}{\omega_0^2 - \omega_0^2} \rightarrow \infty, \text{ so } \delta_f(\omega_0) = -\pi/2$$

Also $\omega_d \approx \omega_0$

Then

$$x(t) = \frac{F_0}{m\omega_0 T} \underbrace{\cos(\omega_0 t - \pi/2)}_{\sin(\omega_0 t)} + B e^{-\gamma t/2} \cos(\omega_0 t + \delta_d)$$

$$x(t) = \frac{F_0}{m\omega_0 T} \sin(\omega_0 t) + B e^{-\gamma t/2} \cos(\omega_0 t + \delta_d)$$

$$x(t=0) = 0 = B e^{-\gamma t/2} \cos(\delta_d) \Rightarrow \delta_d = \pi/2$$

↑ initial condition

And

~~$$\dot{x}(t) = \frac{F_0}{mT} \cos(\omega_0 t) + B \left(\omega_0 \sin(\omega_0 t + \delta_d) - \frac{\gamma}{2} e^{-\gamma t/2} \cos(\omega_0 t + \delta_d) \right)$$

$$\dot{x}(t=0) = 0 = \frac{F_0}{mT} + B \left(-\omega_0 \sin(\delta_d) - \frac{\gamma}{2} \cos(\delta_d) \right)$$

Initial Condition~~

And

$$\dot{x}(t) = \frac{F_0}{m\gamma} \cos(\omega_0 t) + B (-\omega_0 \sin(\omega_0 t + \delta)) e^{-\gamma t/2} - \frac{B\gamma}{2} (\cos(\omega_0 t + \delta)) e^{-\gamma t/2}$$

$\begin{matrix} \pi/2 \\ \downarrow \\ \end{matrix}$
 $\begin{matrix} \uparrow \\ \pi/2 \end{matrix}$

initial condition \uparrow

$$\dot{x}(t=0) = 0 = \frac{F_0}{m\gamma} + B(-\omega_0 \sin(\pi/2)) - \frac{B\gamma}{2} (\cos(\pi/2))$$

$$0 = \frac{F_0}{m\gamma} - B\omega_0 \Rightarrow \boxed{B = \frac{F_0}{m\omega_0\gamma}}$$

Finally: When $\omega_f = \omega_0$, $\omega_d \approx \omega_0$, $x(t=0) = 0$ and $\dot{x}(t=0) = 0$


~~x(t)~~

$$x(t) = \frac{F_0}{m\omega_0\gamma} \sin(\omega_0 t) + \left(\frac{F_0}{m\omega_0\gamma}\right) e^{-\gamma t/2} \underbrace{\cos(\omega_0 t + \pi/2)}_{-\sin(\omega_0 t)}$$

$$\boxed{x(t) = \frac{F_0}{m\omega_0\gamma} (1 - e^{-\gamma t/2}) \sin(\omega_0 t)}$$

Special case:
 $\omega_f = \omega_0$
 $\omega_d \approx \omega_0$ ($\gamma \ll \omega_0$)
 $x = 0$ at $t = 0$
 $\dot{x} = 0$ at $t = 0$

What does it look like?

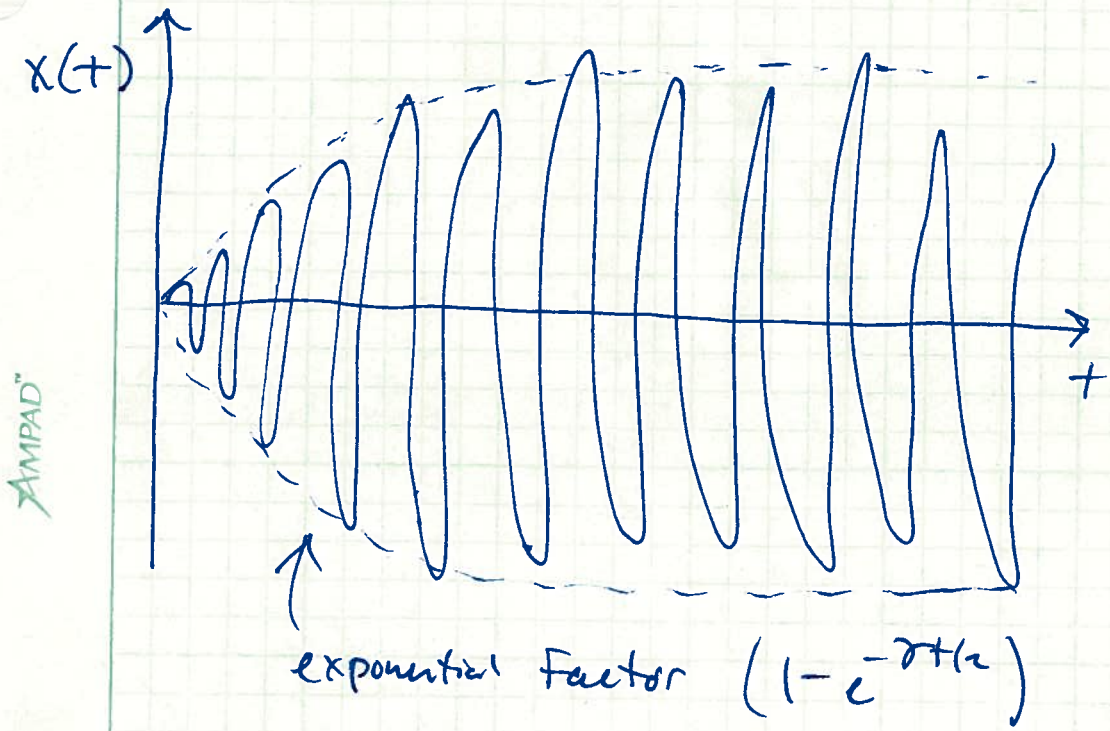

The amplitude increases then levels off to the steady state solution. This is like pushing a child on a swing in phase at the natural frequency of the swing.