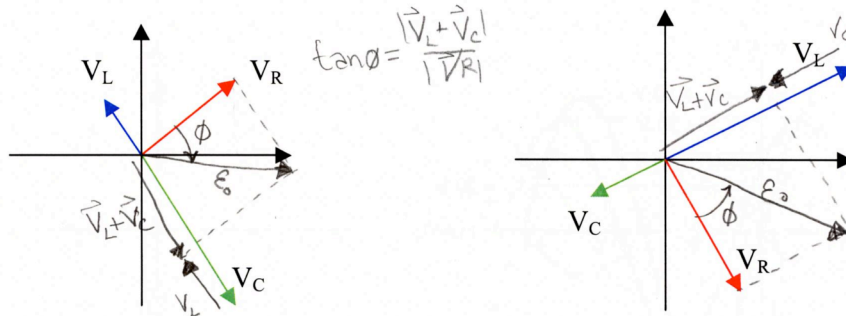




# Forced Oscillations

Name: \_\_\_\_\_

- Using the following phasor diagrams representing series RLC circuits, draw the vector representing the driving voltage and estimate the phase shift between the current and the driving voltage.



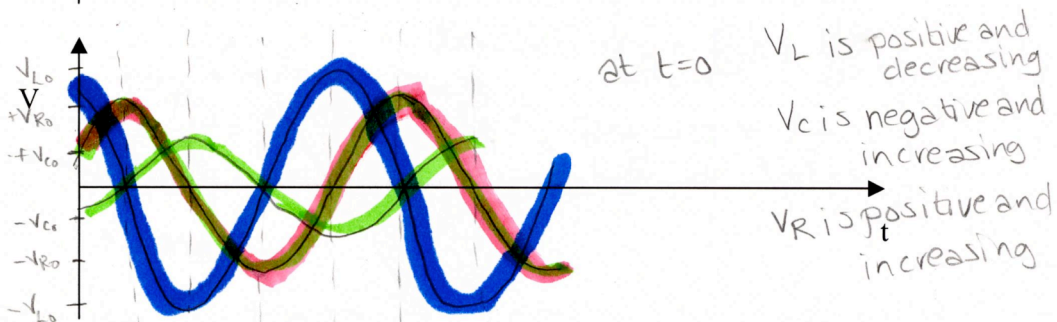
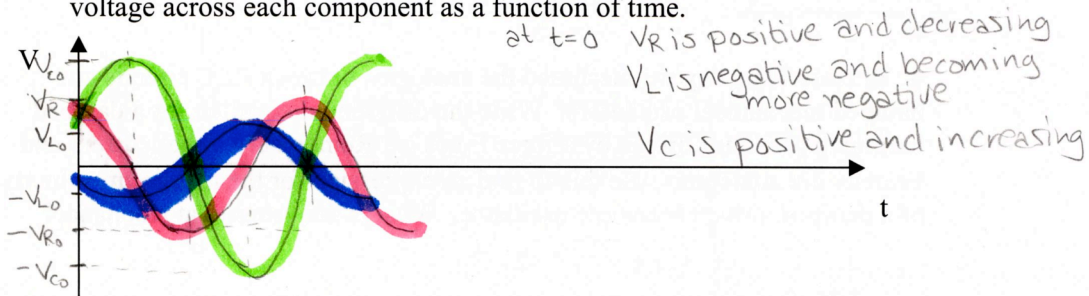
- Assuming the snapshots above were taken at  $t=0$ , for each circuit, draw the voltage across each component as a function of time.



- Qualitatively explain why there is a phase difference between the components in the circuit.

$V_R$  is proportional to  $I$   
 $V_L$  is proportional to  $dI/dt$  and is maximum when  $i=0$   
 $V_C$  is 180 out of phase with  $V_L$ . It also has a maximum absolute value when  $i=0$

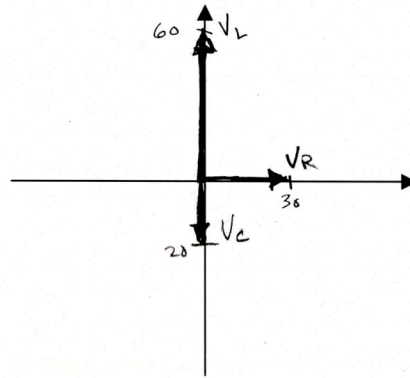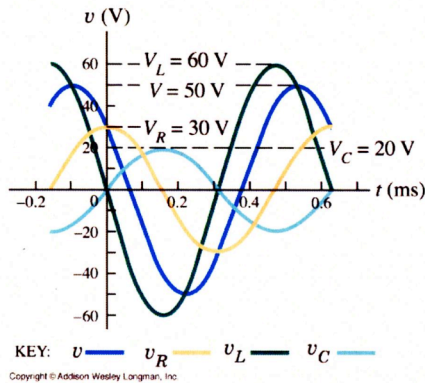3. Draw a phasor diagram representing the following circuit at time  $t=0$ .



4. In class Thursday we discussed the analogies between RLC circuits and damped mechanical oscillators. Write the differential equation for a damped harmonic oscillator driven by a force  $F_0 \cos \omega t$ . Remembering that current and velocity are analogous, use this to find an expression for the maximum velocity of a damped, driven harmonic oscillator. What is the velocity at resonance?

$$m \frac{d^2x}{dt^2} + f \frac{dx}{dt} + kx = F_0 \cos \omega t$$

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = \mathcal{E}_0 \cos \omega t$$

$$i = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\mathcal{E}_0 \rightarrow F_0$$

$$\frac{1}{C} \rightarrow k$$

$$R \rightarrow f$$

$$L \rightarrow m$$

$$\frac{dq}{dt} \rightarrow \frac{dx}{dt}$$

$$\frac{dx}{dt} = \frac{F_0}{\sqrt{f^2 + (\omega m - \frac{k}{\omega})^2}}$$

$$\text{at resonance } \omega = \omega_0 = \sqrt{\frac{k}{m}}$$

$$\begin{aligned} \frac{dx}{dt} \Big|_{\omega=\omega_0} &= \frac{F_0}{\sqrt{f^2 + (m\sqrt{\frac{k}{m}} - k\sqrt{\frac{m}{k}})^2}} \\ &= \frac{F_0}{\sqrt{f^2 + (\sqrt{mk} - \sqrt{mk})^2}} \end{aligned}$$

$$= \frac{F_0}{f}$$