

## Solution to Hw 5

1. a)  $V_R = Ri = RI_0 e^{-\alpha t} \cos \omega t$

$$V_L = L \frac{di}{dt} = -LI_0 e^{-\alpha t} (\alpha \cos \omega t + \omega \sin \omega t)$$



$$V_{RL} = V_R + V_L = I_0 e^{-\alpha t} [(R - L\alpha) \cos \omega t - L\omega \sin \omega t]$$

$$= V_0 e^{-\alpha t} \cos(\omega t + \theta)$$

Where  $V_0 = I_0 \sqrt{(R - L\alpha)^2 + L^2 \omega^2}$  and  $\theta = \tan^{-1} [L\omega / (R - L\alpha)]$

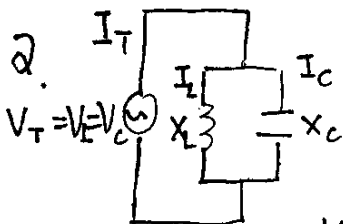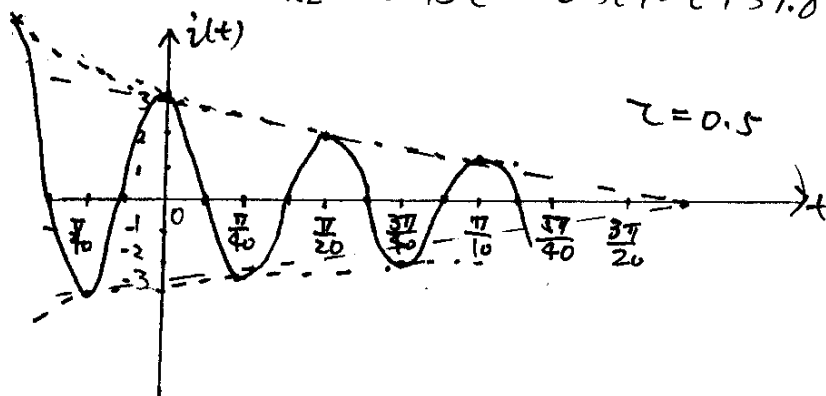b) Plug in the data,  $V_0 = 18.75V$ ,  $\theta = 39.8^\circ$

$$\therefore i = 3e^{-2t} \cos 40t \quad V_{RL} = 18.75e^{-2t} \cos(40t + 39.8^\circ)$$



In the pure LC parallel-tuned circuit (that is, one in which there is no resistance), the coil and the capacitor are placed in parallel and the applied voltage  $V_T$  appears across these circuit components. In this parallel-tuned circuit, as in the series-tuned circuit, resonance occurs when the inductive reactance is equal to the capacitive reactance.

$$X_L = X_C$$