

Because the applied voltage is common to both branches,

$$V_L = V_C$$

So that $\frac{V_L}{X_L} = \frac{V_C}{X_C}$, $I_L = I_C$.


and I_L lags the applied V_T 90° while I_C leads by 90° , so their phase difference is 180° , therefore, I_L and I_C vector sum is zero, \therefore total current $I_T = 0$. Under this condition, the impedance of circuit at the resonant frequency must be infinite in value.

The formula for the resonant frequency of a pure LC parallel-tuned circuit is the same as that for a series tuned circuit

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{0.159}{\sqrt{LC}}$$

$$\therefore L = \frac{0.0254}{f_r^2 C}$$

$$C = \frac{0.0254}{f_r^2 L}$$

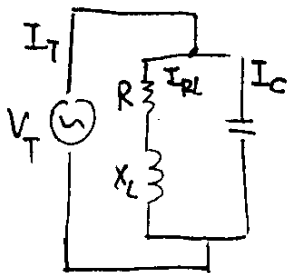

In a practical LC parallel-tuned circuit, there's some resistance, most of which is due to the resistance of the inductor wire. The resonant frequency of a parallel circuit also is defined as that frequency at which the parallel circuit acts as a pure resistance, therefore, the line current I_T must be in phase with the ~~parallel circuit~~ applied V_T . This means that the out of phase or quadrature component of the current