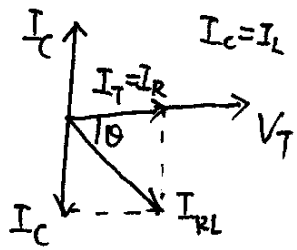


through the inductive branch I_L must be equal to the current through the capacitive branch I_C ; and the total line current I_T equals the in phase component of the current through the inductive branch, or $I_T = I_R$, since the impedance is maximum, I_T is minimum.



The resonant frequency for the circuit is

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

where f_r = resonant frequency, Hz
 L = inductance, H
 C = capacitance, F
 R = resistance, Ω .

If Q of the coil is high, say greater than 10, or $1/LC \gg R^2/L^2$, then R^2/L^2 can be disregarded.

$$\therefore f_r \approx \frac{1}{2\pi\sqrt{LC}}$$

total impedance $Z_T = L/RC$

3. The system given has two degrees of freedom, and therefore, it also has two characteristic frequencies of vibration.

Assume: $x_1(t) = A e^{i\omega t}$ $x_2(t) = B e^{i\omega t}$.

$$\therefore \dot{x}_1 = A i \omega e^{i\omega t}$$

$$\ddot{x}_1 = -A \omega^2 e^{i\omega t}$$

$$\dot{x}_2 = B i \omega e^{i\omega t}$$

$$\ddot{x}_2 = -B \omega^2 e^{i\omega t}$$

$$\left. \begin{array}{l} \dot{x}_1 = A i \omega e^{i\omega t} \\ \dot{x}_2 = B i \omega e^{i\omega t} \end{array} \right\} \Rightarrow \begin{array}{l} (-A \omega^2 m + b A i \omega + (k + k_c) A + k_c B) e^{i\omega t} \\ (-B \omega^2 m + b B i \omega + (k + k_c) B + k_c A) e^{i\omega t} \end{array}$$