

Solutions to hw 4

1) my numbers: $N=100$, $d=10\text{ mm}$, $l=9\text{ cm}$, $\mu_m=650/\mu_0$

a) $L = \mu_0 N^2 \frac{A}{l} = 11\text{ }\mu\text{H}$

b) $\mu_m = 650/\mu_0 \Rightarrow L = 7.13\text{ mH}$

2) my numbers: $\mathcal{E}=6\text{ V}$, $L=9.0\text{ mH}$, $R=4.0\text{ }\Omega$

a) $\tau = \frac{L}{R} = 2.25\text{ ms}$

b) $I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$, $t=250\text{ }\mu\text{s} \Rightarrow I=0.1577\text{ A}$


c) $t \rightarrow \infty \Rightarrow I \rightarrow \frac{\mathcal{E}}{R} = 1.5\text{ A}$

d) $f = 1 - e^{-t/\tau} \Rightarrow t = -\tau \ln(1-f)$; $f=0.8 \Rightarrow t=3.62\text{ ms}$

3) my numbers: $\mathcal{E}=12.5\text{ V}$, $R_1=1200\text{ }\Omega$, $R_2=12.0\text{ }\Omega$, $L=2.0\text{ H}$

a) $I \rightarrow \frac{\mathcal{E}}{R_2} = 1.04\text{ A}$

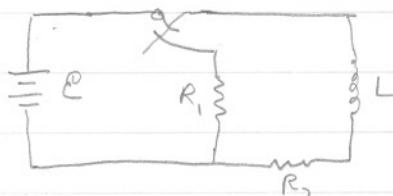b) $I R_2 = 12.5\text{ V}$ } $\Delta V_L = 1262.5\text{ V}$
 $I R_1 = 1.25\text{ kV}$



c) $\tau = \frac{L}{R_1 + R_2} = 1.65\text{ ms}$

$e^{-t/\tau} = \frac{12.5}{1262.5} \Rightarrow t=7.26\text{ ms}$

4a) $U = 4\pi \int_R^\infty r dr \frac{B^2}{2\mu_0} \quad , \quad B = B_0 \left(\frac{R}{r}\right)^2 \Rightarrow U = \frac{2\pi}{\mu_0} B_0^2 R^3$

b) $B_0 = 5.2 \times 10^{-5}\text{ T}$, $R = 6.4 \times 10^6\text{ m} \Rightarrow U = 3.54 \times 10^{18}\text{ J}$

5) my numbers: $R=110\text{ }\Omega$, $L=250\text{ mH}$, $C=2.0\text{ }\mu\text{F}$, $\Delta V_{\max}=210\text{ V}$, $f=50\text{ Hz}$

a) $X_L = \omega L = 78.5\text{ }\Omega$ $\omega = 2\pi f$

b) $X_C = \frac{1}{\omega C} = 1.59\text{ k}\Omega$

c) $Z = (R^2 + (X_L - X_C)^2)^{1/2} = 1.52\text{ k}\Omega$

d) $I_{\max} = \frac{V_{\max}}{Z} = 138\text{ mA}$

e) $\phi = \tan^{-1} \frac{X_L - X_C}{R} = -85.8^\circ$


my numbers: $V_{rms} = 5000 \text{ V}$, $C_s = 23 \mu\text{F}$, $R_b = 40 \Omega$, $f = 60 \text{ Hz}$

$$Z = (R^2 + X_c^2)^{1/2} \quad Z = 1.15 \times 10^8 \Omega$$

$$X_c = \frac{1}{\omega C}$$

$$I_{rms} = \frac{V_{rms}}{Z} = 4.335 \times 10^{-5} \text{ A}$$

$$V_b = I_{rms} R_b = 1.73 \text{ V}$$

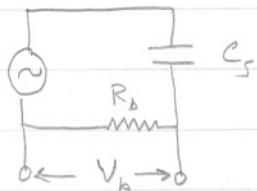

my numbers: $E_{rms} = 120 \text{ V}$, $f = 60 \text{ Hz}$, $L = 28 \text{ mH}$, $R = 20 \Omega$

a) $Z = (R^2 + X_L^2)^{1/2}$, $X_L = \omega L \Rightarrow Z = 22.6 \Omega \quad I_{rms} = \frac{E_{rms}}{Z} = 5.31 \text{ A}$

b) $\cos \phi = \frac{R}{Z} = 0.884$

c) need $X_L = X_C \Rightarrow \frac{1}{\omega C} = \omega L \Rightarrow C = \frac{1}{\omega^2 L} = 251.2 \mu\text{F}$

d) $E \Rightarrow E \cos \phi = 106 \text{ V}$

my numbers: $L = 20 \text{ mH}$, $C = 90 \mu\text{F}$, $R = 10 \Omega$, $\Delta V_{max} = 100 \text{ V}$

a) $\omega_0 = \sqrt{\frac{1}{LC}} = 2.357 \times 10^4 \text{ rad/s} = 2\pi f \Rightarrow f = 3.75 \text{ kHz}$

b) $\omega = \omega_0 \Rightarrow Z = R \Rightarrow I_{max} = \frac{V_{max}}{R} = 10 \text{ A}$

c) $Q = \frac{\omega}{\Delta \omega} = \omega_0 \frac{L}{R} = 47.1$

d) $Z_L = \omega L \Rightarrow \Delta V_L = \omega L I_{max} = V_{max} \frac{\omega L}{Z}$

$\omega = \omega_0 \Rightarrow Z = R \Rightarrow \Delta V_L = V_{max} \frac{\omega_0 L}{R} = 4.71 \text{ kV}$