**35.10.**  $I_d > I_c = I_e > I_b > I_a$ . The intensity passing through a polarizer is  $I_0 \cos^2 \theta$ . Polarizer *d* is aligned with the incident wave ( $\theta = 0$ ) while  $\theta = 90^\circ$  for polarizer *a*. Polarizers *c* and *e* are at the same angle  $\theta$  from the vertical.

**35.27.** Model: Use Malus's law for polarized light. Visualize:



**Solve:** For unpolarized light, the electric field vector varies randomly through all possible values of  $\theta$ . Because the *average* value of  $\cos^2 \theta$  is  $\frac{1}{2}$ , the intensity transmitted by a polarizing filter is  $I_{\text{transmitted}} = \frac{1}{2}I_0$ . On the other hand, for polarized light  $I_{\text{transmitted}} = I_0 \cos^2 \theta$ . Therefore,

 $I_{\text{transmitted } 2} = I_{\text{transmitted } 1} \cos^2 \theta = \frac{1}{2} I_0 \cos^2 \theta = \frac{1}{2} (350 \text{ W/m}^2) \cos^2 30^\circ = 131 \text{ W/m}^2$ 

Assess: Note that any particular *wave* has a clear polarization. It is only in a "sea" of waves that the resultant wave has no polarization.

**36.2.** (a) 1.0 A. Use 
$$I_R = \frac{V_R}{R}$$
.  
(b) 4.0 A. Use  $I_R = \frac{V_R}{R} = \frac{\varepsilon_0}{R}$ .  
(c) 2.0 A.  $I_R$  is not dependent on the frequency.

**36.3.** (a) 4.0 A. Use  $I_c = \omega C \varepsilon_0$  for all parts of this question. (b) 4.0 A (c) 4.0 A **36.5.** (a)  $I_L = 1.0$  A. Use  $I_L = \frac{V_L}{X_L} = \frac{\varepsilon_0}{\omega L}$  for all parts of this question. (b)  $I_L = 4.0$  A (c)  $I_L = 1.0$  A **36.6.** (a) 1000 Hz. Use  $\omega_0 = \frac{1}{\sqrt{LC}}$ . Resistance does not matter. (b)  $\frac{1}{\sqrt{2}}$  1000 Hz = 707 Hz (c)  $\frac{1}{\sqrt{2}}$  1000 Hz = 707 Hz (d) 1000 Hz. Peak emf does not matter. **36.8.** The current lags the emf. The phase angle  $\phi > 0$  and  $X_L > X_C$ .

**36.2.** Model: A phasor is a vector that rotates counterclockwise around the origin at angular frequency  $\omega$ . Solve: (a) Referring to the phasor in Figure EX36.2, the phase angle is

$$\omega t = 135^\circ = 135^\circ \times \frac{\pi \text{ rad}}{180^\circ} = \frac{3\pi}{4} \text{ rad} \Rightarrow \omega = \frac{3\pi/4}{2.0 \text{ ms}} = 1178 \text{ rad/s}$$

(b) From Figure EX36.2,

$$\mathcal{E} = \mathcal{E}_0 \cos \omega t \Longrightarrow \mathcal{E}_0 = \frac{\mathcal{E}}{\cos \omega t} = \frac{50 \text{ V}}{\cos(3\pi/4 \text{ rad})} = -71 \text{ V}$$

**36.9.** Visualize: Figure EX36.7 shows a simple one-capacitor circuit. Solve: (a) From Equation 36.11,

$$I_{\rm C} = \frac{V_{\rm C}}{X_{\rm C}} = \frac{V_{\rm C}}{1/\omega C} = \omega C V_{\rm C} = 2\pi f C V_{\rm C} \Rightarrow f = \frac{50 \times 10^{-3} \text{ A}}{2\pi (5.0 \text{ V}) (20 \times 10^{-9} \text{ F})} = 80 \text{ kHz}$$

(b) The AC current through a capacitor *leads* the capacitor voltage by 90° or  $\pi/2$  rad. For a simple one-capacitor circuit  $i_{\rm C} = I_{\rm C} \cos(\omega t + \frac{1}{2}\pi)$ . For  $i_{\rm C} = I_{\rm C}$ ,  $(\omega t + \frac{1}{2}\pi)$  must be equal to  $2n\pi$ , where n = 1, 2, ... This means

$$\omega t = \frac{3\pi}{2}, \frac{7\pi}{2}, \frac{11\pi}{2}, \dots$$

At these values of  $\omega t$ ,  $v_c = V_c \cos(\omega t) = 0$  V. That is,  $i_c$  is maximum when  $v_c = 0$  V.

**36.11. Solve:** (a) From Equation 36.11,

$$I_c = \frac{V_c}{X_c} = \frac{V_c}{1/\omega C} = \omega C V_c = 2\pi f C V_c$$
$$\Rightarrow C = \frac{I_c}{2\pi f V_c} = \frac{(330 \times 10^{-6} \text{ A})}{2\pi (250 \times 10^3 \text{ Hz})(2.2 \text{ V})} = 9.5 \times 10^{-11} \text{ C} = 95 \text{ pC}$$

(b) Doubling the frequency will halve the capacitive reactance  $X_c$ , doubling the current, so  $I_c = 2$  (330  $\mu$ A) = 660  $\mu$ A.

**36.12.** Model: The current and voltage of a resistor are in phase, but the capacitor current leads the capacitor voltage by 90°.

Solve: For an RC circuit, the peak voltages are related through Equation 36.12. We have

$$\mathcal{E}_0^2 = V_R^2 + V_C^2 \Longrightarrow V_R = \sqrt{\mathcal{E}_0^2 - V_C^2} = \sqrt{(10.0 \text{ V})^2 - (6.0 \text{ V})^2} = 8.0 \text{ V}$$

**36.22. Model:** The AC current through an inductor lags the inductor voltage by 90°. **Solve:** (a) From Equation 36.21,

$$I_L = 330\mu A = \frac{V_L}{X_L} = \frac{V_L}{2\pi fL}$$
$$\Rightarrow L = \frac{2.2 \text{ V}}{2\pi (45 \times 10^6 \text{ Hz})(330 \times 10^{-6} \text{ A})} = 2.4 \times 10^{-5} \text{ H} = 24 \ \mu\text{H}$$

(b) Doubling the frequency will double the inductive reactance and halve the current, so

$$I_L = \frac{330\mu A}{2} = 165\mu A$$

**36.23.** Solve: (a) When the resistance is doubled, the resonance frequency stays the same because f is independent of R. Hence, f = 200 kHz. (b) From Equation 36.30,

$$f = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

When the capacitor value is doubled,

$$f' = \frac{1}{2\pi} \frac{1}{\sqrt{L(2C)}} = \frac{f}{\sqrt{2}} = \frac{200 \text{ kHz}}{\sqrt{2}} = 141 \text{ kHz}$$

**36.25.** Model: At the resonance frequency, the current in a series RLC circuit is a maximum. The resistor does not affect the resonance frequency. **Solve:** From Equation 36.30,

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \implies C = \frac{1}{4\pi^2 f^2 L} = \frac{1}{4\pi^2 (1000 \text{ Hz})^2 (20 \times 10^{-3} \text{ H})} = 1.27 \times 10^{-6} \text{ F} = 1.27 \ \mu\text{F}$$

**36.35. Solve:** (a) From Equation 36.14,

$$V_{\rm R} = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + (\omega_{\rm cap} C)^{-2}}} = \frac{\mathcal{E}_0}{2} \Longrightarrow R^2 + \frac{1}{\omega_{\rm res}^2 C^2} = 4R^2 \Longrightarrow \omega_{\rm res} = \frac{1}{\sqrt{3}RC}$$

(b) At this frequency,

$$V_{\rm C} = IX_{\rm C} = \frac{V_{\rm R}}{R} \left(\frac{1}{\omega_{\rm res}C}\right) = \frac{\left(\mathcal{E}_0/2\right)}{R} \left(\sqrt{3}RC\right) \frac{1}{C} = \frac{\sqrt{3}}{2}\mathcal{E}_0$$

(c) The crossover frequency is

$$\omega_{\rm c} = \frac{1}{RC} = 6280 \text{ rad/s} \implies \omega_{\rm res} = \omega_{\rm c} / \sqrt{3} = 3630 \text{ rad/s}$$

**36.39.** Visualize: Please refer to Figure 36.13. Solve: For an RC filter,  $I = \mathcal{E}_0 / \sqrt{R^2 + X_c^2}$  and

$$V_{\rm R} = IR = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + (1/\omega C)^2}} \qquad V_{\rm C} = IX_{\rm C} = \frac{\mathcal{E}_0 X_{\rm C}}{\sqrt{R^2 + (1/\omega C)^2}}$$

At the crossover frequency  $\omega = \omega_c = 1/RC$  and thus  $1/\omega_c C = R$ . Hence,

$$V_{\rm R} = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + R^2}} = \frac{\mathcal{E}_0}{\sqrt{2}} \qquad V_{\rm C} = \frac{\mathcal{E}_0 (1/\omega C)}{\sqrt{R^2 + (1/\omega C)^2}} = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + R^2}} = \frac{\mathcal{E}_0}{\sqrt{2}}$$