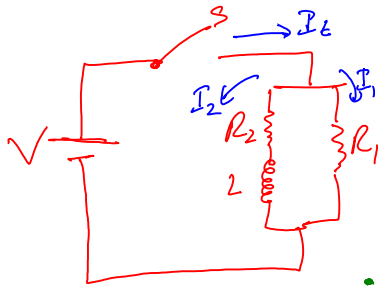


RL Circuit Example

Friday, September 25, 2009
1:06 AM

Switch is closed at $t=0$ seconds, Find the current through the battery as a function of time:



@ $t=0$, Switch is closed.
Find the current through the battery as a function of time:

$$V = I_1 R_1, \quad V = I_2 R_2 + L \frac{dI_2}{dt} \quad \text{--- ①}$$

$$\text{or } I_t = I_1 + I_2$$

$$\therefore I_t = \frac{V}{R_1} + I_2 \Rightarrow I_2 = I_t - \frac{V}{R_1} \quad \text{--- ②}$$

Solve these 3 equations for $I_t(t)$.
Also, apply boundary conditions @ $t \rightarrow 0$

$\therefore$ using equation ① + ②

$$V = \left(I_t - \frac{V}{R_1}\right) R_2 + L \frac{d}{dt} \left(I_t - \frac{V}{R_1}\right)$$

$$\frac{V}{R_2} = I_t - \frac{V}{R_1} + \frac{L}{R_2} \frac{dI_t}{dt}$$

The rest is math, solving for $I_t(t)$

$$\Rightarrow \frac{R_2}{L} \left[\frac{V}{R_2} - I_t + \frac{V}{R_1} \right] = \frac{dI_t}{dt}$$

$$\Rightarrow \frac{R_2}{L} V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{R_2}{L} I_t = \frac{dI_t}{dt}$$

$\tau = C$ a constant

$$I_t - I' = C - \frac{R_2}{L} I_t \Rightarrow \frac{dI'}{dt} = \frac{R_2}{L} \frac{dI_2}{dt}$$

$$\therefore -I' = \frac{L}{R_2} \frac{dI'}{dt} \Rightarrow -\frac{R_2}{L} dt = \frac{dI'}{I'}$$

$$\text{integrate } \Rightarrow \ln I' \Big|_{I_0'} = -\frac{R_2}{L} t$$

$$\text{Let } \tau \equiv L/R_2$$

$$\Rightarrow I' = I_0' e^{-t/\tau}$$

no current through inductor @ $t=0$

$$\text{Boundary Conditions: @ } t=0 \quad I_t = I_1 = \frac{V}{R_1} \Rightarrow I_0' = -C + \frac{R_2}{L} \frac{V}{R_1}$$

$$\therefore -C + \frac{I_t}{\tau} = \left(C + \frac{R_2}{R_1} \frac{V}{L} \right) e^{-t/\tau}$$

$$I_t(t) = \tau C (1 - e^{-t/\tau}) + \frac{R_2 V}{L} \frac{\tau}{R_1} e^{-t/\tau}; \quad \tau = \frac{L}{R_2}, \quad C = \frac{R_2 V}{L} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$I_t(t) = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) (1 - e^{-t/\tau}) + \frac{V}{R_1} e^{-t/\tau}$$

$$I_t(t) = \frac{V}{R_1} + \frac{V}{R_2} (1 - e^{-t/\tau})$$

$$\text{@ } t=0, I_b(t) = V/R_1 \quad \checkmark$$

$$\text{@ } t \rightarrow \infty, I_b(t) = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

This makes sense because

as $t \rightarrow \infty$, current is steady & inductor can be ignored

$$\Rightarrow I_b = \frac{V}{R_{eq}}, \quad \frac{1}{R_{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow I_b = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \quad \checkmark$$