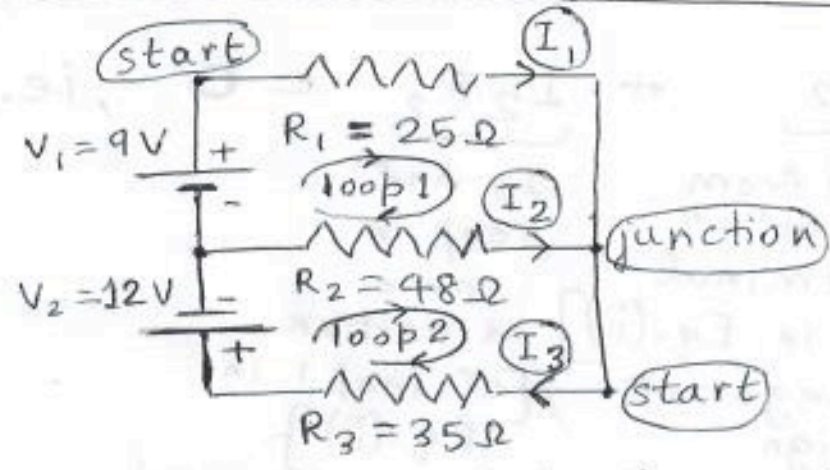


Kirchhoff's rules problem



Follow the recipe/strategy given in HW 7 and with #28 of Wed. session: i.e., part between 2 junctions

step (1): label current in each branch ($I_1, 2, 3$ above), choosing direction for each "randomly" (e.g. $I_1, 2$ are "to right" vs. I_3 "to left")

step (2): apply junction rule (at point marked):
 $I_1 + I_2$ (sum of incoming) = I_3 (outgoing) ... (i)

step (3): apply voltage rule to loops shown [we choose both directions to be clockwise just for simplicity: in general, directions could be different for each loop and loop direction is chosen independently of ^{the} currents in step (1)]:

loop 1 ("starting" at top left):

$$\underbrace{-I_1 R_1}_{\substack{I_1 \text{ to right} \\ \text{loop going to} \\ \text{right} \Rightarrow \\ \text{negative sign}}} + \underbrace{I_2 R_2}_{\substack{I_2 \text{ to right,} \\ \text{but loop going} \\ \text{to left} \\ \Rightarrow \text{positive sign.} \\ \text{(opposite directions)}}} + \underbrace{V_1}_{\substack{\text{loop going from} \\ \text{"-" to "+"} \\ \text{terminal} \Rightarrow \\ \text{positive sign}}} = 0, \text{ i.e.,}$$

$$-I_1 25\Omega + I_2 48\Omega + 9V = 0 \dots (ii)$$

loop 2 ("starting" at bottom right) : → any choice is ok

$$\underbrace{-I_3 R_3}_{I_3 \text{ \& loop same direction}} - \underbrace{V_2}_{\substack{\text{loop from} \\ \text{"+" to "-" \\ \text{terminal} \\ \text{[cf. in Eq. (ii)]} \\ \Rightarrow \text{negative sign}}} = \underbrace{I_2 R_2}_{\substack{I_2 \text{ and} \\ \text{loop in} \\ \text{same} \\ \text{direction} \\ \text{[cf. loop 1 in} \\ \text{Eq. (ii)]}}} = 0, \text{ i.e.,}$$

$$-I_3 35 \Omega - 12V - I_2 48 \Omega = 0 \dots \text{(iii)}$$

step (4) : We do have as many equations as unknowns here, i.e., Eqs (i)-(iii) for $I_{1,2,3}$ so that we do not need to apply rules further.

step (5) Solve Eqs (i)-(iii), e.g., Eq. (ii) gives

$$I_1 = (9V + 48 I_2) / (25 \Omega) \dots \text{(iv)}$$

Plugging I_1 from Eq. (iv) and I_3 from Eq. (i) into Eq. (iii) gives

$$-48 I_2 - 12V - 35 \Omega \left[I_2 + \underbrace{\left(\frac{9V + 48 I_2}{25 \Omega} \right)}_{I_3} \right] = 0$$

(after bit of algebra!)

$$\text{or } \boxed{I_2 = -\frac{123}{751} \text{ A}} = \boxed{0.164 \text{ A}}, \text{ but to left (due to negative sign)}$$

Plugging above value of I_2 in Eq. (iv) gives

$$I_1 = 0.0455 \text{ A (i.e., to right)}$$

and plugging values of $I_1, 2$ in Eq. (i) gives $I_3 = -0.118 \text{ A}$ (i.e., to right)

$$\left[\text{Check with overall loop: } -I_1 R_1 - R_3 I_3 - V_2 + V_1 \stackrel{?}{=} 0 \right]$$

$$(\text{in V}) - 0.0455 \times 25 + 35 \times 0.118 - 12 + 9 \stackrel{\checkmark}{=} 0$$