 


# Traffic controller



circuit will have 2 input (clock, enable)  
3 outputs (R,G,B lines for lights)

module TRAFFIC(  
input clk,ena,

output reg R,G,Y);

no need for wire here, it's  
the default

can put type declaration here

need 3 timers. Let's assume clk has  $f=1\text{kHz}$   
so period  $T=1\text{ms}$

want G,R lights on for 30s

$Y = "1100" \cdot 2\text{s}$

for GR, 30s at 1us/tick = 30k ticks

need register that can count to 30k

for 15 bits,  $2^{15} = 32768$

for Y, 2s  $\Rightarrow$  2k ticks so need 11 bits:  $2^{11} = 2048$

decimal 30,000 = Hex 7530  $\Rightarrow$  15'h7530

decimal 2,000 = Hex 7D00  $\Rightarrow$  11'h7D00

Counters:  
#bits 'h  $\Rightarrow$  hex  
'd  $\Rightarrow$  decimal

reg [14:0] rT, gT;

reg [10:0] yT;

then a done line for each timer

wire rD, gD, yD;

parenthese optional

assign rD = (rT == 'd30000);

assign gD = (gT == 'd30000);

assign yD = (yT == 'd2000);

counters

always @ (posedge clk) begin

if (R) rT <= rT + 1;

else rT <= 0; (don't need 'd0000)

if (G) gT <= gT + 1;

```

else  $gT \leq 0;$ 
if (Y)  $yT \leq yT + 1;$ 
else  $yT \leq 0;$ 
end

```

next comes state machine

$\Rightarrow$  3 states RED, GREEN, YELLOW

parameter [1:0]  $\underbrace{\text{RED}=0, \text{GREEN}=1, \text{YELLOW}=2}$ ;

2 bits to hold numbers 0, 1, 2

FSM has 3 states so need 2-bit state bus

reg [1:0] state;

always @ (posedge clk) begin

if (ena) begin

case (state)

RED: begin

R <= 1;


G <= 0;

Y <= 0;

} specify every output  
reg!

{ if (rD) state <= GREEN;  
else state 2 = state;

end

 

GREEN: begin

R <= 0;

G <= 1;

Y <= 0;

if (gD) state <= YELLOW;

else state <= GREEN

end

YELLOW: begin

R <= 0;

G <= 0;

Y <= 1;

if (yD) state <= RED;

else state <= YELLOW;

end

end <sup>end</sup>      ← ends if (end) begin

else begin

R <= 1;

← turns on red light

G <= 0;

note when end is asserted,  
red counter has been  
counting so will go to  
red state for unknown  
time, prob or

Y <= 0;

state <= RED;

end case      ← ends case switching

end      ← ends always @ ... begin

## Reset

above we used clear signal

we could also use a reset signal that puts FSM into determined state

2 types of reset: synchronous } with respect  
asynchronous } to clock

### synchronous

```
always @ (posedge clk) begin
```

```
    if (reset) begin ← only @ posedge clk &  
        state <= RED;           will effect FSM
```

```
R <= 1;
```

```
G <= 0;
```

```
Y <= 0;
```

```
end
```

synchronous w/clk

```
else begin
```

```
    case (state)
```

```
    :
```

```
end case
```

```
end
```

asynchronous

always @ (posedge clk or posedge reset)

;

not synched w/ clock!