

A "test bench" is a verilog program that can drive a verilog (or any) circuit, simulating the inputs to that circuit to test the response


Response:

1. "functional" - test the logic
2. timing - to make sure things happen when they should

#1 is easy

#2 is only as good as the ability to simulate actual timing

ex circuit to test:

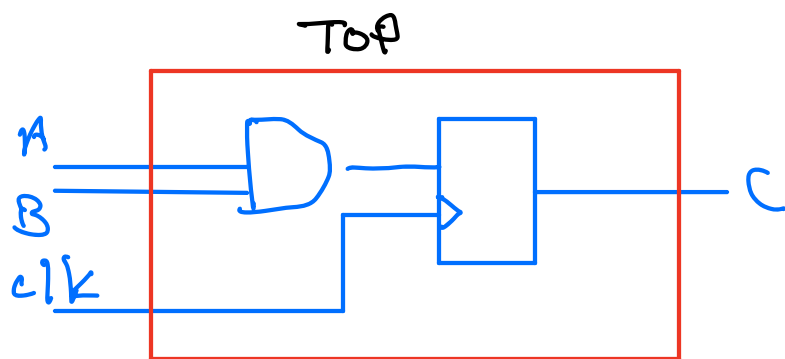

verilog code:

```
module top (
    input A, B, clk,
    output reg C);
```

```
wire d = A & B;  
always @ (posedge clk) C <= d;  
endmodule
```

verilog test bench:

```
'timescale 1ns/1ps  
module top_tb;
```

```
'timescale a/b
```

( ' = backquote, no ; at end )

a  $\equiv$  time unit  
b  $\equiv$  precision

time units are used w/ # sign in verilog to add a delay

```
ex: 'timescale 1ns/1ps  
a = 0;  
#1 a = 1;  
#5 a = 0;
```

- this means
1. set a = 0
  2. wait 1 "tick" (1ns) and then set a = 1
  3. wait 5ns and set a = 0

Next: we need to define inputs & outputs to the circuit

circuit inputs:  $A, B, clk$

we need to drive these from the testbench so they will be reg's

$reg\ a, b, clock;$   $\neq$  names do not have to match!

circuit outputs:  $C$

the testbench looks at  $C$  which is driven by the circuit

$wire\ c;$

now we instantiate the circuit:

$top\ MYTOP (.A(a), .B(b), clk(clock),$   
 $.C(c));$

↑↑  
circuit module

↑↑  
instantiation  
name (any thing!)

now we need to drive the inputs  
lets say we want a 1kHz clock

⇒ period is  $1\text{ms} = 10^6\text{ns}$  or  $10^6$  ticks

always begin

clock = 0;

# 500000 clock = 1;

# 500000 ;

end

start at  $\phi$

set to 1 after  $\frac{1}{2}\text{ms}$

wait  $\frac{1}{2}\text{ms}$

repeat forever

now we have to specify A, B inputs

initial begin

a = 0;


b = 0;

# 5000000 a = 1; after 5  $\mu\text{s}$ , set a = 1

# 2000000 b = 1; after 2  $\mu\text{s}$ , set b = 1

end

so input looks like this

 

then you should see C do this



↑  
posedge  
clock

