
 



Application of SR latch:

Simple analog circuit to turn on a load

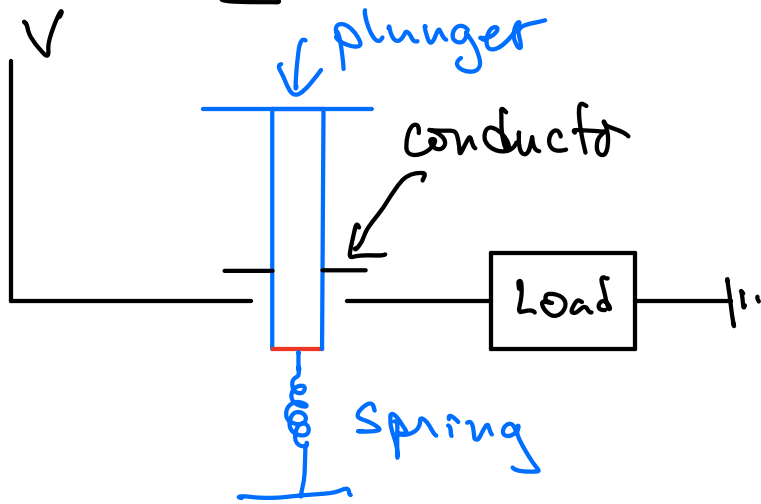


press plunger, current flows from source V to ground through load

plot V across load V_L vs time

 


 blow up edges \rightarrow always see "bouncing"



too much coffee !!

solution: use RS latch

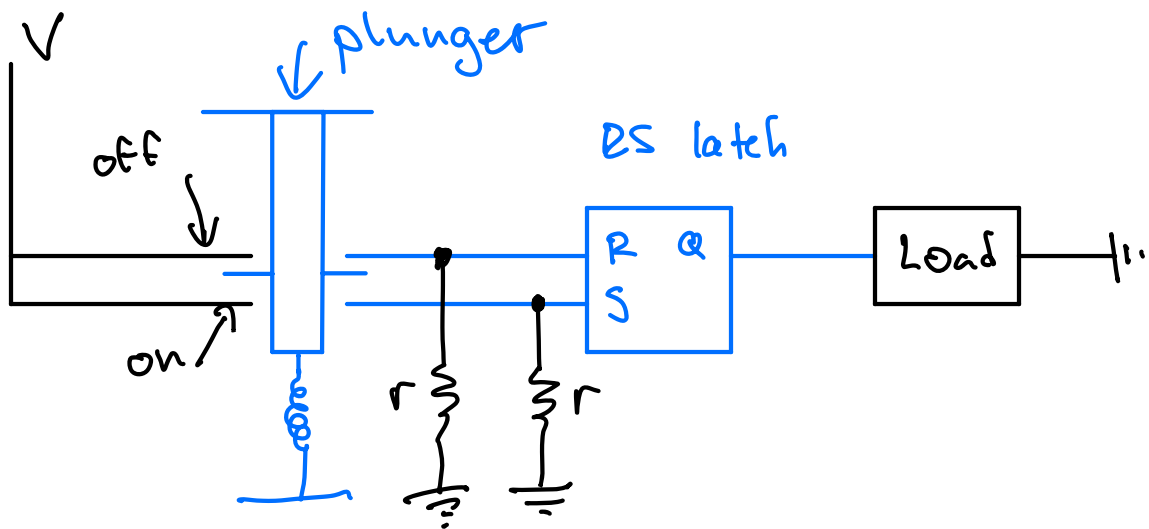


push down turns Q on, release and Q → 0
 bouncing will be "forgotten" due to latching



Note: pull-down resistors set EM voltage levels to 0
 when not active so that R & S are well-defined
 Value for r should be $r \gg R_{LOAD}$ so very little
 current is diverted before latch

Gated R-S latch

 control when R-S is active: enable signal



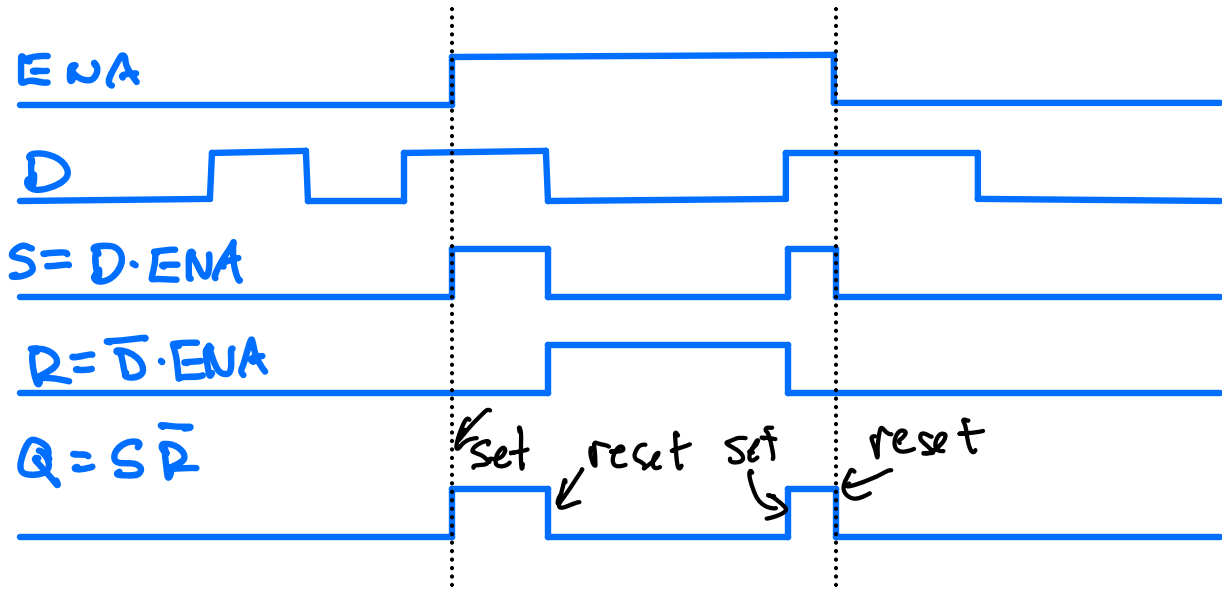 Gated D-latch - uses data input to set/reset




Q "follows" D when ENA is asserted


D Flip-flop (DFF)

want Q to follow D at a specified time as opposed to a time interval, and otherwise stay latched

 ex: want Q to follow D at rising (pos) edge of ENA




 
this is called an "edge-triggered" flip flop
 so we need to make an "edge detector" to
 drive ENA input of gated latch \equiv "D-flip-flop"



This is the basic building block of "synchronous logic"
 as opposed to previous "combinatorial" logic

Synchronous logic: every thing happens in sync
 with a "clock" signal

But how to make edge detector? Easy!

 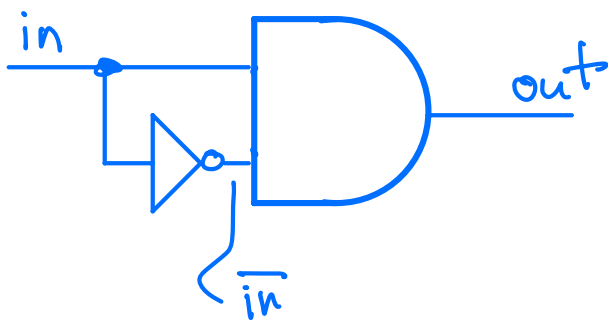

} \bar{in} signal has to propagate
 thru inverter.
 takes small $\Delta t > 0$

Synchronous logic


Example: A sends B 8-bits of info over an 8-bit "bus" (8 wires)
B's job is to latch the 8 signals

Problem:

 1. could be noise on the lines when not being driven
2. transitions of each line won't be perfectly simultaneous

Both of these problems happen near transition time

Solution: latch the lines when things are stable, away from edges



Easy if T is large. If $T \sim 100\text{ns}$ ($f = 10\text{MHz}$),
easy to find region to latch

If each bit is transitioning at 10MHz and sending 8 bits
then bit rate = $80\text{Mb/s} = 10\text{MB/s}$ (byte/sec)

At 100MHz , 10ns per transition, 100MB/s for 8 bits

⇒ even 10ns is "easy" to handle
What if you want 1GB/s rates?

Can go from 8 bits to 80 bits, add more lines!
and still run at 100MHz per line


But now you have larger jitters that an edge
will fluctuate, so single-bit-errors will increase
solution: serial transmission (later)

Synchronizing

You have a circuit w/ many inputs
Want to implement logic on those signals, all
making transitions

Want to use DFF's & latches inside circuit,
need to know where the transitions are

⇒ "Register everything"!

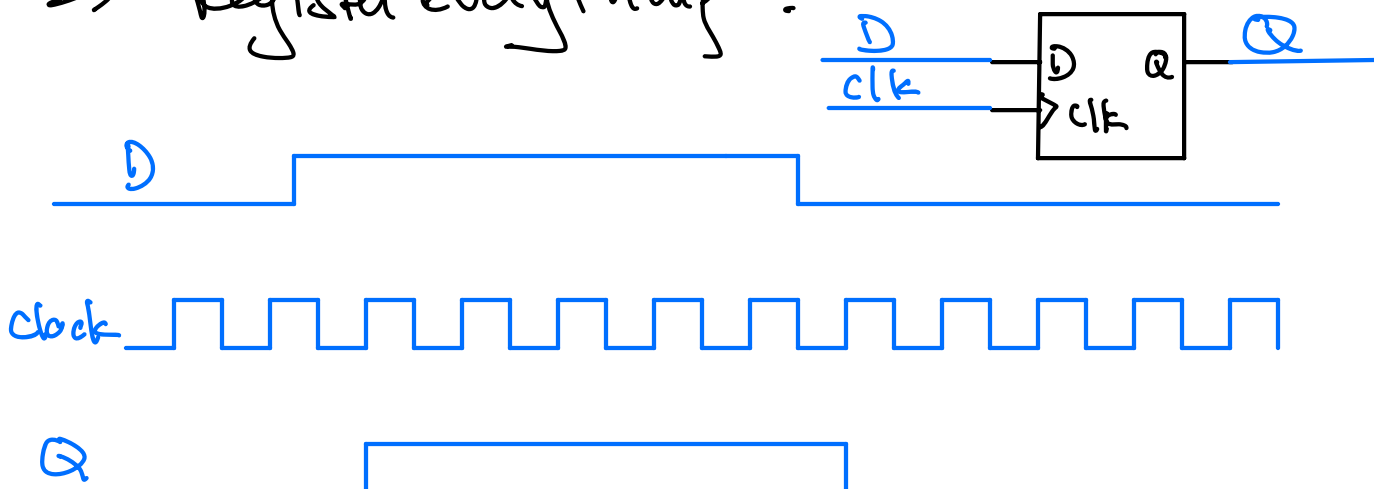

Q is now synchronous w/clock