
 





Clock divider

 

$clk2$ has a period $T_2 = 2T_1$ so $f_2 = f_1/2$ clock divider!

next add another divider onto $clk2 \rightarrow clk4$,

and one on $clk4 \rightarrow clk8$:

   

each "wire" is either 0 or 1, so look at the values of the Bus that is made from the wires

$$B[3:0] = \{clk_8, clk_4, clk_2, clk\}$$

$\{ \}$ called a "concatenation"

B_0 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1

B_1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1

B_2 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0 1 1

B_3 1 1 1 1 1 1 1 0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1 0 0

14 13 12 11 10 9 8 7 6 5 4 3 2 1 0 15 14 13 12 11 10 9 8 7 6

$B[3:0]$ is a "count-down" timer

if we want a "count-up" timer we invert B



ex: we have a 1 MHz clock and want to use it to generate a pulse at ~ 1 Hz (not critical if it's $\pm 10\%$ of 1 Hz)

1 MHz \rightarrow 1 μ s period

1 Hz \rightarrow 1000 μ s period so need 1,000 "ticks" of the clock between pulses


if we make a 10-bit count-up counter, max would be $2^{10} = 1024$ ticks before counter "rolls over"

decimal 1000 = 3E8 hex

= 1111101000 binary


10-bit counter C[9:0]

generate pulse when C = 3E8 hex

 

Serial data

 say you want to send data on a line serially, so 1 bit of info followed by another and ... in finitum
define a "bit clock" → transition between bits
(between posedge of bit clock)



"data stream" of bits, grouping into 4-bit groups "nibbles"

need a way to take these serial bits and form

4-bit "words" : $Q[3:0]$




\Rightarrow it takes 4 bit clock ticks to get 1 4-bit word

use a "shift register"

bclk = bit clock

Bclk = byte clock

(here 1 byte = 4 bits)

   

black DFF's are called a "shift register"

we shift data into SP w/ bclk

\Rightarrow add red DFF's w/ Bclk to make

"serial-in parallel-out" shift register
(SIPO)