

(Finite) State machines

Imagine a machine that has a finite number of states it could be in at any 1 time to perform a task


⇒ has inputs & outputs

⇒ well defined states

⇒ transitions from 1 state to the other depends on inputs & current state


⇒ outputs are determined by what state it's in

 ex: build a digital controller for traffic lights



want the transition $G \rightarrow Y$ to take a time T_g
 $Y \rightarrow R$ " T_y
 $R \rightarrow G$ " T_r

 want to be able to "program" T_g, T_y, T_r
so need 3 "timers"



ena enables a count-up counter

reset sets the counter to ϕ

target is a n-bit number


done goes high when the counter = target

note: $reset = \overline{ena}$ (when not enabled, reset to ϕ)

3 done lines: G_d, Y_d, R_d input to FSM


3 ena " : G_e, Y_e, R_e output of FSM

 3 signals to turn on the 3 lights, can use timer ena lines




we can build this out of DFFs and logic gates

start in G state

 


with feedback, stays in the state

 G_e asserted turns on green light and starts green timer
 \Rightarrow But want to go to yellow when G_d is asserted




 now we transition to Y state on next clock tick
 condition is that G_d is asserted AND we are in G state




Y state has same feedback circuit as G state

 \Rightarrow but it is turned on by Y' or feedback circuit




now put it all together:

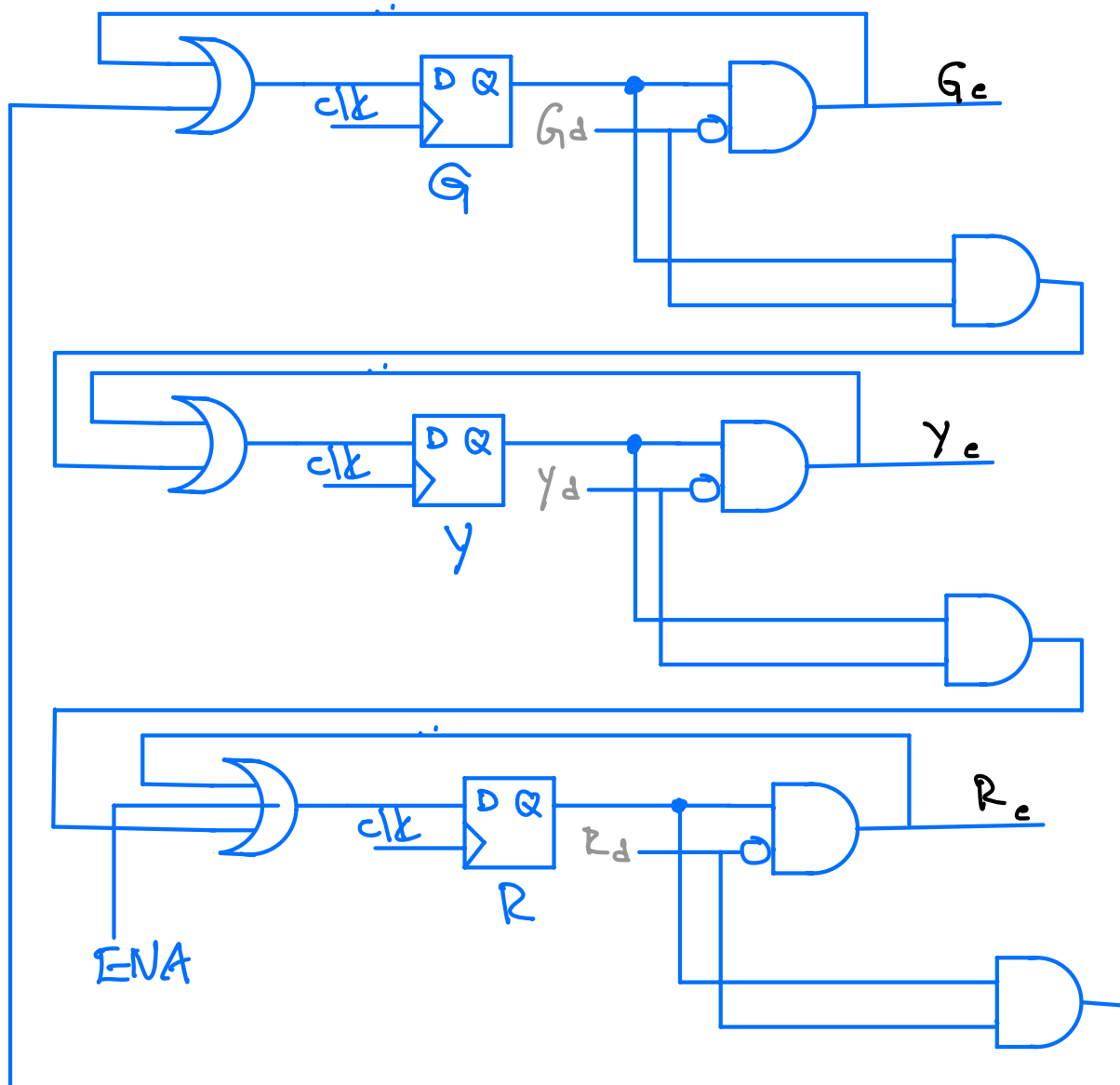


- Note: timer enables also turn on the lights
⇒ when done is asserted, the light goes out after a single AND gate
⇒ transition to next state happens at posedge of next clock via DFF, so can't have 2 lights on at same time!
- note: need a global start ENA

Timing diagram

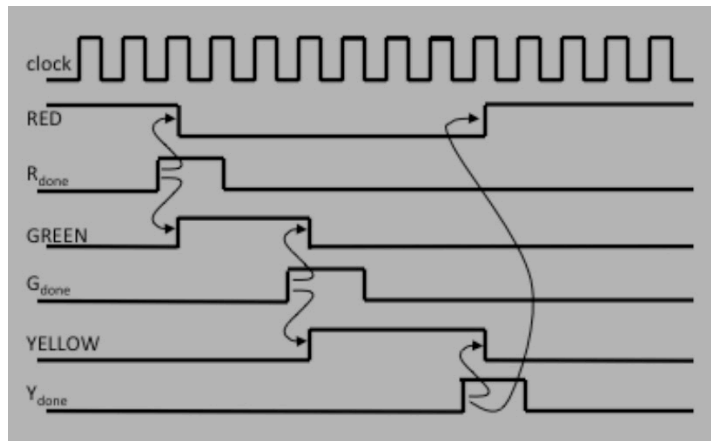

 note that done signal is a pulse \rightarrow comes from timer, which is reset when enable signal goes away



this is called a "handshake":


1. ena asserted starts counter
2. done asserted when counter reaches target
3. ena deasserted when done asserted
4. done reset (deasserted) when ena deasserted (waits!)

done doesn't have a required width since it is just used by the FSM to trigger a transition

Handshake

Often, 2 state machines "talk" to each other



ex:

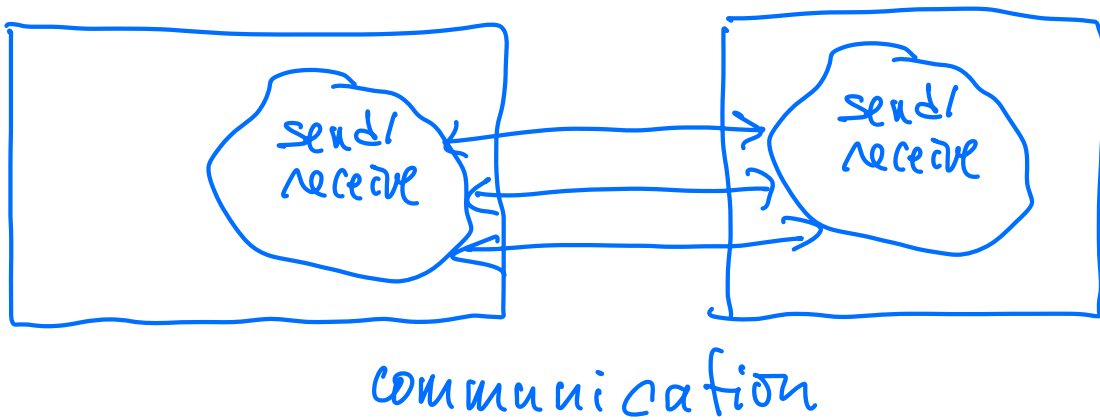

each FSM sends signals to the other
⇒ need to be clear on the protocol

- ex:
- FSM₁ receives ENA from FSM₂
 - FSM₁ then performs a task & sends DONE
 - FSM₂ waits for DONE

"Careful" handshake

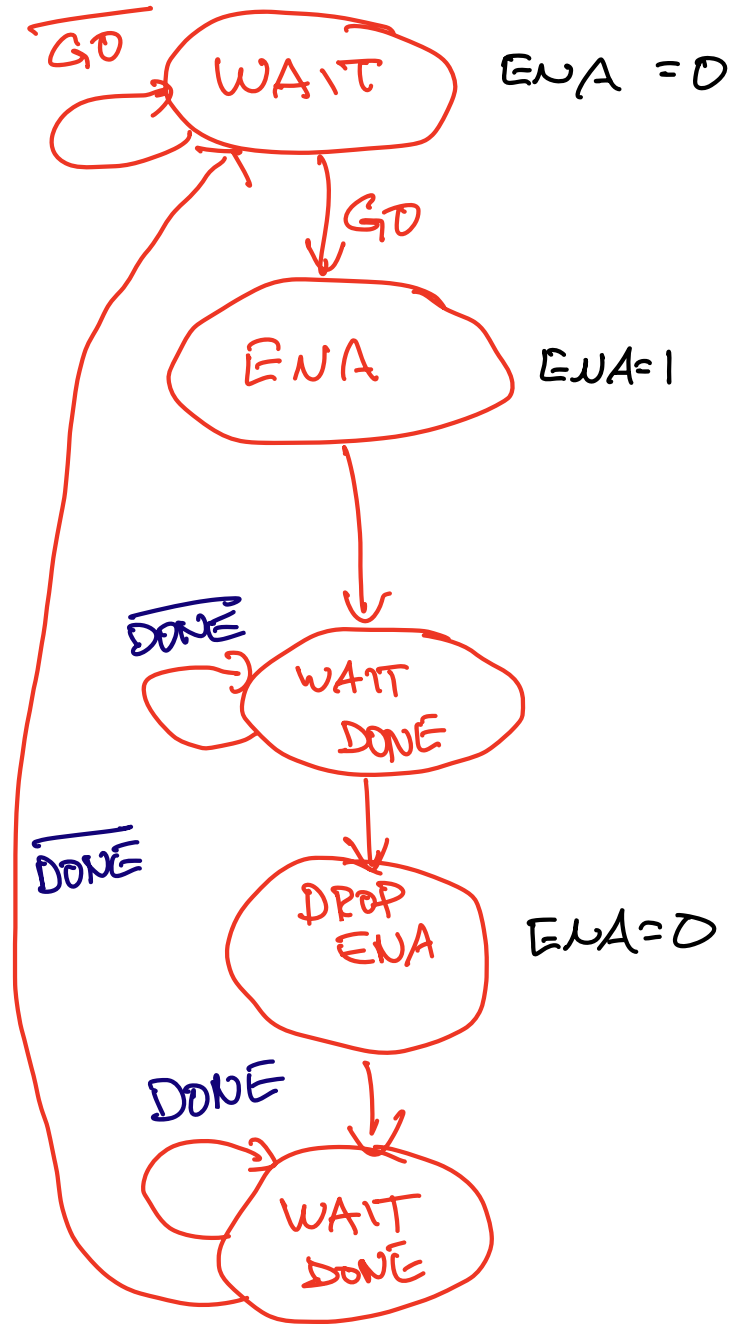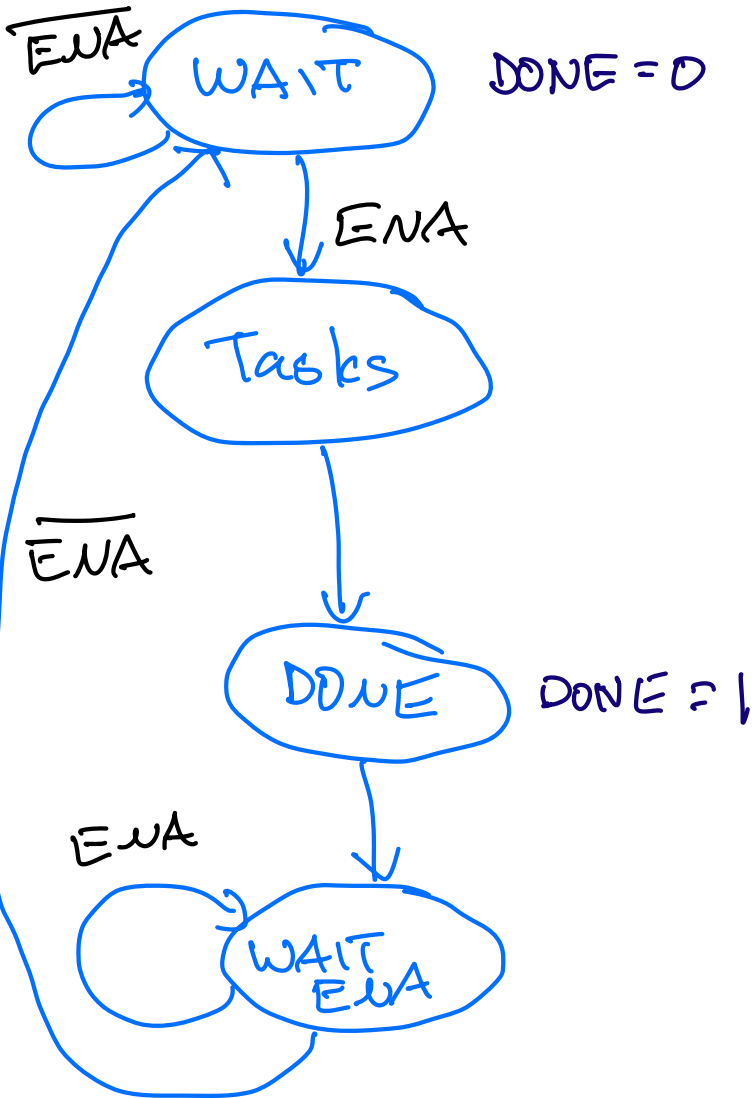


1. GO starts red FSM

2. Red → ENA state, asserts ENA signal and goes to WAIT_DONE state to wait for DONE signal

3. Blue FSM sees ENA & execute tasks. When finished, go to DONE state and assert DONE signal and goes to WAIT_ENA to wait for ENA to go away

 
4. Red sees DONE asserted, goes to DROPEVA state and deasserts ENA (set to \emptyset) and then goes to WAITDONE state
5. Blue sees ENA deasserted & goes back to WAIT state where DONE is deasserted
6. Red sees DONE deasserted & goes back to WAIT



HANDS SHAKE!


⇒ often, a signal like DONE can stay asserted but have no meaning → somewhat dangerous, can lead to faulty transitions

 ⇒ here's how you can assure a signal like done has a finite width: "one-shot"



this assures "done pulse" will have width
1 - 2 ticks

ex: done asserted close to posedge

 

ex: done asserted far from posedge

