

Verilog - a "Hardware Description Language"
(HDL)

⇒ originally invented in early 1980s

for simulation of discrete component networks

Verilog ⇒ synthesis of verification & logic

Originally owned by Cadence, INC
but made available in public domain ~1990

VHDL ⇒ originally from DOD military
for ASIC (application specific integrated
circuits) production


VHDL allows very specific details of everything
down to hardware level

ex transistor rise times, etc

⇒ it is too detailed & Verilog is easier to
learn

Verilog is used to describe circuits

 For example, here's an FPGA chip with inputs & outputs



Inside you want to instantiate a circuit
⇒ this is your "Top level" circuit, or "module"

Verilog code:

```
module TOP (inpts, outputs)
    :
end module
```

↑ arbitrary name

~ all lines end with j

Inputs: these are input FROM somewhere

Outputs: these drive signals TO somewhere


⇒ will discuss external to FPGA later

Specifying inputs & outputs:

old way: name the inputs A, B, C, D
and the output E

```
module TOP (A, B, C, D, E);  
input A, B, C, D;  
output E;  
:  
end module
```

lets code this circuit:

 

we have 3 AND gates

Verilog: use data type "WIRE" to specify
connections → like a real wire
that connects components on a
circuit board

```
module TOP (A, B, C, D, E);
```

```
input A, B, C, D;
```

```
output E;
```

```
wire A, B, C, D;
```

```
wire E;
```

```
or wire A;  
wire B;  
wire D;
```

now we need a wire to connect gates ② to ③

```
wire C1;
```

```
wire C2;
```

next, perform logic using operators

$\&$ = AND

$|$ = OR

\wedge = XOR

\sim = NOT

and use assign to perform logic

```
assign C1 = A & B;
```

```
assign C2 = C & D;
```

shortcut:

```
wire C1 = A & B;
wire C2 = C & D; } implicit assign
```

or

```
wire C1, C2;
C1 = A & B;
C2 = C & D;
```

both are OK: 1st method is used to keep declaration together, separated from assignments

Then for output E:

```
assign E = C1 & C2;
```

code:


```
module TOP (A, B, C, D, E);
input A, B, C, D;
output E;
wire A, B, C, D;
wire E;
```

```


wire c1, c2;
assign c1 = A & B;
assign c2 = c1 & D;
assign E = c1 & c2;
end module

```

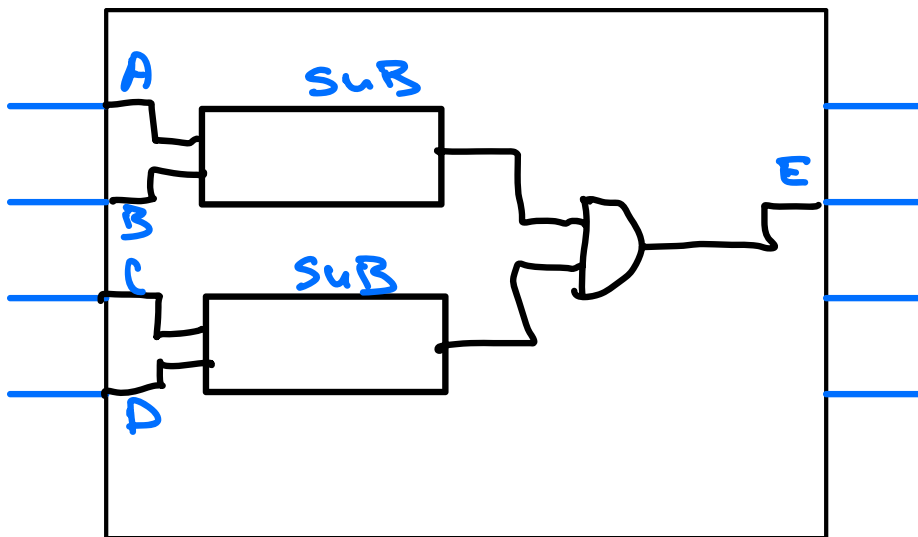Subcircuits: lets put the 1st 2 AND gates into a subcircuit



 subcircuit name is suB ; there are 2 here



code is:

```
module sub(a,b,c)
input a,b;
output c;
assign c = a & b;
end module
```

now I place 2 copies of sub inside top
and specify connections
⇒ have to specify a "local name"
for sub inside TOP

```
module TOP(A,B,C,D,E);
input A,B,C,D;
output E;
wire A,B,C,D;
wire E;
wire c1;
sub local1(A,B,c1);
wire c2;
sub local2(c,D,c2);
assign E = c1 & c2;
end module
```

follows order of arguments
in sub

completely arbitrary
names

variation on instantiating SUBs:

```
sub local1 (.a(A), .b(B), .c(C));
```

↑
module
arg name

this says connect A to a, B to b, etc.
=> no longer depends on order!

note: assign is mostly just for simulation


```
assign A = B & C;
```

means if B or C changes, then change A

for making FPGA circuits it's often
not necessary

exception: for driving an output

Verilog mux

 

if control = 0, out = in1
else out = in2

in verilog, use a "conditional"

wire out;

assign out = control ? in1 : in2;

in1 : in2 ;
1 0

Verilog bus

bus \Rightarrow collection of wires

wire [1:0] N;

MSB \uparrow \downarrow LSB

then there are 2 wires: N[0] is LSB
N[1] is MSB


Verilog register

mostly used as output of DFF or latch,
 \Rightarrow holds data

reg A;

can think of a reg as a DFF or a
"driver" that drives current
(but mostly for DFFs)

Verilog flip-flops

 

Q always follows D at
posedge of the clock clk

```
wire D;
```

```
reg Q;
```

```
always @ (posedge clk) Q = D;
```

if we have 2 DFF's, can use this syntax:

```
wire D1, D2;
```

```
reg Q1, Q2;
```

```
always @ (posedge clk) Q1 = D1;
```

```
always @ (posedge clk) Q2 = D2;
```

or

```
wire D1, D2;
```

```
reg Q1, Q2;
```

```
always @ posedge (clk) begin
```

```
    Q1 = D1;
```

```
    Q2 = D2;
```


```
end
```

matched!


problem: take following

```
wire D ;  
reg Q1, Q2 ;  
always @ (posedge clk) begin  
    Q1 = D ;  
    Q2 = Q1 ;  
end
```

ambiguous!

 

or

 

what we probably want is:

1. 1st edge, $Q1 = D$
2. 2nd edge, $Q2 = Q1$

using $Q1 = D ;$ executing in series
 $Q2 = Q1 ;$ or parallel ?

BLOCKING :	$Q1 = D ;$	evaluate
	$Q2 = Q1 ;$	continuously
NON-BLOCKING	$Q1 \leftarrow D ;$	evaluate 1 st ,
	$Q2 \leftarrow Q1 ;$	then assign,
		all at once

ex:

```

reg A, B, C;
always @ (posedge clk) begin
    A = 1;
    B = A;
    C = B;
end

```

if this was a computer code, then things would happen sequentially
 \Rightarrow after $C = B;$ they would all be = 1

so each statement "blocks" the next one from occurring until executed

In FPGA we want things to happen in parallel!

so after 1st clock: $A=1$

$B=?$

$C=?$

2nd " $A=1$

$B=1$

$C=?$

3rd " $A=1$

$B=1$

$C=1$

each statement is evaluated and assigned simultaneously, and are non-blocking

For programmable logic, need to distinguish:


BLOCKING Assignment: use $=$
always for combinatorial logic

NON-BLOCKING Assignment: use \leftarrow
always for sequential logic

note: for DFF inside always, use \leftarrow

ex circuit

TOP

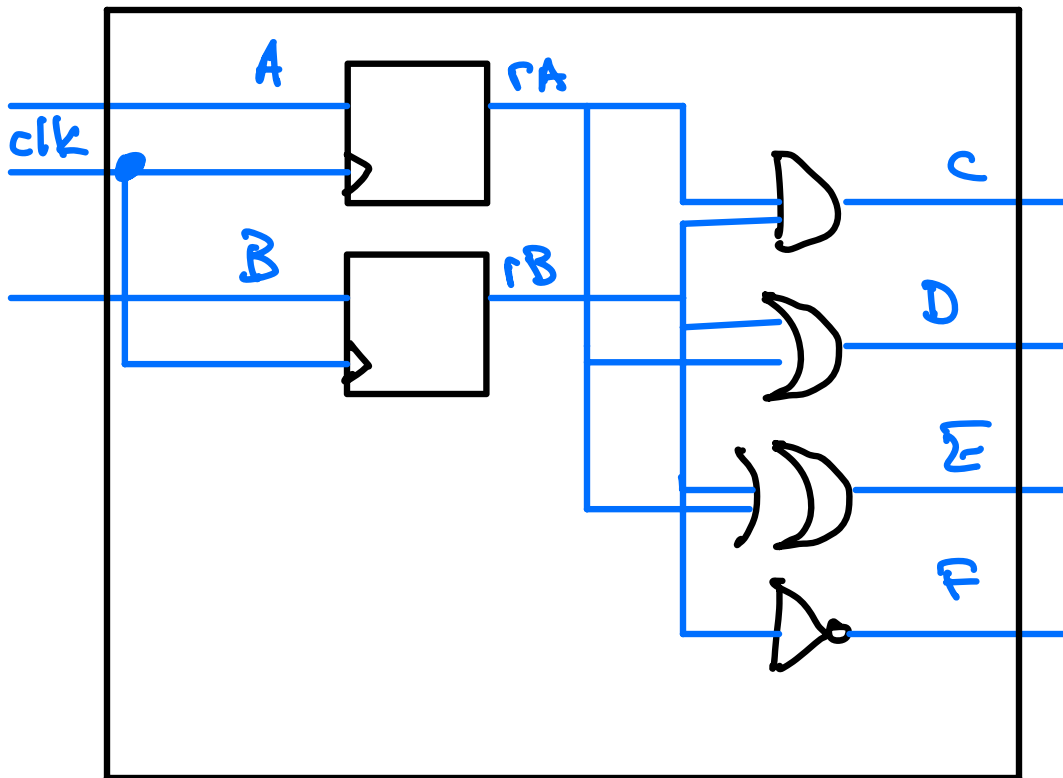

```
module TOP (  
  // declare in/out  
  input A, B, clk,  
  output C, D, E, F  
);  
  reg rA, rB;  
  always @(posedge clk) begin  
    rA <= A;  
    rB <= B;  
  end  
  /*  
  combinatorial logic
```

*/

```
assign C = rA & rB;  
assign D = rA | rB;  
assign E = rA ^ rB;  
assign F = ~ rA;  
endmodule
```

} optional assign
} not optional, drives output

Conditionals a wire that determines an output depending on if it is 0 or 1

ex: x is a wire (binary)

if x is 0, y = 2, else y = 5

wire x;

wire [2:0] y; (need 3 bits to hold values)

if (x) y = 5; (or $y = \{1, 0, 1\}$)

else y = 2; (or $y = \{0, 1, 0\}$)

alternative:

 true false
 ↓ ↓
y = x ? 5 : 2;

Math verilog synthesizer can implement math!

ex: wire [1:0] a, b;

wire [2:0] c;

c = a * b;

synthesizer will build the logic to implement "*"

⇒ will also do this for +, -, /