

Key phenomena:

1. changing Φ_m magnetic thru loop causes induced EMF around loop

$$\mathcal{E}_{ind} = - \frac{d\Phi_m}{dt}$$

if loop is a conductor w/ resistance R , an induced current will flow

$$I_{ind} = \frac{\mathcal{E}_{ind}}{R}$$

2. external currents in wires cause magnetic fields

solenoid: $B = \mu_0 n I$ along center

wire: $B = \frac{\mu_0 I}{2\pi r}$ $r = \text{dist from wire}$

next put them together with external currents causing induced currents




- current thru coil ① causes B field
- B₁ will go thru coil ②, causing flux Φ_2

$$\Phi_2 = B_1 N_2 A_2 \quad N_2 = \# \text{ turns in}$$

- if B doesn't change, then $\frac{d\Phi_2}{dt} = 0$ coil ②
so no induced \mathcal{E}_2 in coil ②
- if you move coil ① closer to coil 2 you will cause a $\frac{d\Phi_2}{dt} \Rightarrow \mathcal{E}_2$ induced in ②

\Rightarrow these coils are said to be "flux linked"

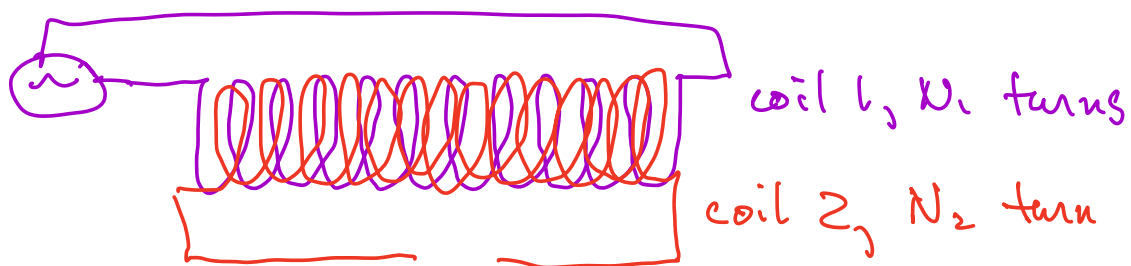now vary I_1 using variable voltage source, and couple the coils so it's easy to calculate the flux



say they have same length,

$$\text{so } \mu_1 = \frac{N_1}{L} \quad \therefore \quad \mu_2 = \frac{N_2}{L}$$

B_1 produced inside coil ①

$$B_1 = \mu_0 n_1 I_1(t)$$

ϕ_2 is flux through 1 turn of coil 2

total flux in coil 2 is $\Phi_2 = N_2 \phi_2$ N_2 loops

$$\phi_2 = B_1 \cdot A_2 = B_1 A \quad (A_1 = A_2)$$

so $\Phi_2 = N_2 B_1 A = N_2 A \mu_0 n_1 I_1(t)$

note: Φ_2 total flux in coil ② due to

B_1 from coil ① is proportional to

only physical characteristics of coils

$$\Phi_2 = (N_2 n_1 A \mu_0) I_1$$

coils that are flux linked always have this:

$$\Phi_2 \propto I_1$$

in general it may be difficult to calculate proportionality, but we can usually measure it!


$$\Phi_2 = M I_1 \quad M \equiv \text{"mutual" inductance}$$

units of M : $M = \Phi_2 / I_1$ so units are
Webers/ampere

this is a Henry

$$1H = 1WB/A$$

ex: 2 coils w/ different areas

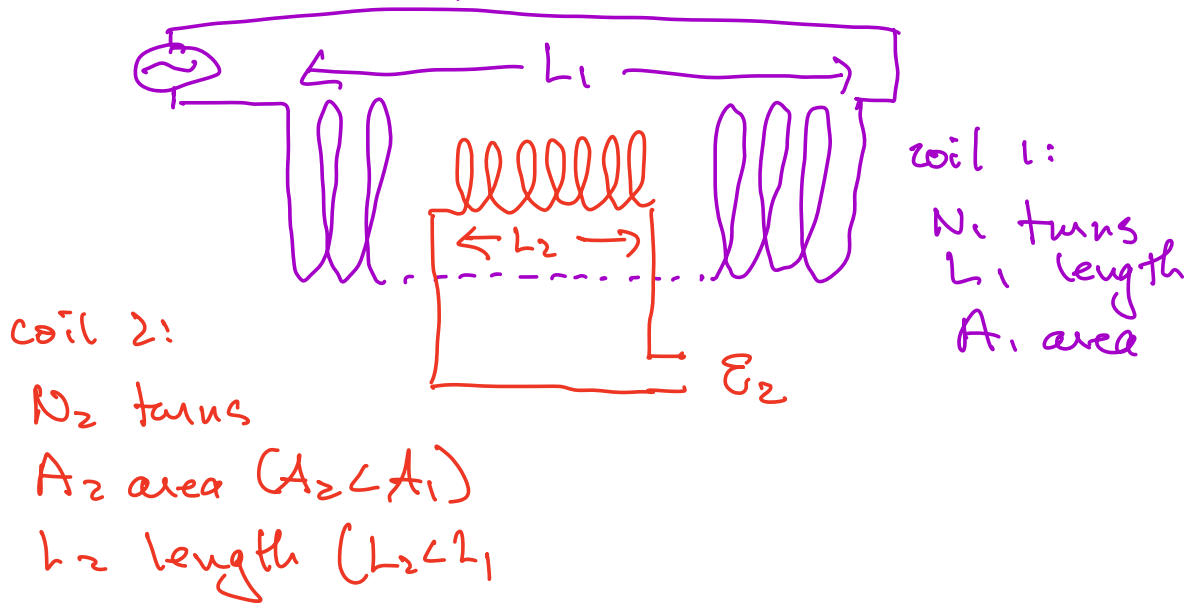

current I_1 generates B_1 constant inside coil ①

$$B_1 = \mu_0 n_1 I_1 \quad n_1 = N_1 / L_1$$

this B-field goes thru coil ②

$$\Phi_2 = B_1 A_2 \quad \text{so} \quad \Phi_2 = N_2 B_1 A_2$$

$$= \underbrace{\mu_0 n_1 N_2 A_2}_{M} \cdot I_1$$

$$M = \Phi_2 / I_1 = \mu_0 n_1 N_2 L_2 A_2 \quad (N_2 L_2 = N_2)$$

what if instead you put current in coil ② and calculate M ?

$$B_2 = \mu_0 n_2 I_2$$

$$\Phi_1 = B_2 \cdot A_2 ! \text{ why not } B_2 A_1 ?$$

because B_2 only exists inside area A_2 , not A_1 , which is $> A_2$


so $\Phi_1 = N_1' \Phi_1$ where N_1' is the # loops in coil ① that overlap with coil 2

$$N_1' = n_1 L_2 \text{ since only } L_2 \text{ length has overlap}$$

$$\begin{aligned} \text{so } \Phi_1 &= n_1 L_2 \Phi_1 = n_1 L_2 A_2 B_2 \\ &= n_1 L_2 A_2 \mu_0 n_2 I_2 \\ &= (\mu_0 n_1 n_2 L_2 A_2) I_2 \\ &= M I_2 \end{aligned}$$

this is the same as before & is why we call M "mutual inductance"

Self-inductance

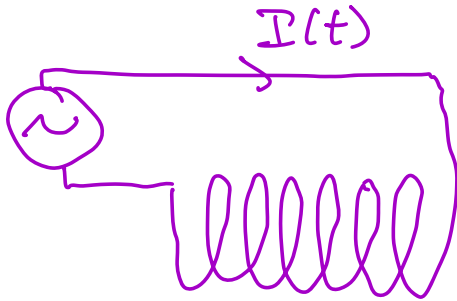

single coil w/ variable voltage source generates time varying current

$I(t) \rightarrow B(t)$ but since its a function of time, $B(t)$ will change

$$B(t) \propto I(t)$$

this will produce a time vary flux $\phi(t)$ thru each loop

$$\text{total flux } \underline{\Phi} = N\phi \quad N = \# \text{ turns}$$

self inductance L defined just like M

$$N\phi = LI$$

for solenoid $B = \mu_0 n I$

$$\phi = BA$$

$$\underline{\Phi} = NBA = \underbrace{\mu_0 N n A}_{L} I$$

since $I(t)$ changes then $\frac{d\Phi}{dt} \neq 0$

so there's a "back" EMF around the loops

$$\mathcal{E} = -\frac{d\Phi}{dt} = -\frac{d}{dt} LI = -L \frac{dI}{dt}$$


so use $\Phi = LI$ to calculate L

$$\mathcal{E} = -\frac{d\Phi}{dt} \text{ to calculate EMF}$$

coils all have a self inductance L (aka "inductance")

Inductors in circuits

constant voltage source:

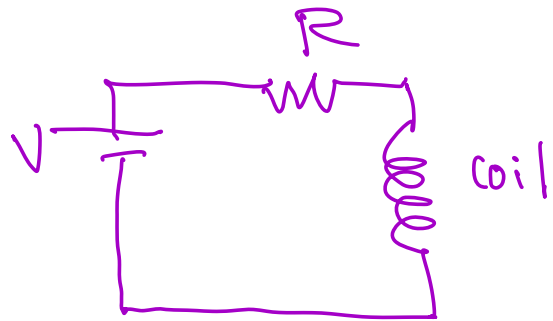

neglect resistance of coil
($R_{\text{coil}} \ll R$)

coil is called "an inductor" w/ self inductance L

if $V = \text{constant}$ then $I = V/R = \text{constant}$

$$\frac{dI}{dt} = 0 \therefore \mathcal{E} = \text{constant inside } L$$

so no induced EMF around inductor coils

Now make voltage source variable



$$\frac{dV}{dt} \neq 0 \text{ so } \frac{dI}{dt} \neq 0 \text{ so } \frac{dB}{dt} \neq 0$$

so $\frac{d\Phi}{dt}$ self $\neq 0$ \therefore will be induced \mathcal{E} around inductor coils

\Rightarrow induced current will oppose current driven by voltage source

so net current will be less than I with no inductor $\Rightarrow L$ reduces current just like a resistor with some impedance

\Rightarrow all due to Faraday's law

just like a resistor, must be a voltage drop along direction of current

since I & I_{ind} are opposed, $V_L = L \frac{dI}{dt}$

this preserves energy conservation around the loop



note that as frequency of $V(t)$ increases, $\frac{dI}{dt}$ increases $\Leftarrow V_L$ increases which

means induced current increases so net current decreases

\rightarrow inductors act like frequency dependent resistor!

Energy picture

in the LR circuit the inductor acts like a resistor in reducing the current.

⇒ this takes energy! inductor is pushing against power supply

power thru any component is always $P = I \cdot V$

where $V =$ voltage drop across it

$$\text{for inductor } V \equiv \mathcal{E} = L \frac{dI}{dt}$$

$$\text{so } P = LI \frac{dI}{dt} = L \frac{d}{dt} \left(\frac{1}{2} I^2 \right) = \frac{d}{dt} \left(\frac{1}{2} LI^2 \right)$$

power is always $\frac{d}{dt}$ energy

so the energy stored in inductor coil is

$$U_L = \frac{1}{2} LI^2$$

for solenoid $L = \mu_0 n^2 NA$

$$U = \frac{1}{2} \mu_0 n^2 NA I^2 \quad \text{here } B = \mu_0 n I$$

$$\text{(use } N = nL) = \frac{1}{2} NA \mu_0 n I^2 = \frac{1}{2} nLA \mu_0 n I^2$$


$$= LA \cdot \frac{\mu_0 n^2 I^2}{2} = LA \cdot \frac{\mu_0^2 n^2 I^2}{2\mu_0}$$
$$= LA \frac{B^2}{2\mu_0} \quad \text{note that } LA = \text{volume of solenoid}$$

$$\text{so } U = \frac{B^2}{2\mu_0} \cdot \text{Volume}$$

$$\text{so } \frac{B^2}{2\mu_0} = \text{magnetic energy density}$$

\Rightarrow inductor is storing energy!

DC R-L circuit

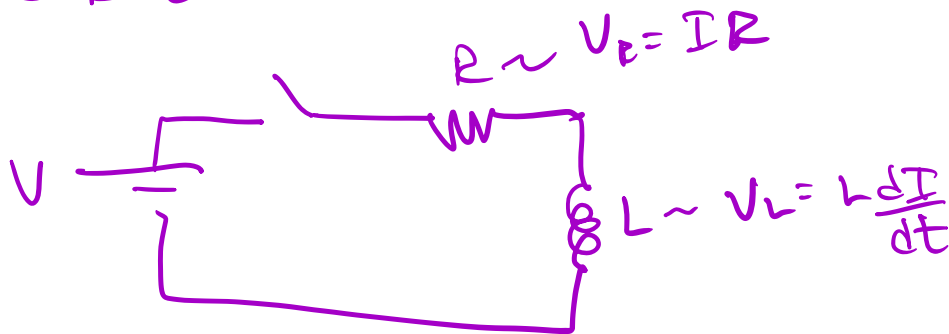

close switch: $V = IR + L \frac{dI}{dt}$

solution: diff eqn

$$L \frac{dI}{dt} = V - IR$$

$$\frac{dI}{dt} = \frac{V}{L} - \frac{IR}{L}$$

must have units of $\frac{A}{s}$
 $\therefore L/R$ has units of time

let $\tau \equiv L/R$

write as
$$\frac{dI}{dt} = \frac{V}{R} - \frac{I}{\tau}$$
$$= \left(\frac{V}{R} - I \right) \frac{1}{\tau}$$

so
$$\frac{dI}{\frac{V}{R} - I} = \frac{dt}{\tau}$$


$$\frac{dI}{I - V/R} = -dt/\tau$$

so $\ln(I - V/R) = -\frac{t}{\tau} + k$ indefinite integral


$$I - V/R = e^k e^{-t/\tau}$$

at $t=0, I=0 \therefore e^k = -V/R$
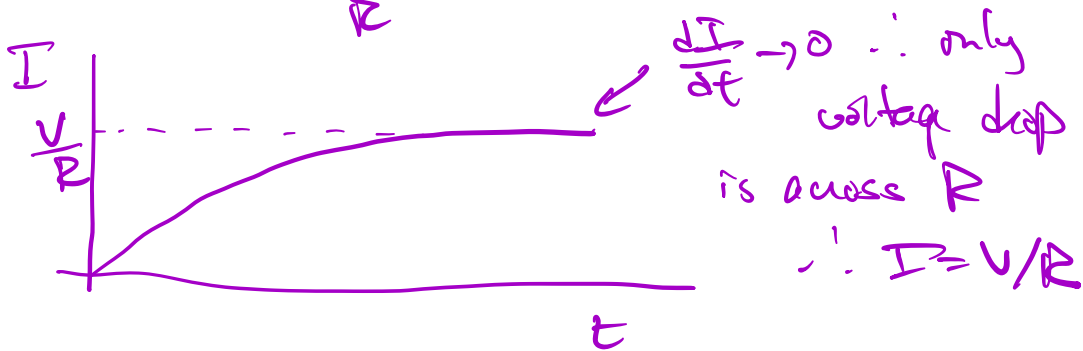
$$\therefore I = \frac{V}{R} (1 - e^{-t/\tau})$$



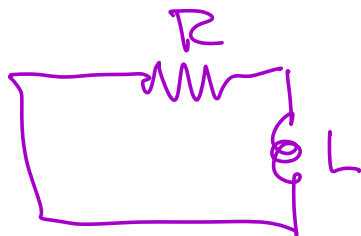now jumper V out of circuit leaving only R & L




current will collapse causing $\frac{dI}{dt}$


$$V_R + V_L = 0 \text{ now}$$

$$\text{so } IR + L \frac{dI}{dt} = 0 \Rightarrow \frac{I}{\frac{L/R}{\tau}} + \frac{dI}{dt} = 0$$
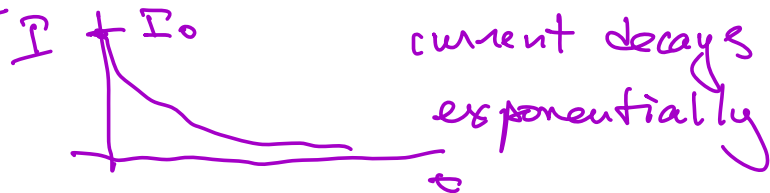
$$\frac{dI}{dt} = -\frac{I}{\tau} \Rightarrow I = I_0 e^{-t/\tau} \text{ where } I_0 = I(t=0)$$



LC circuit

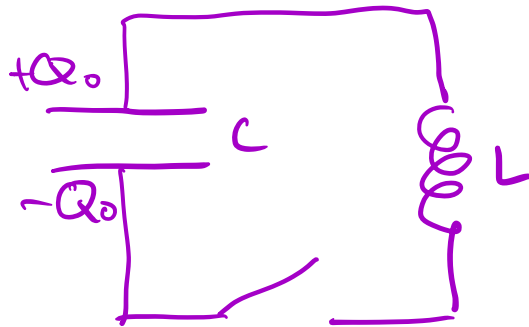

charge up capacitor
by charge $+Q$ on top,
 $-Q$ on bottom

$$C = Q/V$$
$$\text{so } V_C = Q_0/C$$

so will be a voltage $V_C = Q_0/C$

- close switch. this will draw current thru inductor causing a voltage drop across C as the charge is reduced.
- current thru L will cause EMF that will generate induced current back towards capacitor
- induced EMF $\mathcal{E} = -L \frac{dI}{dt}$ will be equal to voltage across capacitor as it discharges

$$\frac{Q(t)}{C} = -L \frac{dI(t)}{dt}$$

- after cap discharges (or as it tries to?) then induced current (now L) will try to recharge

what's happening: energy density $\overset{V}{u_E}$ inside C
decreases, increasing u_B inside
inductor

But they are out of phase

because $\mathcal{E}_L \propto$ rate of change of I

and $V_C \sim Q$ so I is rate of change
of Q

so $V_L \propto$ rate of change of rate of change
of V_C !

solve:
$$\frac{Q}{C} = -L \frac{dI}{dt} = -L \frac{d^2Q}{dt^2}$$

$$\frac{d^2Q}{dt^2} + \frac{1}{LC} Q = 0$$

this is SHM: $\frac{d^2x}{dt^2} + \omega^2 x = 0 \Rightarrow x = x_0 \cos \omega t$

for LC, $\omega^2 = 1/LC$

so $Q = Q_0 \cos \omega t$ ($t=0, Q=Q_0 = CV_0$
and voltage across capacitor will oscillate
across C)

at $t=0, Q = Q_0 = CV_0$

$$\text{so } Q = CV_0 \cos \omega t$$

current thru inductor:

$$I = \frac{dQ}{dt} = -CV_0 \omega \sin \omega t$$

in cap: $E \propto Q$

in ind: $B \propto I$

$\therefore E$ & B "exchange" energy


ex: 100 μF capacitor charged up
25 mH inductor

$$LC = 100 \times 10^{-6} \cdot 25 \times 10^{-3} = 2500 \times 10^{-9} \\ = 2.5 \times 10^{-12}$$

$$\omega = \frac{1}{\sqrt{LC}} = 632 \times 10^3 \text{ rad/sec}$$

$$f = \omega / 2\pi \approx 100 \text{ kHz} \text{ oscillator!}$$

ex:

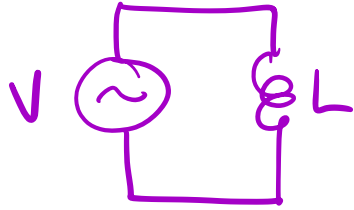

$$V(t) = V_0 \cos \omega t$$

conservation of energy: $V = \mathcal{E}_L = L \frac{dI}{dt}$

$$\text{so } V_0 \cos \omega t = L \frac{dI}{dt}$$

this says $I \propto \sin \omega t$

$$\text{solve: } I = A \sin \omega t + B$$

$$\frac{dI}{dt} = A \omega \cos \omega t = \frac{V_0 \cos \omega t}{L}$$

$$\therefore A = \frac{V_0}{\omega L}$$


$$I(t) = \frac{V_0}{\omega L} \sin \omega t$$

① $\frac{V_0}{\omega L} \Rightarrow$ looks like a current $\therefore R_L = \omega L$
looks like a resistance

for inductor, as $f \uparrow R_L \uparrow$ so inductors do not like high frequencies

$L \rightarrow$ low pass filter

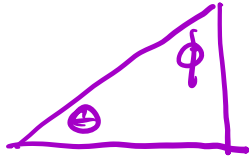② current and voltage are now out of phase by 90°




$$\cos \theta = \sin \phi \quad \text{and} \quad \phi + \theta = 90$$

$$\text{so } \sin \theta = \cos (90 - \theta)$$

$$= \cos (\theta - 90)$$


$$\text{so can write } \underline{I}(t) = \frac{V_0}{\omega L} \sin \omega t$$
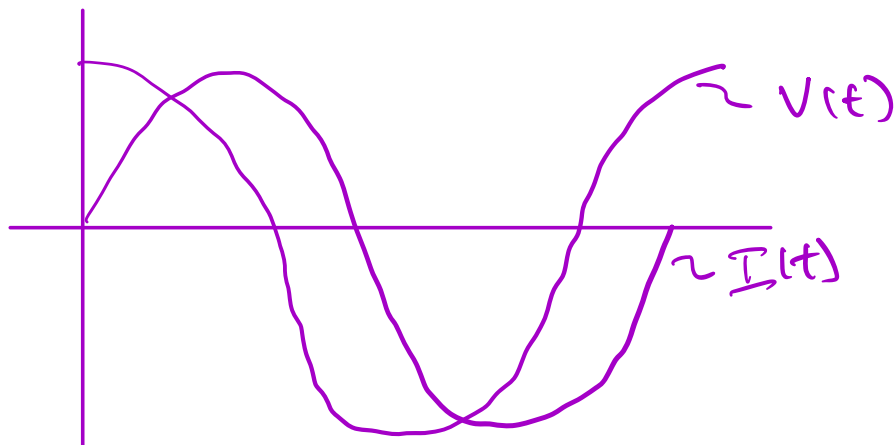
$$= \frac{V_0}{\omega L} \cos (\omega t - \pi/2)$$



I "lags" V by $\pi/2$

AC circuit w/ complex numbers

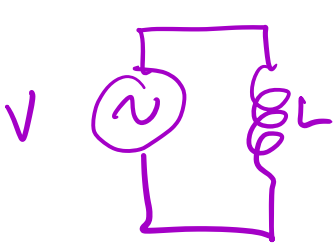

$$V(t) = V_0 \cos \omega t$$

$$\text{make } V(t) = V_0 e^{i\omega t}$$

$$= V_0 \cos \omega t + V_0 i \sin \omega t$$

then keep only real part

$$\text{Re}(V(t)) = V_0 \cos \omega t$$

now solve circuit

gain loss

$$V = V_L = L \frac{dI}{dt}$$

$$\text{so } V_0 e^{i\omega t} = L \frac{dI}{dt}$$

$$\therefore \frac{dI}{dt} = \frac{V_0}{L} e^{i\omega t}$$

$$\therefore I = \frac{V_0}{i\omega L} e^{i\omega t} = -\frac{iV_0}{\omega L} e^{i\omega t}$$

$$I = -\frac{V_0}{\omega L} (i \cos \omega t + i^2 \sin \omega t)$$

$$= \frac{V_0}{\omega L} (\sin \omega t - i \cos \omega t)$$

$$\text{keep } \text{Re}(I) \Rightarrow I = \frac{V_0}{\omega L} \sin \omega t \text{ as above!}$$

ⓐ notice: $I = \frac{V_0}{i\omega L} e^{i\omega t} \Rightarrow$ rewrite

$$V_0 e^{i\omega t} = I(i\omega L)$$

$$\text{or } V = I(i\omega L)$$

$i\omega L$
"reactance" X_L


$X_L = i\omega L$ complex impedance

inductors act like resistors in AC circuits
w/ complex impedance

so if we replace inductors w/ X_L then we
can use "Ohm's Law" for AC circuits easy!

$$V = I X_L$$

L R circuit using complex numbers

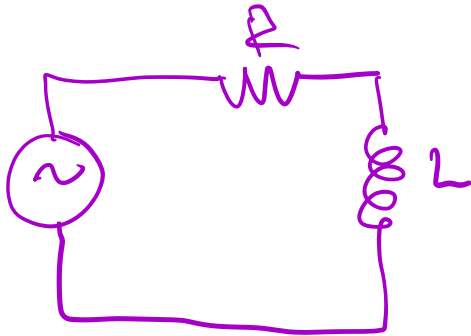

$$X_R = R$$

$$X_L = i\omega L$$

$$\begin{aligned} \text{then } V &= IR + IX_L \\ &= I(R + i\omega L) \end{aligned}$$

$$\therefore I(t) = \frac{V(t)}{R + i\omega L}$$

now take real part

$$\text{write } \frac{1}{R + i\omega L} = \frac{1}{R + i\omega L} \cdot \frac{R - i\omega L}{R - i\omega L} = \frac{R - i\omega L}{R^2 + \omega^2 L^2}$$

$$= \frac{R - i\omega L}{\sqrt{R^2 + \omega^2 L^2}} \cdot \frac{1}{\sqrt{1}}$$

$$\text{let } \cos\phi = \frac{R}{\sqrt{1}}, \quad \sin\phi = \frac{\omega L}{\sqrt{1}}$$

$$\tan\phi = \omega L/R \quad \text{let } \tau \equiv L/R$$

$$\tan\phi = \omega\tau$$

$$\text{so } \frac{1}{R + i\omega L} = \frac{\cos\phi - i\sin\phi}{\sqrt{R^2 + \omega^2 L^2}} = \frac{e^{-i\phi}}{\sqrt{1}}$$

$$\begin{aligned} \therefore I(t) &= V_0 e^{i\omega t} \cdot \frac{e^{-i\phi}}{\sqrt{R^2 + \omega^2 L^2}} \\ &= \frac{V_0}{R} \frac{e^{i(\omega t - \phi)}}{\sqrt{1 + \omega^2 \tau^2}} \end{aligned}$$

$$\text{keep } \text{Re}(I) = \frac{V_0 \cos(\omega t - \phi)}{R \sqrt{1 + \omega^2 \tau^2}}$$

$\phi \equiv$ phase shift \Rightarrow gets smaller (I in phase w/ V)
as $L \rightarrow 0$ or $R \rightarrow \infty$

① inductor causes a phase change in current wrt driving voltage

$$\tan \phi = \frac{\omega L}{R} = \omega \tau$$


② as $\omega \rightarrow 0$, becomes constant voltage

$$\omega \tau \rightarrow 0, \tan \phi \rightarrow 0 \Rightarrow \theta \rightarrow 0$$

$$I(t) = \frac{V_0}{R} \cos \omega t \quad \checkmark$$

③ as $\omega \rightarrow$ large, $I \rightarrow 0$ because $X_L \rightarrow \infty$ acts like a large resistance so inductor is a low pass filter

AC - capacitor

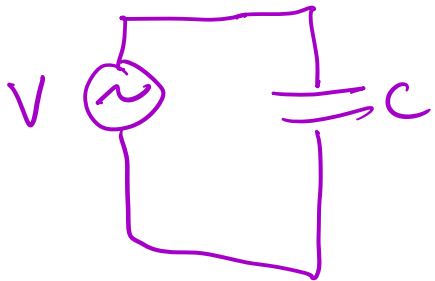

$$V(t) = V_0 e^{i\omega t}$$

$$V_c = \frac{Q}{C} = V \text{ supply}$$

$$\text{so } Q = CV$$


$$\begin{aligned} I &= \frac{dQ}{dt} = C \frac{dV}{dt} = C \frac{dV_0 e^{i\omega t}}{dt} \\ &= i\omega C V_0 e^{i\omega t} \\ &= \frac{V_0}{X_c} e^{i\omega t} \end{aligned}$$

$\therefore X_c = \frac{1}{i\omega C}$ complex reactance for capacitor

and $X_L = i\omega L$

$$X_R = R$$

LCR circuit

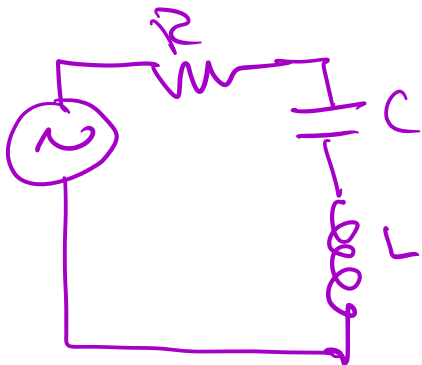

} C & L have "complex" impedances

R has "real" impedance

$$\begin{aligned} \overset{\text{gain}}{V} &= \overset{\text{drops}}{I}R + IX_c + IX_L \\ &= I \left(R + \frac{1}{i\omega C} + i\omega L \right) \end{aligned}$$

$$\therefore I = \frac{V_0 e^{i\omega t}}{R + \frac{1}{i\omega C} + i\omega L}$$

$$\begin{aligned} R + \frac{1}{i\omega C} + i\omega L &= R - \frac{i}{\omega C} + i\omega L = R + i \left(\omega L - \frac{1}{\omega C} \right) \\ &= R + i \frac{L}{\omega} \left(\omega^2 - \frac{1}{LC} \right) \end{aligned}$$