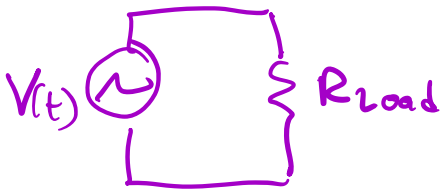


AC Circuits




$$V(t) = V_0 \cos \omega t \quad \omega = 2\pi f$$

by Ohm's law: $V = IR$
 $\therefore I(t) = \frac{V_0}{R} \cos \omega t$

current & voltage are in phase.
 why important?

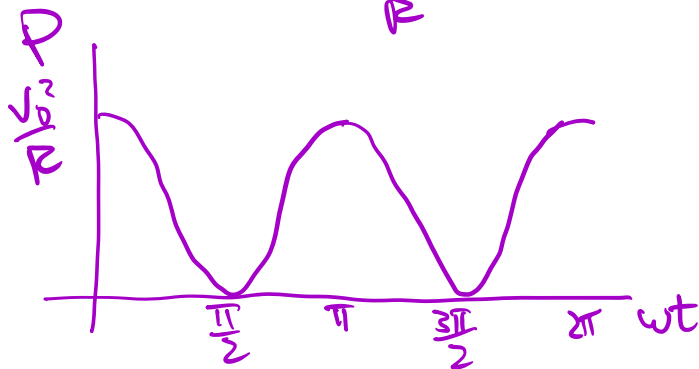
$$\text{Power} = IV = \frac{V_0^2}{R} \cos^2 \omega t$$



Power oscillates. Average power: $\bar{P} = \frac{1}{T} \int_0^T P(t) dt \quad \omega T = 2\pi$

$$\bar{P} = \frac{1}{T} \frac{V_0^2}{R} \int_0^T \cos^2 \omega t dt$$

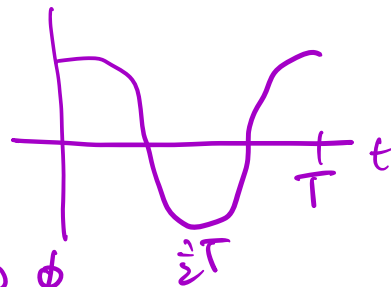$\underbrace{\qquad\qquad\qquad}_{\frac{1}{2}(1 + \cos 2\omega t)}$



so $\bar{P} = \frac{1}{T} \frac{V_0^2}{R} \int_0^T$

$$= \frac{1}{2} \frac{V_0^2}{R}$$

ave power = $\frac{1}{2}$ max power

RMS root mean square

$$V_{\text{rms}} = \sqrt{\overline{V^2}} \quad \text{note: } \overline{V^2} \neq \overline{V}^2$$

$$\overline{V^2} = \frac{1}{T} \int_0^T V^2 \cos^2 \omega t \, dt = \frac{V_0^2}{T} \int_0^T \cos^2 \omega t \, dt = \frac{V_0^2}{2}$$

$$\therefore V_{\text{rms}} = \frac{V_0}{\sqrt{2}} \quad \text{max voltage}$$

$$\text{Similarly } I_{\text{rms}} = \frac{I_0}{\sqrt{2}} = \frac{V_0}{\sqrt{2}R}$$

$$\therefore \overline{P} = \frac{1}{2} \frac{V_0^2}{R} = \frac{1}{2} V_0 \cdot \frac{V_0}{R} = \frac{V_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} = V_{\text{rms}} I_{\text{rms}}$$

in home $V_{\text{rms}} = 120$ Volts

if you draw 10A, that's I_{rms}

$$\text{so } \overline{P} = 120 \cdot 10 = 1.2 \text{ kW}$$

$$V = IR + L \frac{dI}{dt}$$

$$IR - V = L \frac{dI}{dt}$$

$$I - V/R = \frac{L}{R} \frac{dI}{dt}$$

$$I - I_0 = \tau \frac{dI}{dt} \quad \tau = L/R$$

AC w/ Inductor

$$V = V_0 \cos \omega t \rightarrow V_0 e^{i\omega t}$$



$$V_L = L \frac{dI}{dt} = V$$

$$\frac{dI}{dt} = \frac{V}{L} = \frac{V_0}{L} e^{i\omega t}$$

$$I = \frac{V_0}{i\omega L} e^{i\omega t}$$

↑
"resistance"

$X_L = i\omega L$ reactance of ind.
↳ complex impedance

note: as $\omega \rightarrow \infty$ inductor impedance $\rightarrow \infty$

so inductor is "low pass filter"

lets low freq signals thru

to get $I(t)$ keep only real part

$$I = \frac{V_0}{i\omega L} e^{i\omega t} = -\frac{iV_0}{\omega L} (\cos \omega t + i \sin \omega t)$$

$$= \frac{V_0}{\omega L} \sin \omega t - \frac{iV_0}{\omega L} \cos \omega t$$

throw away $\text{Im}(I)$

$$V = V_0 \cos \omega t$$

$$I = \frac{V_0}{\omega L} \sin \omega t = \frac{V_0}{\omega L} \cos(\omega t - \pi/2)$$

current "lags" voltage by 90°


average power: $P_{av} = \frac{1}{T} \int_0^T I(t)V(t) dt$

$$= \frac{1}{T} \frac{V_0^2}{\omega L} \int_0^T \sin \omega t \cos \omega t dt = 0$$

no power loss in (ideal) inductor (assumes $R_L = 0$)

AC w/ capacitor

$$V = V_0 e^{i\omega t}$$

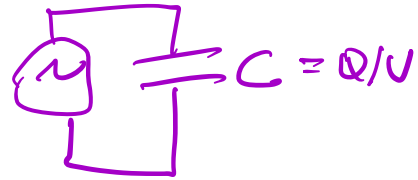

$$V_c = \frac{Q}{C} \Rightarrow Q = V_c C = VC$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt} = V_0 i\omega C e^{i\omega t} = \frac{V_0}{X_c} e^{i\omega t}$$

$X_c = \frac{1}{i\omega C}$ capacitor $X_c \rightarrow \infty$ as $\omega \rightarrow 0$ DC open

capacitor filters out low freq, passes high
"high pass filter"

$$I = V_0 i\omega C e^{i\omega t} = V_0 \omega C i (\cos \omega t + i \sin \omega t) \\ = \frac{-V_0}{1/\omega C} \sin \omega t$$

P_c also zero for same reason as capacitor

$$- \sin \omega t = \cos(\omega t + \alpha) = \cos \omega t \cos \alpha - \sin \omega t \sin \alpha$$


$$\alpha = \pi/2$$

$$\text{so } I = \frac{V_0}{1/\omega C} \cos(\omega t + \pi/2)$$

current "leads" vol lagg by $\pi/2$

LC

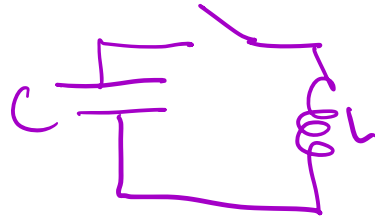Charge up plates, Q
voltage will be $V = Q/C$



close switch: $\frac{Q}{C} = -L \frac{dI}{dt}$

$$\frac{Q}{C} + L \frac{dI}{dt} = 0$$

$$\frac{d^2 Q}{dt^2} + \frac{1}{LC} Q = 0 \quad Q = Q_0 \cos \omega_0 t \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$\omega_0 \Rightarrow$ natural freq of oscillation

no power loss in C or L \therefore energy just oscillates between E^2 in cap & B^2 in inductor


AC and LR

$$V = V_0 e^{i\omega t} = IZ$$

$$Z = \text{complex impedance} \\ = R + Z_L = R + i\omega L$$

$$\text{so } I = \frac{V_0 e^{i\omega t}}{R + i\omega L}$$
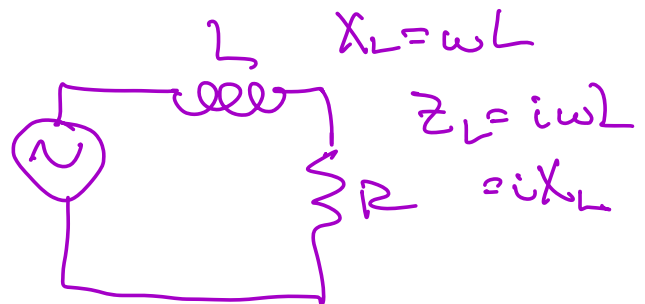
$$\text{write } R + i\omega L = \sqrt{R^2 + (\omega L)^2} e^{i\phi} \quad \tan \phi = \frac{\omega L}{R} \\ = R \sqrt{1 + \left(\frac{\omega L}{R}\right)^2}$$



let $\tau = L/R$ decay time for L in DC circuit
 then $I = \frac{V_0 e^{i\omega t} e^{-i\phi}}{R \sqrt{1 + (\omega\tau)^2}} = \frac{V_0 \cos(\omega t - \phi)}{R \sqrt{1 + (\omega\tau)^2}}$

can write $I_0(\omega) = \frac{V_0}{R} \frac{1}{\sqrt{1 + (\omega\tau)^2}}$

$I(t) = I_0(\omega) \cos(\omega t - \phi)$ $\tan\phi = \frac{\omega L}{R} = \frac{X_L}{R}$

ratio complex / real
impedance


$$\begin{aligned} \overline{P}_{\text{delivered}} &= \overline{I}V = \frac{V_0^2}{R} \frac{1}{\sqrt{1 + (\omega\tau)^2}} \frac{1}{T} \int_0^T \cos(\omega t - \phi) \cos \omega t dt \\ &= \frac{V_0^2}{R} \frac{1}{\sqrt{1 + (\omega\tau)^2}} \frac{1}{T} \int_0^T (\cos \omega t \cos \phi + \sin \omega t \sin \phi) \cos \omega t dt \\ &= \frac{V_0^2}{2R} \frac{1}{\sqrt{1 + (\omega\tau)^2}} \cos \phi \end{aligned}$$

$$\overline{P}_R = \overline{I^2 R} = \frac{1}{T} \frac{V_0^2 R}{R^2 (1 + (\omega\tau)^2)} \int_0^T \cos^2(\omega t - \phi) dt = \frac{V_0^2}{2R(1 + (\omega\tau)^2)}$$


$$\overline{P}_L = \overline{I L \frac{dI}{dt}} = \frac{V_0 \cos(\omega t - \phi)}{R \sqrt{1 + (\omega\tau)^2}} L (-\omega) \frac{V_0 \sin(\omega t - \phi)}{R \sqrt{1 + (\omega\tau)^2}} = 0$$

$\overline{P}_{\text{del}} = \overline{P}_R$ so $\cos \phi = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$

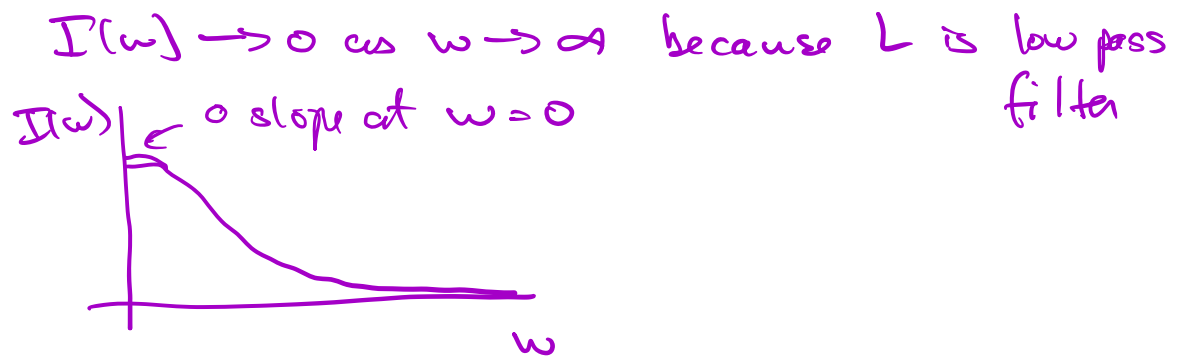$\tan \phi = \frac{\omega L}{R} = \omega\tau \Rightarrow 1 + \tan^2 \phi = \sec^2 \phi = 1 + (\omega\tau)^2 \checkmark$



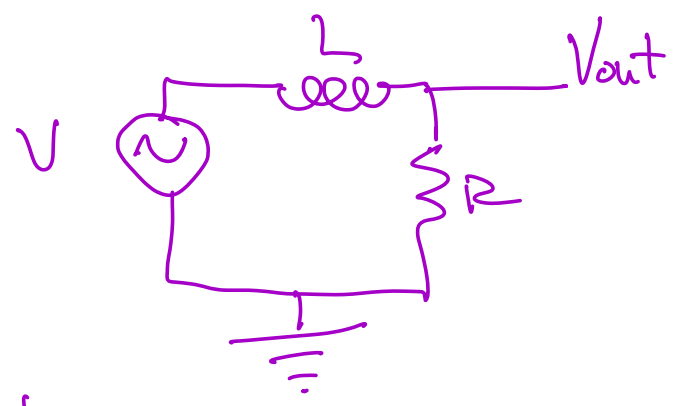
We can ground part of the circuit to set EM potential to be zero there.



\Rightarrow Voltage $V_{out} =$ voltage across resistor

$$V_{out} = IR = \frac{V_0 \cos(\omega t - \phi)}{\sqrt{1 + (\omega L)^2}}$$

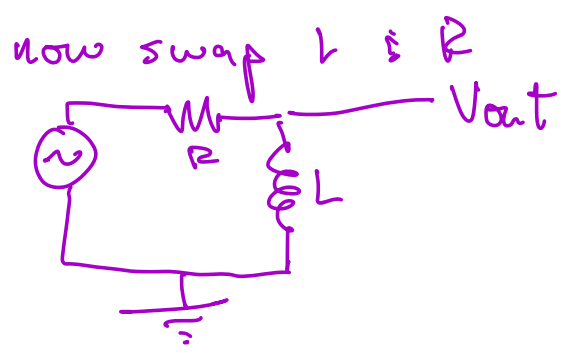as $\omega \rightarrow 0$, $V_{out} \rightarrow V_0$ low pass
 $\omega \rightarrow \infty$, $V_{out} \rightarrow 0$ filters out high frequencies



voltage across inductor:

$$V_{out} = V_L = I X_L = \frac{i V_{in} \omega L e^{i(\omega t - \phi)}}{R \sqrt{1 + (\omega L)^2}}$$

$$\text{Re}(V_{out}) = \text{Re} \left(\frac{V_{in} \omega L}{R \sqrt{1 + (\omega L)^2}} \left[\cos(\omega t - \phi) + i \sin(\omega t - \phi) \right] \right)$$

$$V_{out} = \frac{-V_{in} \omega L \sin(\omega t - \phi)}{R \sqrt{1 + (\omega L)^2}}$$


since ω is in numerator, $V_{out} \rightarrow 0$ as $\omega \rightarrow 0$

as $\omega \rightarrow \infty$, $\frac{\omega L}{\sqrt{1 + (\omega L)^2}} \rightarrow 1$, $V_{out} \rightarrow V_0$

this filters out low frequencies!

\Rightarrow basically, inductor allows low freq to pass to ground leaving high frequencies

AC RC circuits

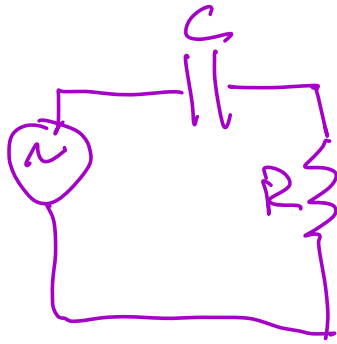

$$X_c = \frac{1}{\omega C}, \quad Z_c = \frac{1}{i\omega C}$$

$$Z = R + Z_c = R + \frac{1}{i\omega C} = \sqrt{R^2 + \frac{1}{(\omega C)^2}} e^{i\phi}$$


$$\tan\phi = \frac{1}{\omega RC}$$

here $RC =$ decay constant for RC discharge

let $\tau = RC$ and write $\sqrt{R^2 + \frac{1}{(\omega C)^2}} = R \sqrt{1 + \frac{1}{(\omega\tau)^2}}$

$$\text{so } I = \frac{V}{Z} = \frac{V_0 e^{i\omega t}}{R \sqrt{1 + 1/(\omega\tau)^2} e^{i\phi}} = \frac{V_0}{R} \frac{e^{i(\omega t - \phi)}}{\sqrt{1 + 1/(\omega\tau)^2}}$$

similar to RL!

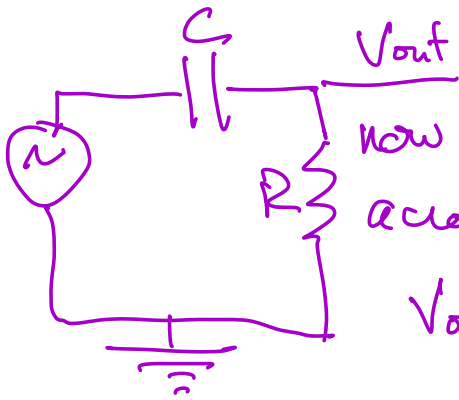


now ground circuit and look at V_{out} across resistor:

$$V_{out} = IR = \frac{V_0 \cos(\omega t - \phi)}{\sqrt{1 + 1/(\omega\tau)^2}}$$

as $\omega \rightarrow \infty$ $V_{out} \rightarrow V$ high pass filter

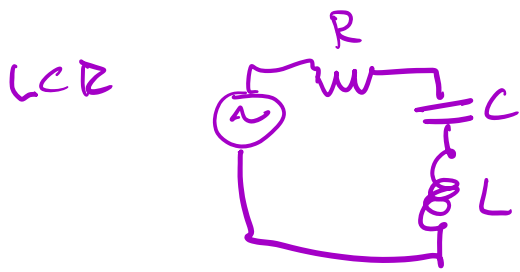swap $R \leftrightarrow C$ to get low pass filter



$$V = V_0 \cos \omega t \rightarrow V_0 e^{i\omega t}$$

complex impedance Z

$$Z = R + i\omega L + \frac{1}{i\omega C}$$

$$= R + i(\omega L - 1/\omega C)$$

write Z in exponential form $Z = r e^{i\phi}$

where $r = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$ and $\tan \phi = \frac{\omega L - 1/\omega C}{R}$

then use "Ohm's" law equivalent $V = IZ$

solve for $I = \frac{V}{Z} = \frac{V_0 e^{i\omega t}}{r e^{i\phi}} = \frac{V_0}{r} e^{i(\omega t - \phi)}$

now keep real part to get

$$I = \frac{V_0}{r} \cos(\omega t - \phi) = \frac{V_0 \cos(\omega t - \phi)}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

write $I(\omega) \equiv \frac{V_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$ gives

$$I(t) = I(\omega) \cos(\omega t - \phi)$$

properties of $I(\omega)$:

$$I(0) = 0 \quad (1/\omega C \text{ term dominates})$$

$$I(\infty) = 0 \quad (\omega L \text{ " " "})$$


$I(\omega_m)$ is a max when $\omega_m L - \frac{1}{\omega_m C} = 0$

$$\text{or } \omega_m = \frac{1}{\sqrt{LC}}$$

this is the resonance freq of LC part

$$\omega_m = \omega_0 = \frac{1}{\sqrt{LC}}$$

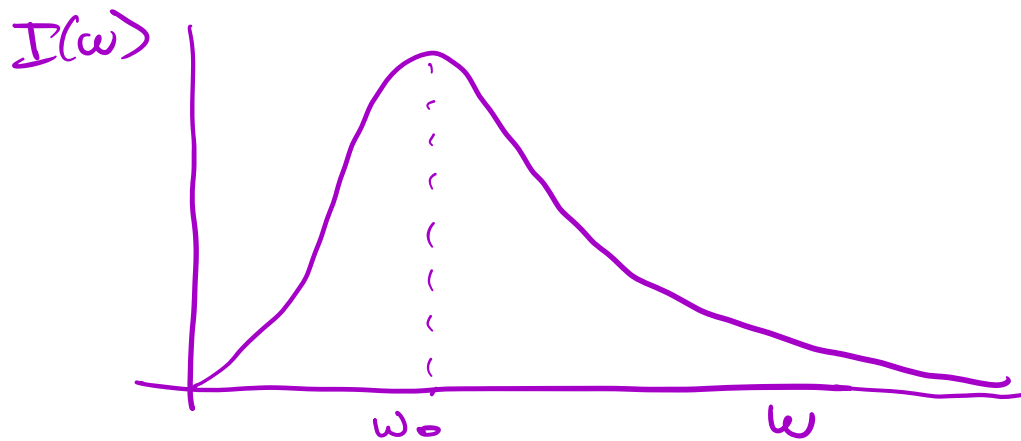Resonance! when drive system at $\omega = \omega_0$, maximizes response



note as $R \rightarrow 0$, $I(\omega_0) \rightarrow \infty$ so its more "peaked"

\Rightarrow this happens when you minimize R , or reduce energy loss thru resistance


can characterize how wide or peaked signal is

P dissipated is thru resistor (load)

$$P = I^2 R = \frac{V_0^2 \omega^2 (\omega t - \theta)}{R^2 + (L\omega - \frac{1}{C\omega})^2} \cdot R$$

max is at $P_{\max} = \frac{V_0^2}{R}$

find ω where $P = \frac{1}{2} P_{\max}$

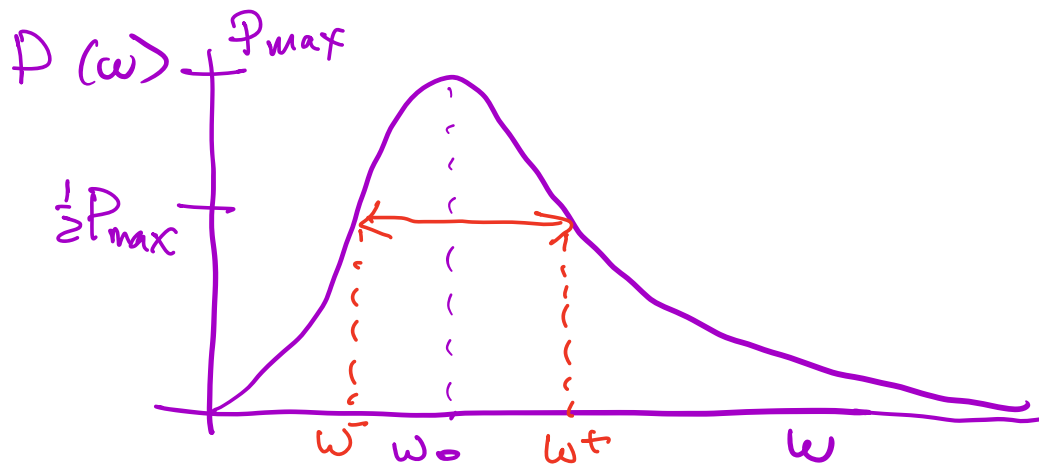

can calculate ω^- & ω^+

$$P(\omega) = \frac{1}{2} P_{\max} = \frac{V_0^2}{2R} = \frac{V_0^2 R}{R^2 + (\omega L - 1/\omega C)^2}$$

$$\text{so } 2R^2 = R^2 + (\quad)^2$$

$$R^2 = (\omega L - 1/\omega C)^2 \quad \text{or } \omega L - \frac{1}{\omega C} = \pm R$$

2 solutions as expected

$$\text{for } +R \text{ solution: } \omega L - \frac{1}{\omega C} = R$$

$$\omega^2 L - R\omega - 1/C = 0$$

$$\omega^2 - \frac{R}{L}\omega - \frac{1}{LC} = 0$$

$$\text{write as } \omega^2 - \omega/\tau - \omega_0^2 = 0 \quad \tau = L/R$$

$$\omega_0^2 = 1/LC$$

solves as
$$\omega = \frac{1}{2\tau} \pm \sqrt{\frac{1}{4\tau^2} + \omega_0^2}$$

only '+' solution gives $\omega > 0$ so write

$$\omega^+ = \frac{1}{2\tau} + \sqrt{\frac{1}{4\tau^2} + \omega_0^2}$$

after more math can show other solution

$$\omega^- = -\frac{1}{2\tau} + \sqrt{\frac{1}{4\tau^2} + \omega_0^2}$$

$$\Delta\omega = \omega^+ - \omega^- = \frac{1}{2\tau} + \sqrt{\quad} - \left(-\frac{1}{2\tau} + \sqrt{\quad} \right)$$

$$\Delta\omega = \frac{1}{\tau} = \frac{R}{L} \iff \text{makes sense that } \Delta\omega \sim R$$

quality factor "Q" = $\frac{\omega_0}{\Delta\omega}$ how peaked

$$Q = \frac{\omega_0}{\Delta\omega} = \omega_0 \tau = \frac{\omega_0 L}{R} \Rightarrow \text{ratio of complex to real impedance}$$

$$= \frac{X_L}{R}$$

want $Q \rightarrow \infty$ for highly selective filtering

note at resonance, $\omega_0 L = \frac{1}{\omega_0 C}$ or $X_L = X_C$

so $Q = \frac{X_C}{R} = \frac{X_L}{R}$ either way

average power delivered gets dissipated only thru real resistance R

$$\bar{P} = \frac{\int_0^T P(t) dt}{T} \quad \text{where } \omega T = 2\pi$$

$$\text{let } I(\omega) = \frac{V_0}{\sqrt{2}}$$

$$= \frac{1}{T} \int_0^T V_0 I(\omega) \cos \omega t \cos(\omega t - \phi) dt$$

$$= V_0 I(\omega) \int_0^T \cos \omega t [\cos \omega t \cos \phi + \sin \omega t \sin \phi] dt$$

$$\text{note: } \int_0^T \cos \omega t \sin \omega t dt = \frac{1}{2} \int_0^T \sin 2\omega t dt$$

$$= \frac{1}{4\omega} [-\cos 2\omega t]_0^T = \frac{1}{4\omega} [1 - \cos 2\pi] = 0$$

$$\int_0^T \cos^2 \omega t dt = \int_0^T \frac{1}{2} (1 + \cos 2\omega t) dt = \frac{T}{2}$$

$$\therefore \bar{P} = \frac{V_0 I(\omega) \cos \phi}{2} = \frac{V_0}{\sqrt{2}} \frac{I(\omega) \cos \phi}{\sqrt{2}}$$

$V_{rms} I_{rms}$

$$\bar{P} = V_{rms} I_{rms} \cos \phi$$

"power factor"

LCR circuits - diff. eqn's



$$V = V_0 \cos \omega t = V_R + V_L + V_C$$

$$V_R = IR = R \frac{dQ}{dt}$$

$$V_L = L \frac{dI}{dt} = L \frac{d^2Q}{dt^2}$$

$$V_C = \frac{Q}{C}$$


diff. eqn is: $L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = V_0 \cos \omega t$

solve for $Q(t)$

⇒ this is the same diff eq for a mass on a spring that is driven by a force $F(t)$ w/ wind resistance

$$F_{\text{spring}} = -kx$$
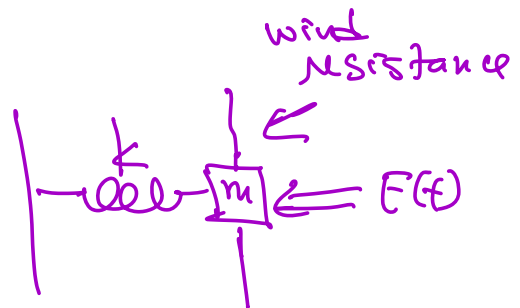
$$F_{\text{resist}} = -bv = -b \frac{dx}{dt}$$



$$ma = m \frac{d^2x}{dt^2} = -kx - bv + F(t)$$

$$\text{or } m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = F(t)$$

same equation!

$m \Leftrightarrow L$ inductance ("inertia")

$b \Leftrightarrow R$ resistance (energy dissipation)

$k \Leftrightarrow \frac{1}{c}$ "elastic" force


$F(t) \Leftrightarrow V(t)$ driver

so we know $x(t) = x(\omega) \cos(\omega t - \phi)$

$$\text{and } \omega_0^2 = \frac{1}{LC} \Rightarrow \frac{k}{m}$$

and $x(\omega)$ has same form as above

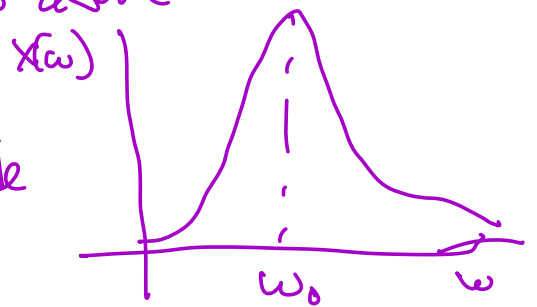
if you drive $\omega / \omega = \omega_0$, amplitude is maximized




quality factor $Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0 L}{R} \Rightarrow \frac{\omega_0 m}{b}$

as $b \rightarrow 0$, $x(\omega)$ becomes narrower

Parallel LCR

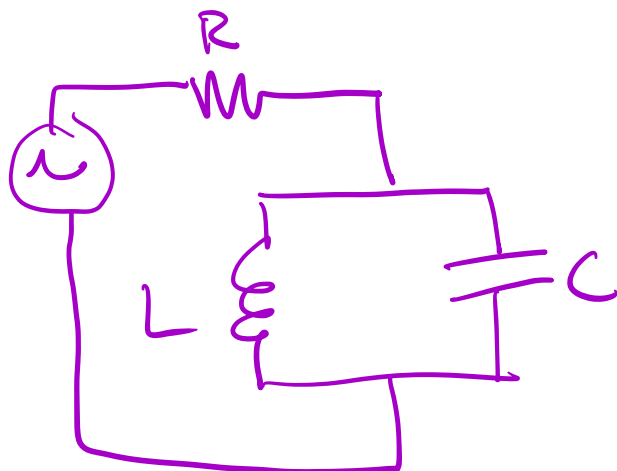


remember with resistors:

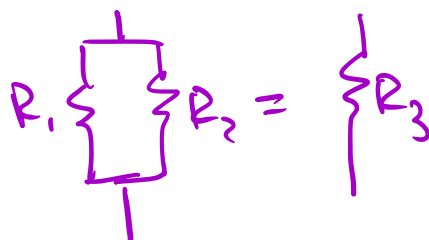

and $\frac{1}{R_3} = \frac{1}{R_1} + \frac{1}{R_2}$ parallel

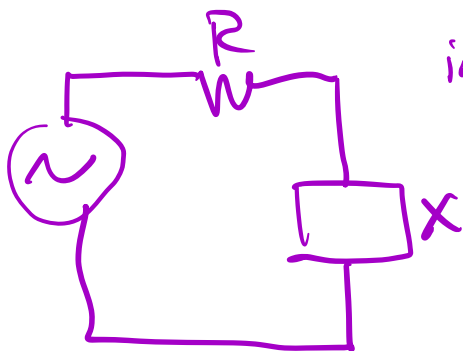so the complex impedance of the parallel L, C looks the same as for real impedances



impedance of "x" is:

$$\begin{aligned} \frac{1}{x} &= \frac{1}{x_L} + \frac{1}{x_C} = \frac{1}{i\omega L} + i\omega C \\ &= i\left(\omega C - \frac{1}{\omega L}\right) \\ x &= \frac{1}{i\left(\omega C - \frac{1}{\omega L}\right)} = \frac{-i}{\left(\omega C - \frac{1}{\omega L}\right)} \end{aligned}$$

we analyze this just like the series LCR

$$V = V_0 e^{i\omega t}$$

$$I = \frac{V}{Z}$$

$$Z = R - i\sigma \quad \text{where } \sigma = \frac{1}{\omega C - \frac{1}{\omega L}}$$

we write $Z = \sqrt{R^2 + r^2} e^{i\phi}$

$$\Rightarrow I(t) = \frac{V_0 e^{i\omega t}}{\sqrt{R^2 + r^2} e^{i\phi}} = \frac{V_0 e^{i(\omega t - \phi)}}{\sqrt{R^2 + r^2}}$$

keeping only the real parts:

$$I(t) = \frac{V_0 \cos(\omega t - \phi)}{\sqrt{R^2 + r^2}}$$

but $r = \frac{1}{\omega C - \frac{1}{\omega L}}$ parallel LCR


$$r = \omega L - \frac{1}{\omega C} \quad \text{series}$$

$r \rightarrow 0$ as $\omega \rightarrow \omega_0 = 1/\sqrt{LC}$ so $1/r \rightarrow \infty$

note: for series LCR, $\omega = \omega_0$ maximizes $I(\omega)$
for parallel $\omega = \omega_0$ minimizes "

$$\text{Power} = I^2 R = \frac{V_0^2 R}{R^2 + r^2} \cos^2(\omega t - \phi)$$

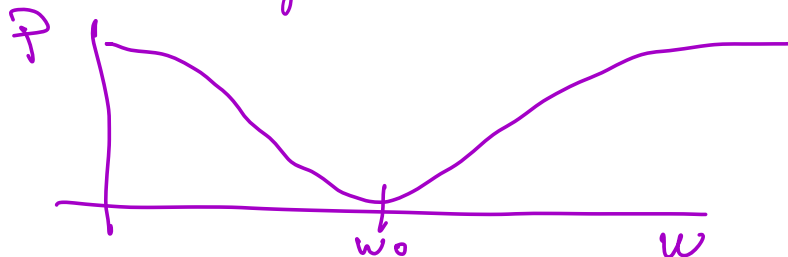
power is minimized at $\omega = \omega_0$!



Transformers

Faraday's law for coils w/ N turns

$$V_i = V_0 \cos \omega t$$

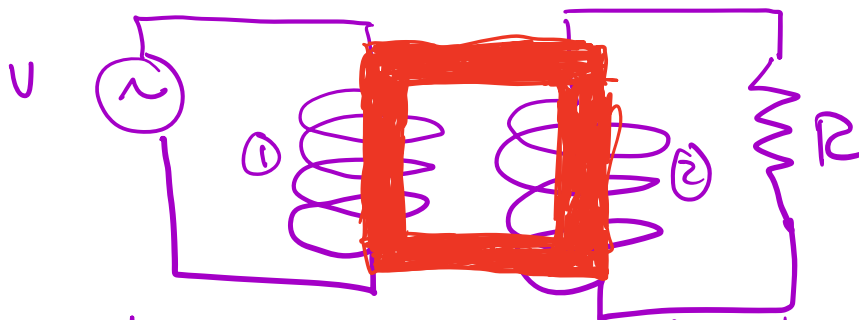

put iron core thru both coils, and connect them
 B will run around the core

coil 1 \equiv "primary"

coil 2 \equiv "secondary"

in primary, $\Phi_1 = B_1 A_1$

in secondary, $\Phi_2 = B_2 A_2$

$B_1 \neq B_2$! $B \propto \#$ field lines

but $\Phi_1 = \Phi_2$ flux is conserved

if $A_1 > A_2$ then more field lines would have to "squeeze" thru a smaller area

so if $\Phi_1 = \Phi_2$ then $\frac{d\Phi_1}{dt} = \frac{d\Phi_2}{dt} = \frac{d\Phi}{dt}$

now apply Faraday's law to each coil

$$\mathcal{E}_1 = -N_1 \frac{d\Phi}{dt} \quad \text{and} \quad \mathcal{E}_2 = -N_2 \frac{d\Phi}{dt}$$

$$\therefore \boxed{\frac{\mathcal{E}_1}{N_1} = \frac{\mathcal{E}_2}{N_2}} \quad \text{transformer equation}$$

ex: say we want $\mathcal{E}_1 = 10V$ and $\mathcal{E}_2 = 100V$

$$\frac{\mathcal{E}_1}{N_1} = \frac{\mathcal{E}_2}{N_2}$$

$$\frac{\mathcal{E}_1}{\mathcal{E}_2} = \frac{N_1}{N_2} = \frac{10}{100} = 0.1$$

if we build transformer with 100 turns in primary ($N_1 = 100$) then the secondary will need $N_2 = \frac{N_1}{0.1} = 10N_1 = 1000$ turns

this is called a "step up" transformer.
what about current?

Power has to be the same in both primary and secondary!

Power = $I \cdot V$ is energy/sec and energy is always conserved!


so $I_1 \mathcal{E}_1 = I_2 \mathcal{E}_2$ but $\mathcal{E}_2 = \mathcal{E}_1 N_2 / N_1$

$$\text{so } I_1 \mathcal{E}_1 = I_2 \mathcal{E}_1 \frac{N_2}{N_1} \Rightarrow \boxed{N_1 I_1 = N_2 I_2}$$

in previous example, $N_1 = 100, N_2 = 10$ so $I_1 > I_2$

step up transformer trades low V , high I for
high V , low I

How can we use this?

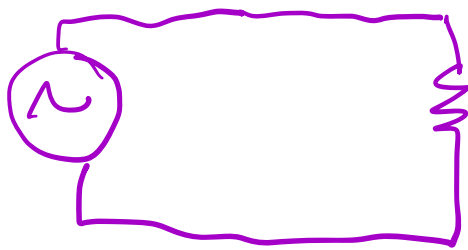

any power source pushes
current thru load R
can we neglect
resistance of wires?

loads usually have resistance $R \sim 100\Omega$
or more

Copper wire: 20 gauge = 0.032 in diameter
= 0.81 mm "

resistance is 10.15Ω per 1000 ft

so in lab, length of wire $\sim 1-10$ ft

total resistance of wire is $.06 \Omega$ for 1 ft

$.1 \Omega$ for 10 ft

R_{wires} is negligible compared to load resistances

14 gauge wire: $0.064 \text{ in} = 1.6 \text{ mm}$
 resistance $\approx 2.53 \Omega$ per 1000 ft

now build power plant that generates current
 and sends it ~ 20 miles on 14 gauge copper wire

20 miles = 10^5 ft

resistance of 14 gauge wire = $\frac{2.53 \Omega}{1000 \text{ ft}} \times 10^5 \text{ ft} = 253 \Omega$

Microwave oven has internal resistance $R_L = 24 \Omega$

if $V = 120 \text{ V}$ then it draws 5A


Power needed is $I \cdot V = 600 \text{ W}$

if wire resistance is 253Ω , then power
 dissipated in wires is

$$P_R = I^2 R = 5^2 \cdot 253 \approx 6,300 \text{ W}$$

so most of the power generated goes into heating
 transmission wires!

solution:

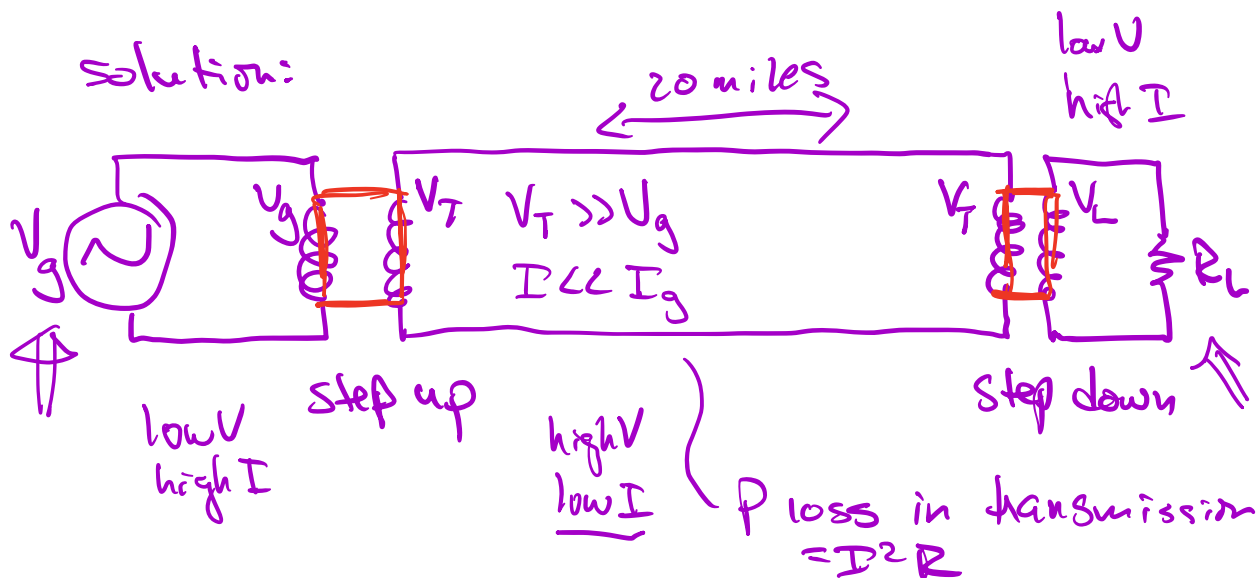

basic idea for transformers: transmit at high voltage / low current to minimize current losses: $P = I^2 R$

