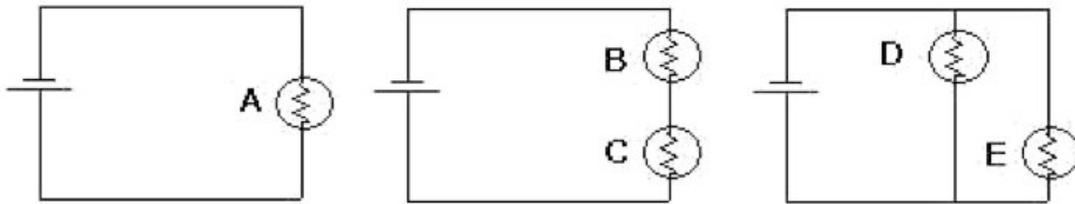


The three circuits below are constructed out of identical batteries and bulbs. (You can ignore the resistance in the wires and in the batteries.)



What is the order of the brightness of the bulbs?