Department of Physics Physics 374 Spring 2009 Due Wednesday, April 22, 2009

1.) Consider the Fourier series expansion for a function that obeys f(x) = f(x + 2L) and that takes the following form in the interval -L < x < L,

$$f(x) = x/L, \quad -L < x < L. \tag{1}$$

- a.) Plot the function for the interval -3L < x < 3L.
- **b.**) Use general symmetry arguments to extract all the Fourier series coefficients that can be determined from symmetry.
 - c.) Calculate the remaining Fourier coefficients.
- d.) Make a plot of the Fourier series result in the interval -L < x < L including terms up to n = 9.
- 2.) Consider the periodic function that obeys f(t + 2T) = f(t) and takes the following form on the interval -T < t < T,

$$f(t) = 1 - |t|/T, -T < t < T.$$
 (2)

- a.) Plot the function for the interval -3T < x < 3T.
- **b.**) Use general symmetry arguments to extract all the Fourier series coefficients that can be determined from symmetry.
 - c.) Calculate the remaining Fourier coefficients.
- d.) Make a plot of the Fourier series result in the interval -T < x < T including terms up to n = 9.
 - 3.) An input signal has the Fourier representation

$$v(t) = \int_{-\infty}^{\infty} dt e^{i\omega t} V(\omega), \tag{3}$$


where

$$V(\omega) = 1$$
, for $\omega < \omega_c$,
 $V(\omega) = 0$, for $\omega > \omega_c$,
 $\omega_c = 2\pi (250Hz)$. (4)


- a.) Plot $|V(\omega)|^2$ versus ω in the interval $0 < \omega < 1.5\omega_c$.
- **b.**) The signal v(t) is passed into a RC circuit as shown below to obtain the output signal o(t). The signal o(t) can also be expressed as a Fourier transform,

$$o(t) = \int_{-\infty}^{\infty} dt e^{i\omega t} O(\omega). \tag{5}$$

Plot the value of $|O(\omega)|^2$ versus omega using the same scales as in part a.).

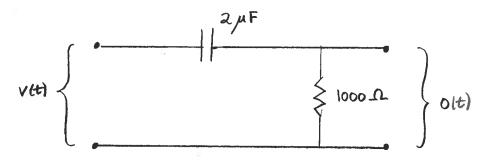

c.) The same signal is passed into a RL circuit as shown below. Plot the absolute value of $|O(\omega)|^2$ versus ω .

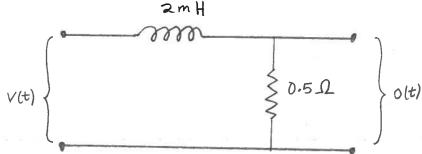

c.) The same signal is passed into a RLC as below. Plot the absolute value of $|O(\omega)|^2$ versus ω .

